

Step response of series R-L-C ckt :

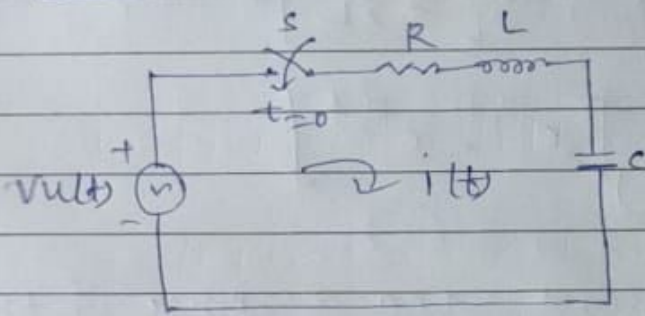


Fig: R-L-C ckt

Fig: R-L-C ckt shows

$$Ri(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int_{-\infty}^t i(t) dt = v(t)$$

$$Ri(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int_{-\infty}^0 i(t) dt + \frac{1}{C} \int_0^t i(t) dt = v(t)$$

Taking Laplace Transform on both sides, we get

$$R I(s) + L [s I(s) - i(0^+)] + \frac{1}{C} \left[\frac{q(0^+)}{s} + \frac{1}{C} \frac{I(s)}{s} \right] = \frac{V}{s}$$

$$R I(s) + L [s I(s) - i(0^+)] + \frac{1}{C} \frac{q(0^+)}{s} + \frac{1}{C} \frac{I(s)}{s} = \frac{V}{s}$$

Where $i(0^+)$ is the initial current through the inductor and $q(0^+)$ is the initial charge on the capacitor. Neglecting the all initial condⁿ, we get

$$R I(s) + L s I(s) + \frac{1}{C s} I(s) = \frac{V}{s}$$

$$I(s) \left[R + Ls + \frac{1}{Cs} \right] = \frac{V}{s}$$

$$I(s) \left[Ls + R + \frac{1}{Cs} \right] = \frac{V}{s}$$

$$I(s) \left[\frac{Lcs^2 + Rcs + 1}{c} \right] = \frac{V}{s}$$

$$I(s) = \frac{V \times c}{Lcs^2 + Rcs + 1}$$


$$= \frac{V}{Ls^2 + Rs + \left(\frac{1}{C}\right)}$$

$$= \frac{V}{L \left[s^2 + \left(\frac{R}{L}\right)s + \left(\frac{1}{LC}\right) \right]} = \frac{V}{L [(s-p_1)(s-p_2)]}$$

$$\text{Where } P_1, P_2 = -\frac{R}{2L} \pm \frac{1}{2L} \sqrt{R^2 - 4\frac{L}{C}}$$

$$i(t) = \frac{V/L}{(P_1 - P_2)} [e^{P_1 t} - e^{P_2 t}]$$

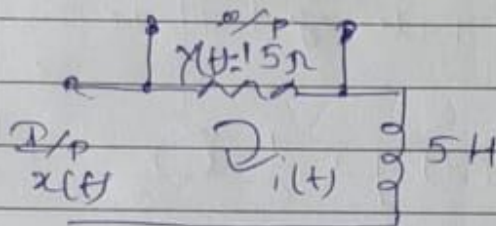Prob ① Find the unit step response of the ckt shown in fig.



$$x(t) = 15 i(t) + 5 \frac{di(t)}{dt}$$

Taking Laplace Transform on both sides, we have

$$X(s) = 15 I(s) + 5 [s I(s) - i(0^+)]$$

$$X(s) = 15 I(s) + 5 s I(s)$$

$$X(s) = I(s) [15 + 5s]$$

$$X(s) = 5 I(s) [3 + s]$$

$$\therefore I(s) = \frac{X(s)}{5(s+3)}$$

$$I/p \rightarrow x(t)$$

$$o/p \rightarrow i(t)$$

$$o/p \text{ value is } 15 \Omega$$

$$\text{output } Y(s) = I(s) \times 15$$

$$= \frac{3}{15} \times \frac{X(s)}{s+3}$$

$$= \frac{1}{5} X(s)$$

For unit step response

$$x(t) = u(t)$$

$$X(s) = \frac{1}{s}$$

6

$$\frac{\text{output}}{\text{Input}} = \text{Transfer}$$

$$\frac{15}{X(s)} =$$

$$Y(s) = \frac{3}{s+3} X(s)$$

$$= \frac{3}{s(s+3)}$$

$$= \frac{A}{s} + \frac{B}{s+3}$$

$$= \frac{1}{s} - \frac{1}{s+3}$$


By part of fraction
find the value of
A & B.

Taking $\pm$ LT, the unit step response of the given circuit is

$$y(t) = u(t) - e^{-3t} u(t)$$

$$= [1 - e^{-3t}] u(t) \quad \underline{\underline{\text{Ans}}}$$

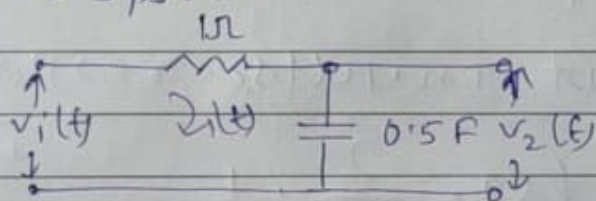- (2) A continuous, causal and linear time invariant system is shown in fig. Determine the unit impulse response and unit step response of the system.



$$v_1(t) = i(t) + \frac{1}{C} \int i dt$$

$$v_1(t) = i(t) + \frac{1}{0.5} \int i dt$$

Taking Laplace Transform on both sides,
we have

$$V_1(s) = I(s) + 2 \left[\frac{I(s)}{s} + \frac{v_2(0^+)}{s} \right] \rightarrow 0$$

$$V_1(s) = I(s) + 2 \frac{I(s)}{s}$$

$$V_1(s) = I(s) \left[1 + \frac{2}{s} \right] = I(s) \left[\frac{s+2}{s} \right]$$

$$I(s) = V_1(s) \times \frac{s}{s+2}$$

$$V_2(s) = \frac{1}{s} \int_0^\infty i(t) dt$$

Taking Laplace

$$= \frac{1}{0.5} \int_0^\infty i(t) dt$$

$$V_2(s) = \frac{2}{s} I(s)$$

Put the value of $I(s)$,

$$\therefore V_2(s) = \frac{2}{s} \times \frac{1}{s+2} \times \frac{s}{s+2}$$

$$V_2(s) = \frac{2}{s+2} V_1(s)$$

If the input is a unit impulse
i.e. $V_1(t) = \delta(t)$

$$V_1(s) = 1$$

The unit impulse response

$$V_2(s) = \frac{2}{s+2} \cdot 1$$

$$V_2(s) = \frac{2}{s+2}$$

Taking I LT

$$V_2(t) = 2e^{-2t} u(t)$$

If the input is a unit step

$$V_1(t) = u(t)$$

$$\text{then } V_1(s) = \frac{1}{s}$$

work

8

The unit step response is

$$V_2(s) = V_1(s) \times \frac{2}{s+2}$$

$$= \frac{1}{s} \times \frac{2}{s+2}$$

$$= \frac{2}{s(s+2)}$$

$$= \frac{A}{s} + \frac{B}{s+2}$$

After find the value of A & B from the partial fraction expansion


$$V_2(s) = \frac{1}{s} - \frac{1}{s+2}$$

$$V_2(t) = u(t) - e^{-2t}u(t)$$

- ⑤ obtain the voltage across the resistor in the ckt shown in fig. as a function of time for $t > 0$. Assume that $i(0) = 0$, $V_C(0) = 0$

① $V_1(t) = \delta(t)$

② $V_1(t) = u(t)$

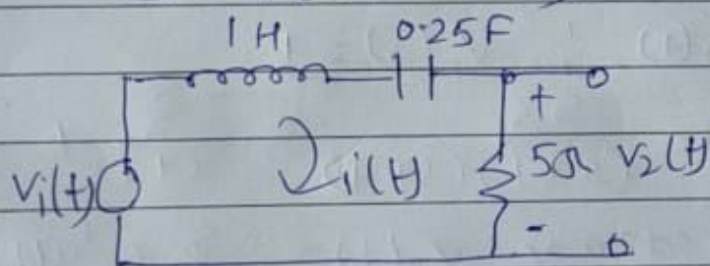

$$V_1(t) = L \frac{di(t)}{dt} + \frac{1}{C} \int i dt + R i(t)$$

$$V_1(t) = \frac{di(t)}{dt} + \frac{1}{0.25} \int i dt + 5 i(t)$$

Taking Laplace on both sides

$$V_i(s) = sI(s) - 1(0^+) + 4 \left[\frac{I(s)}{s} + \frac{v(0^+)}{s} \right] + 5I(s)$$

Neglecting all initial condⁿ we have

$$V_i(s) = sI(s) + 4 \frac{I(s)}{s} + 5I(s)$$

$$= I(s) \left[s + \frac{4}{s} + 5 \right]$$

$$V_i(s) = I(s) \left[\frac{s^2 + 5s + 4}{s} \right]$$

$$\therefore I(s) = V_i(s) \times \frac{s}{s^2 + 5s + 4}$$

output, $V_o(t) = R I(t)$

$$= 5 I(t)$$

Take Laplace

$$V_o(s) = 5 I(s)$$

$$= 5 \times V_i(s) \times \frac{s}{s^2 + 5s + 4}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{5s}{s^2 + 5s + 4}$$

[9] When $v_i(t) = \delta(t)$; $V_i(s) = 1$

After Partial fraction $V_o(s) = \frac{5s}{(s+1)(s+4)} = \frac{-\frac{5}{3}}{s+1} + \frac{20/3}{s+4}$

Impulse response $v_o(t) = -\frac{5}{3} e^{-t} u(t) + \frac{20}{3} e^{-4t} u(t)$

⑤ when $v_i(t) = u(t)$

$$V_i(s) = \frac{1}{s}$$

$$V_o(s) = \frac{1}{s} \cdot \frac{5s}{(s+1)(s+4)} = \frac{5}{(s+1)(s+4)}$$

After Partial fraction $V_o(s) = \frac{5/3}{s+1} - \frac{5/3}{s+4}$

$$v_o(t) = \frac{5}{3} e^{-t} u(t) - \frac{5}{3} e^{-4t} u(t) \quad \text{Ans}$$