
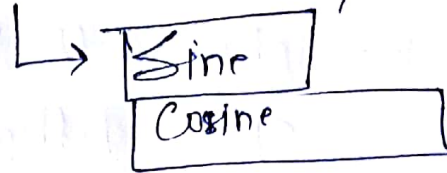


AC steady state (or) circuit Analysis :-

S³A → steady state sinusoidal Analysis.

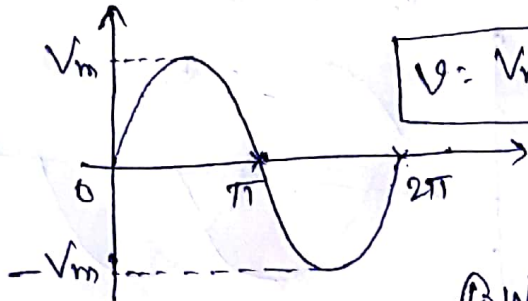

(a) Radian:




$$V = V_m \sin \omega t$$

Here $V_m \rightarrow$ Amplitude (voltage)
 $\omega =$ Angular velocity (rad/sec)


But $f = \frac{1}{T}$ ($\omega = \frac{2\pi}{T}$)

(b) Degree:

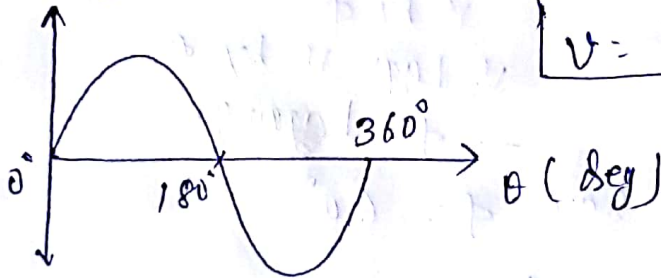

$$V = V_m \sin \theta$$

(c) Time.

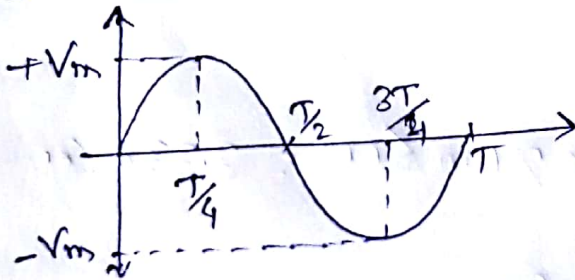

$$V = V_m \sin \left(\frac{2\pi}{T} t \right)$$

INDIA

$$f = 50 \text{ Hz}$$

$$T = \frac{1}{50} \text{ sec} = 20 \text{ mSec.}$$

$$\omega = 2\pi (50) = 100\pi \text{ or } 314 \text{ (rad/sec)}$$

$$1T = 2\pi = 360^\circ = 20 \text{ mSec.}$$

$\downarrow$ $\downarrow$ $\downarrow$
 radian Degree Time

Standard sinusoidal


$$V_n = V_m \sin(\omega t \pm \phi)$$

$\phi \rightarrow$ phase shift (deg)

$\downarrow$
Time shifting.

eg:-

$$V_1 = V_m \sin(\omega t + \phi)$$

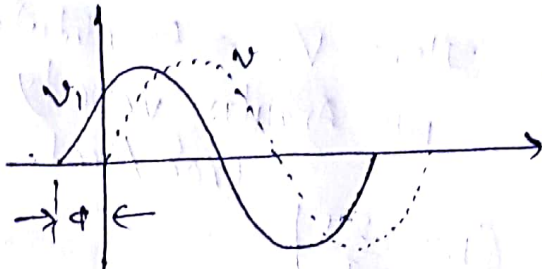


V_1 Comes early then V by ϕ

$V_1 =$ Leads V by ϕ°

$+\phi$ - Leading

$$V_2 = V_m \sin(\omega t - \phi)$$

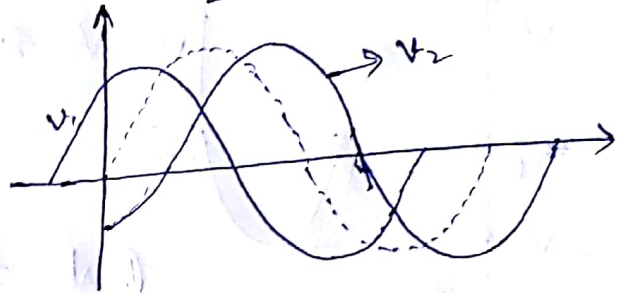

$V_2 \rightarrow$ Comes late to

V by ϕ

V_2 Lags V by ϕ

$-\phi$ - Lagging.

India

$f = 50\text{ Hz}$ say $\phi = 60^\circ$


$360^\circ \rightarrow 20\text{ mSec.}$

$160^\circ \rightarrow t_{\text{shift}}$

$$t_{\text{shift}} = \frac{60}{360^\circ} \times 20\text{ mSec} = 3.33\text{ mSec.}$$

PHASOR


Represent sinusoidal

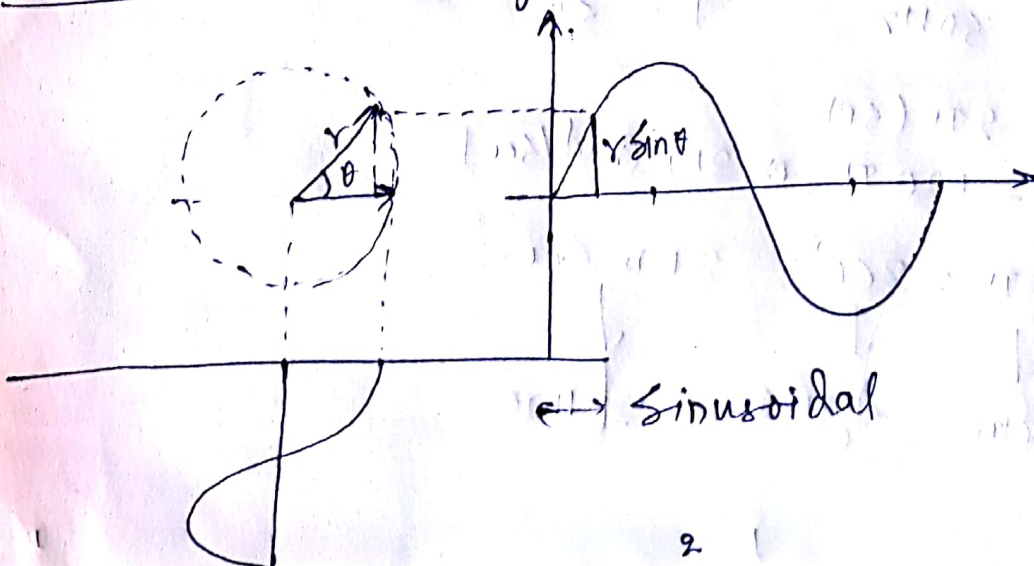


$$V = |V_m| \angle 0^\circ$$

$$V_1 = |V_m| \angle +\phi^\circ$$

$$V_2 = |V_m| \angle -\phi^\circ$$

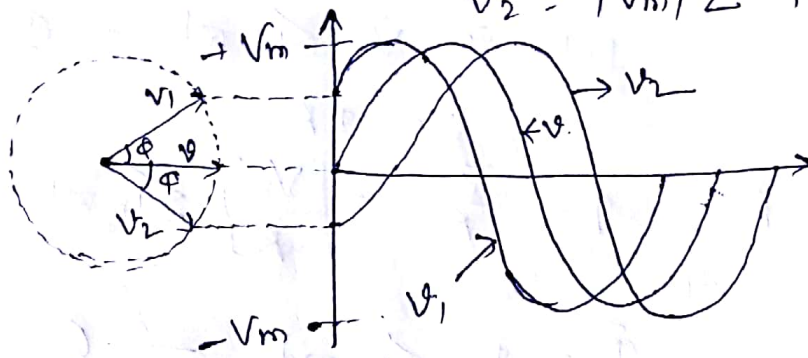

S-plane

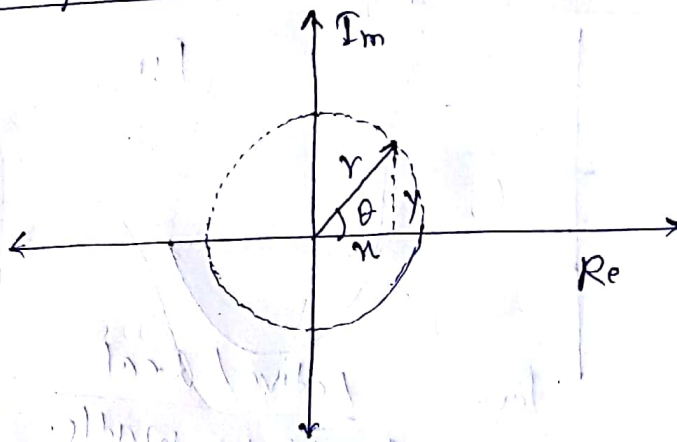

P (a) Rectangular $= (x + jy)$

(b) Polar $\rightarrow r \angle \theta$

(c) Euler's $\rightarrow r e^{j\theta}$

j is a powerful operator in (E.E.) Electrical Engineering

R Rectangular

$$0 + j0$$

$$1 + j0$$

$$0 + j1$$

$$1 + j1$$

$$0 - j1$$

P Polar

$$0 \angle 0$$

$$1 \angle 0$$


$$1 \angle 90^\circ$$

$$\sqrt{2} \angle 45^\circ$$

$$1 \angle -90^\circ$$

* Phasor Relationship b/w voltage and current in passive elements

(a) Resistor

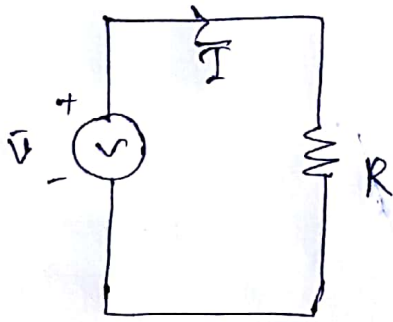

$$\text{Let } \bar{V} = V_m \sin \omega t \quad \text{--- (1)}$$



$$\therefore V = IR$$

$$I = \frac{\bar{V}}{R} = \left[\frac{V_m}{R} \right] \sin \omega t$$

$$\bar{I} = I_m \sin \omega t \quad \text{--- (2)}$$

$$\bar{V} = \bar{I} \cdot R$$

Phasor diagram

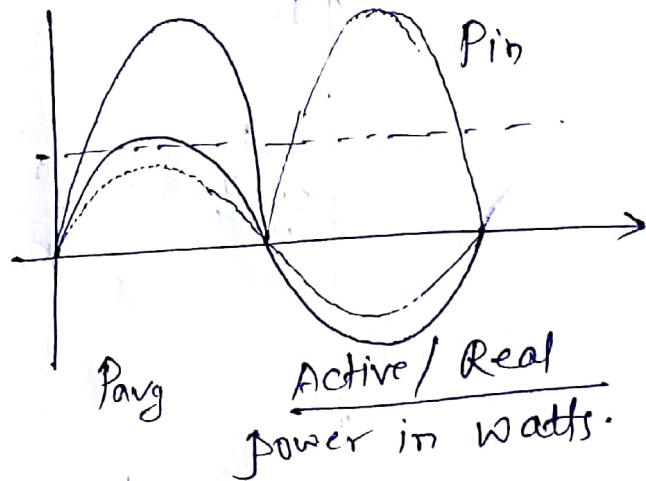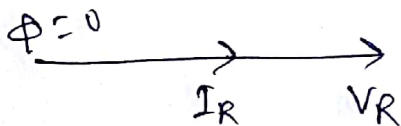

Power factor :-

$$\cos \phi = \cos 0^\circ = 1 \quad (\text{UPF}) \text{ Unity power factor.}$$


$$P_{\text{avg}} = \frac{1}{T} \int_0^T V(t) \cdot I(t) \cdot dt = \frac{1}{T} \int_0^T V_m I_m \sin^2 \omega t \, d(\omega t)$$

$$= \frac{V_m I_m}{T} \int_0^T \left[\frac{1 - \cos 2\omega t}{2} \right] d(\omega t)$$

$$P_{\text{avg}} = \frac{V_m I_m}{2} \left[\frac{1}{T} \int_0^T d\omega t - \frac{1}{T} \int_0^T \cos 2\omega t \, d\omega t \right]$$

$$P_{\text{avg}} = \frac{V_m I_m}{2} [1 - 0] = \frac{V_m I_m}{2}$$

$$P_{\text{avg}} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} = V_{\text{rms}} \cdot I_{\text{rms}} \quad (\text{watts})$$

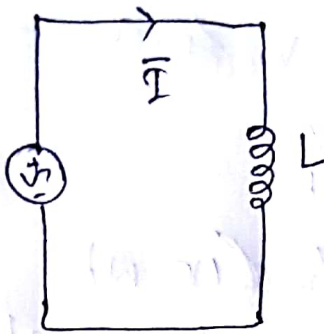Inductor:-

$$\therefore V = L \cdot \frac{d}{dt} (I_m \sin \omega t)$$

$$= L I_m \omega \cos \omega t$$

$$= \omega L I_m \sin(\omega t + 90^\circ)$$

$$\text{Let } \bar{I} = I_m \sin \omega t \quad \text{--- (1)} \quad \therefore \bar{V} = \omega L I_m \sin(\omega t + 90^\circ) \quad \text{--- (2)}$$

$$\therefore V = L \frac{dI}{dt}$$


$$\bar{V} = \omega L \underbrace{I_m \sin \omega t}_{\bar{I}} (j)$$

$$\bar{V} = j \omega L \bar{I}$$

$$\therefore \bar{V} = j X_L \bar{I}$$

$$X_L = \omega L = 2\pi f L$$

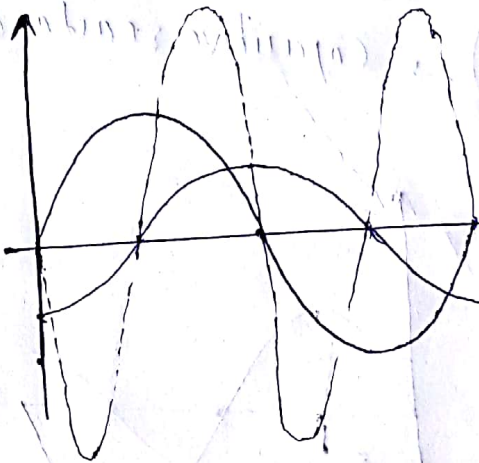$\hookrightarrow$ Inductive Reactance (Ω)




$$P_{av} = 0 \quad \text{ZPF}$$

If V & I freq is f

$$P \text{ then } P_{\text{freq}} = 2f \quad (\text{power freq})$$

Phasor diagram

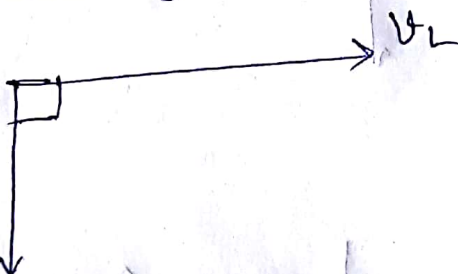


Power factor

$$\cos \phi = \cos 90^\circ = 0$$

(ZPF) (zero power factor)

Capacitor :-

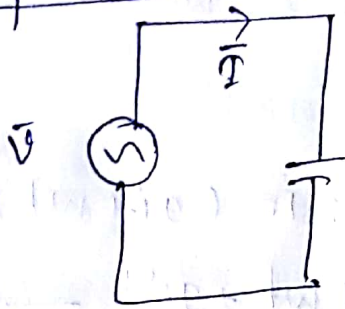

Let ~~the~~ $\bar{V} = V_m \sin \omega t$ — (1)

$$I = C \frac{dV}{dt}$$

$$\therefore \bar{I} = C \omega V_m \cos \omega t$$

$$= \omega C V_m \sin (90^\circ + \omega t)$$

$$\therefore \bar{I} = \omega C V_m \sin (\omega t + 90^\circ) \text{ — (11)}$$

$$\bar{I} = \omega C V_m \sin \omega t (j)$$


$$\boxed{\bar{I} = j \omega C \bar{V}}$$

$$\therefore \bar{V} = \frac{\bar{I}}{j \omega C}$$


$$\boxed{\bar{V} = -j X_C \bar{I}}$$

Here $X_C = \frac{1}{\omega C} = \left(\frac{1}{2\pi f C} \right) \rightarrow$ Capacitive reactance (Ω)

Phasor Diagram

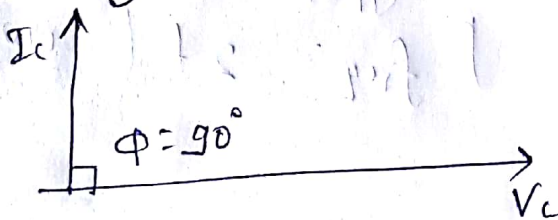

$$\boxed{P_{avg} = 0}$$

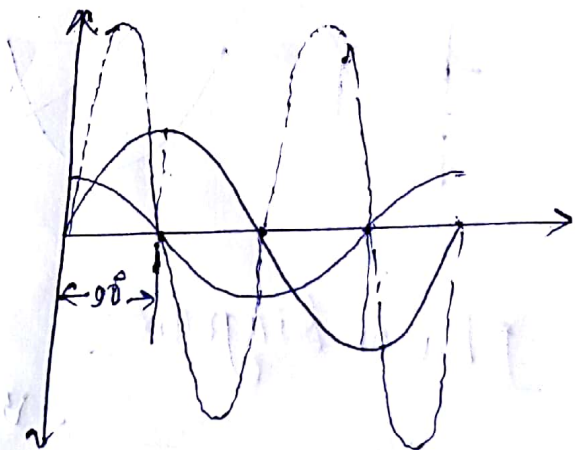


Power factor :

$$\boxed{\cos \phi = \cos 90^\circ = 0}$$

ZPF (Zero power factor)

(d) Series R-L

By: Er. Pranav Kumar

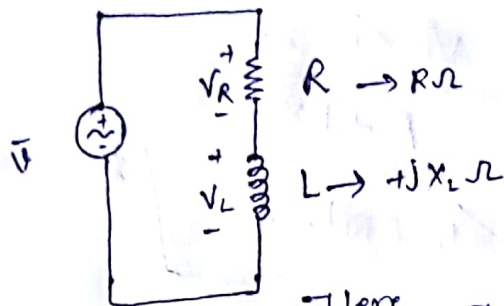

$$\bar{V} = \bar{V}_R + \bar{V}_L$$


$$= \bar{I} (R + jX_L)$$

$$\boxed{\bar{V} = \bar{I} Z}$$


Here $Z = R + jX_L$

↓

Impedance (Ω)

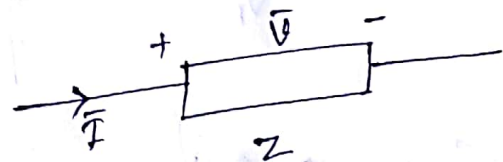

Impedance Δ

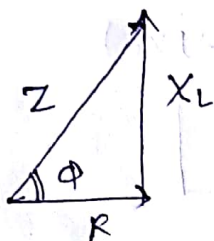

$$|Z| = \sqrt{R^2 + X_L^2}$$

$$\phi = \tan^{-1} \left(\frac{X_L}{R} \right) = \tan^{-1} \left(\frac{\omega L}{R} \right)$$

→ Impedance angle.

Power factor (p.f.)

$$\boxed{\cos \phi = \frac{R}{|Z|}}$$

$$\sin \phi = \frac{X_L}{|Z|}$$

$$Z = R + jX_L$$

$$I^2 Z = I^2 R + j I^2 X_L$$


$$\underbrace{VI}_{S} = \underbrace{I^2 R}_P + j \underbrace{I^2 X_L}_{Q_L}$$

$Q_L \rightarrow$ Reactive power (VAR's)

$I^2 R \rightarrow P \rightarrow$ Real power / Active / True power (watts)

$S \rightarrow$ Total / Apparent power (VA's)

Power Δ

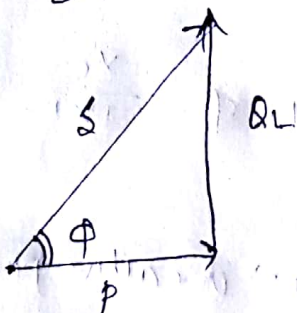

$$|S| = \sqrt{P^2 + Q_L^2}$$

$$\phi = \tan^{-1} \left(\frac{Q_L}{P} \right)$$


Power factor

$$\cos \phi = \frac{P}{S} \Rightarrow P = S \cos \phi = VI \cos \phi \text{ watts}$$

$$\sin \phi = \frac{Q_L}{S} \Rightarrow Q_L = S \sin \phi = VI \sin \phi \text{ VAR's}$$

} V, I
R.M.S
value

Phasor diagram :-

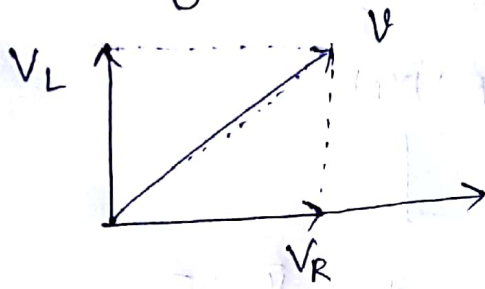


I lags V by $\phi \angle 90^\circ$

$$\bar{I} = \frac{\bar{V}}{Z} = \frac{V_m \sin \omega t}{R + jX_L}$$

$$\bar{I} = \frac{V_m}{|Z|} \sin(\omega t - \phi) \quad **$$

Series R.C.:

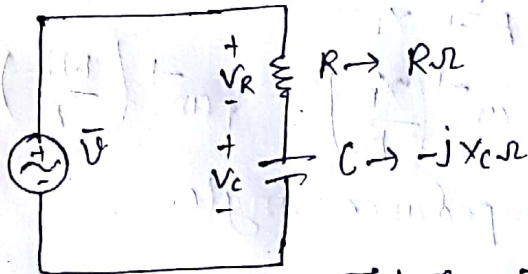


$$\bar{V} = \bar{V}_R + \bar{V}_C$$


$$\bar{V} = \bar{I} (R - jX_C)$$

$$\bar{V} = \bar{I} Z$$

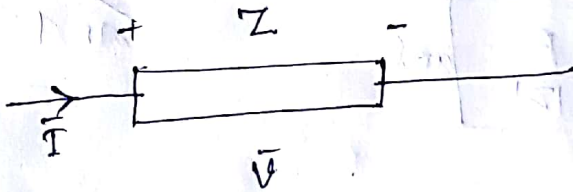Here $Z = R - jX_C$
 $\hookrightarrow$ Impedance.



Impedance Triangle:

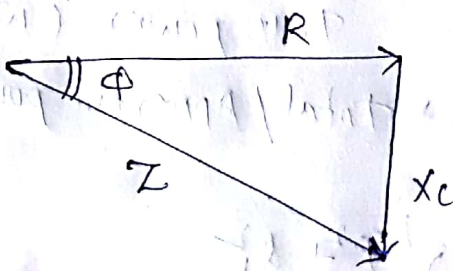

$$|Z| = \sqrt{R^2 + X_C^2}$$

$$\phi = \tan^{-1} \left(\frac{X_C}{R} \right) = \tan^{-1} \left(\frac{1}{\omega RC} \right)$$

$\hookrightarrow$ Impedance angle.

Power factor

$$\cos \phi = \frac{R}{|Z|}$$

$$\sin \phi = \frac{X_C}{|Z|}$$

$$I^2 Z = I^2 R - jX_C I^2$$

$$I \cdot V = I^2 R - jX_C I^2$$

$$\downarrow \quad \downarrow \quad \downarrow$$


$$S = P - jQ$$

$Q \rightarrow$ Reactive power (VAR's)

$P \rightarrow$ Real power / Active power

$S \rightarrow$ Total / Apparent power (VA's)

Power Triangle

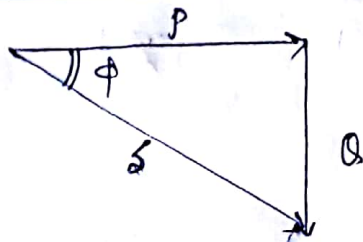


$$|S| = \sqrt{P^2 + Q^2}$$

$$\phi = \tan^{-1} \left(\frac{Q}{P} \right)$$

Power factor:-

$$\begin{aligned} \cos \phi &= \frac{P}{S} \Rightarrow P = S \cos \phi = VI \cos \phi \text{ watts} \\ \sin \phi &= \frac{Q}{S} \Rightarrow Q = S \sin \phi = VI \sin \phi \text{ VARs} \end{aligned} \left. \begin{array}{l} V, I \\ \text{r.m.s} \\ \text{value.} \end{array} \right\}$$

Phasor diagram:-

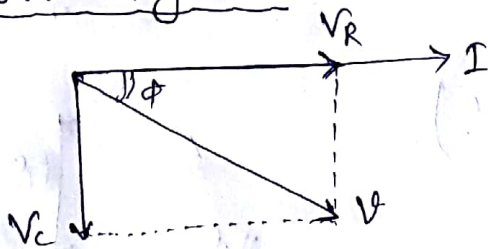

'I' Leads 'V' by $\phi < 90^\circ$


$$\bar{I} = \frac{\bar{V}}{R - jX_c} = \frac{V_m}{|Z|} \sin(\omega t + \phi)$$

Look point of view:-

+ $Q_L =$ (Absorbing VAR's Lagging)

- $Q_c =$ (Generating VAR's Leading)

* Series R-L-C

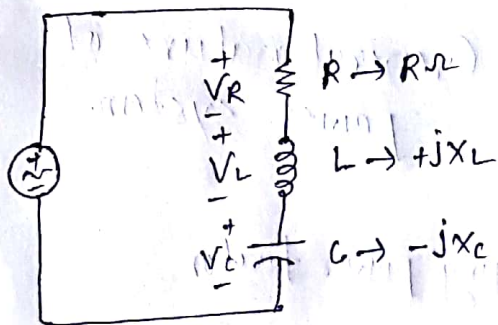

$$\bar{V} = \bar{V}_R + \bar{V}_L + \bar{V}_C$$

$$\bar{V} = \bar{I}R - jX_c \bar{I} + jX_L \bar{I}$$

$$\bar{V} = \bar{I} [R + j(X_L - X_c)]$$


$$\bar{V} = \bar{I} Z$$

Here $Z = R + j(X_L - X_c)$

$$|Z| = \sqrt{R^2 + (X_L - X_c)^2}$$

$$\phi = \tan^{-1} \left[\frac{X_L - X_c}{R} \right]$$

$\hookrightarrow$ Net impedance angle.

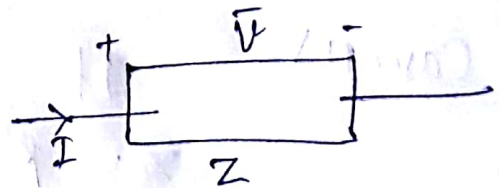

Power factor:-

$$\cos \phi = \frac{R}{|Z|} \quad \& \quad \sin \phi = \frac{X_{net}}{|Z|} = \frac{(X_L - X_C)}{|Z|}$$

Also

$$I^2 Z = I^2 R + j(I^2 X_L - I^2 X_C)$$



$$V \cdot I = I^2 R + j(I^2 X_L - I^2 X_C)$$

$$\boxed{S = P + j(Q_L - Q_C)}$$

$\downarrow$
 Q_{net}

$$S = \sqrt{P^2 + (Q_L - Q_C)^2}$$
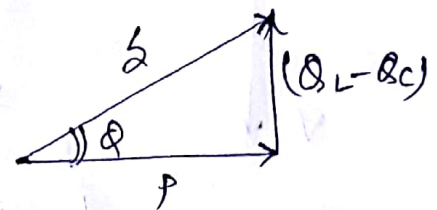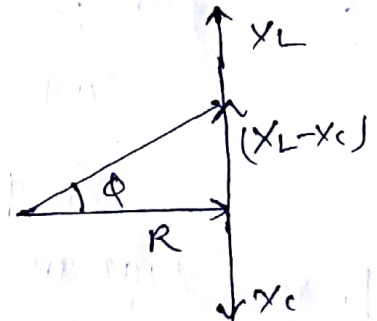
$$\therefore \phi = \tan^{-1} \left(\frac{Q_L - Q_C}{P} \right)$$



Power factor.

$$\cos \phi = \frac{P}{S} \quad \therefore \quad P = S \cos \phi = VI \cos \phi \text{ watts.}$$

$$\sin \phi = \frac{Q_{net}}{S} \Rightarrow Q_{net} = S \sin \phi = VI \sin \phi \text{ (VAR'S)}$$

Case(I)

$$\text{If } X_L > X_C$$

$$Z = R + jX_{net}$$

$\rightarrow$ R-L circuit

} General nature of power system.

I lags V by $\phi < 90^\circ$ Lagging power factor

Case(II)

$$\text{If } X_L < X_C$$

$$Z = R - jX_{net}$$

$\rightarrow$ R-C circuit

} Ferranti effect

I Leads V by $\phi < 90^\circ$

Case III:- If $X_L = X_C$


$Z = R \rightarrow$ Purely resistive.

I is in phase with ' V '.

Power factor = 1 (UPF)

Resonance.
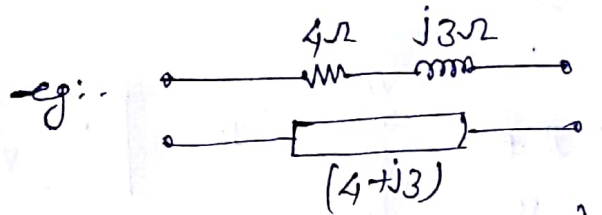
$$\begin{aligned} Z &= R \pm jX \\ \hookrightarrow Z &= R + jX_L \\ Z &= R - jX_C \end{aligned}$$




$Y = \frac{1}{Z}$ (Admittance Y)

$$Y = \frac{1}{4 + j3} \times \frac{4 - j3}{4 - j3} = \frac{4 - j3}{25} = (0.16 - j0.12) \text{ S.}$$

$$Y = G \pm jB \quad \begin{cases} \rightarrow Y = G - jB_L \\ \rightarrow Y = G + jB_C \end{cases}$$

Where $B_L \propto \frac{1}{X_L} \propto \frac{1}{\omega L} \propto \frac{1}{2\pi f L}$
 $\hookrightarrow$ Inductive susceptance. (S)

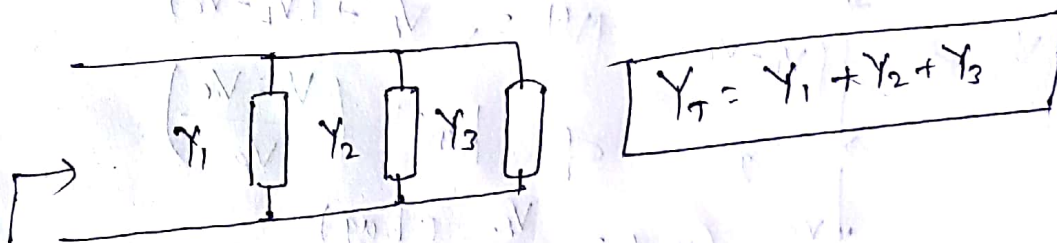
$B_C \propto \frac{1}{X_C} \propto \frac{1}{\frac{1}{\omega C}} \propto \omega C \propto \frac{2\pi f C}{1}$
 $\hookrightarrow$ Capacitive susceptance




* Phasor diagram:-

Series circuit. (I , ref.)

① Series RL

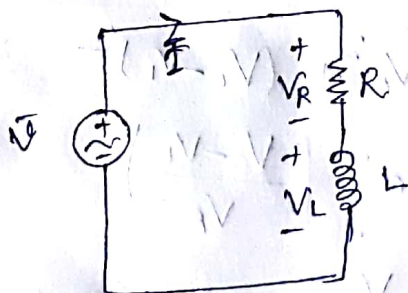
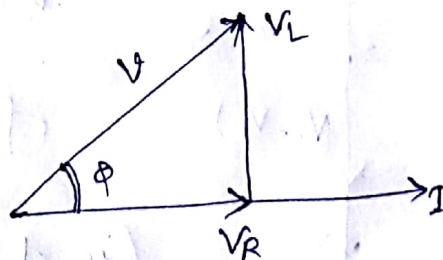
$$\begin{aligned} V_R &= IR \angle 0^\circ \\ V_L &= jX_L I = I X_L \angle +90^\circ \end{aligned}$$




$$V = \sqrt{V_R^2 + V_L^2}$$

$$\phi = \tan^{-1} \left(\frac{V_L}{V_R} \right)$$


$$\cos \phi = \frac{V_R}{V} \text{ (lagging)}$$

(b) Series R-C :-

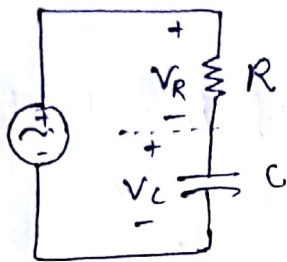

$$V_R = I \cdot R \angle 0^\circ$$
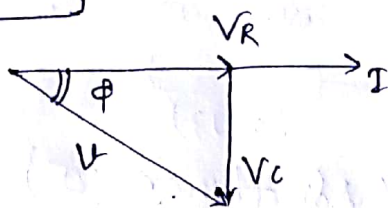
$$V_C = -jX_C I = I X_C \angle -90^\circ$$




$$V = \sqrt{V_R^2 + V_C^2}$$

$$\phi = \tan^{-1} \left(\frac{V_C}{V_R} \right)$$

$$\cos \phi = \frac{V_R}{V} \text{ (Leading)}$$

(c) Series R-L-C

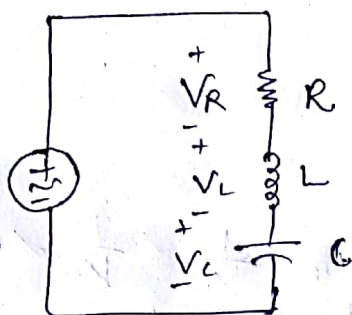


$$V_R = I R \angle 0^\circ$$

$$V_L = I X_L \angle +90^\circ$$

$$V_C = I X_C \angle -90^\circ$$

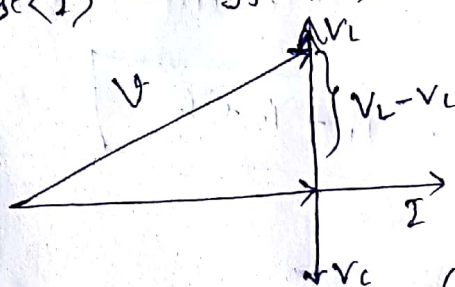Case (I) If $X_L > X_C \rightarrow V_L > V_C$




$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$\phi = \tan^{-1} \left(\frac{V_L - V_C}{V_R} \right)$$

$$\cos \phi = \frac{V_R}{V} \text{ (Lag)}$$

Case (II) :-

If $X_L < X_C \rightarrow V_L < V_C$

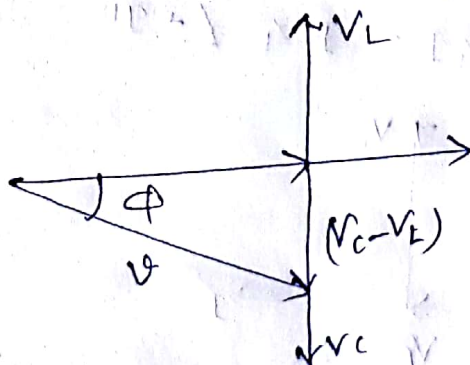


$$V = \sqrt{V_R^2 + (V_C - V_L)^2}$$

$$\phi = \tan^{-1} \left(\frac{V_C - V_L}{V_R} \right)$$

$$\cos \phi = \frac{V_R}{V} \text{ (Leading)}$$

Case (3):-

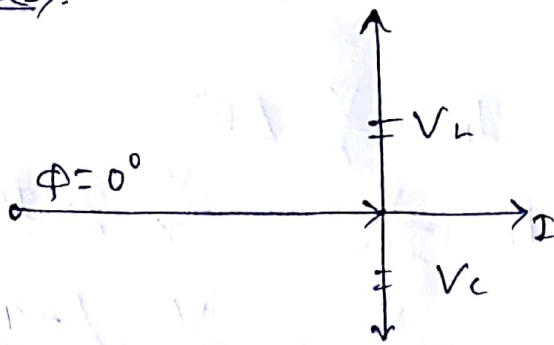

$$X_C = X_L$$



$$V_L = V_C$$

$$|V| = V_R$$

$$\phi = 0^\circ \quad \text{p.f.} = 1 (\text{UPF})$$

$\Rightarrow$ Parallel circuit $V \rightarrow \text{ref}$

① Parallel R-L ckt

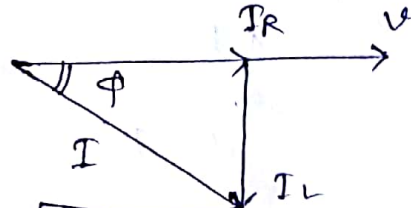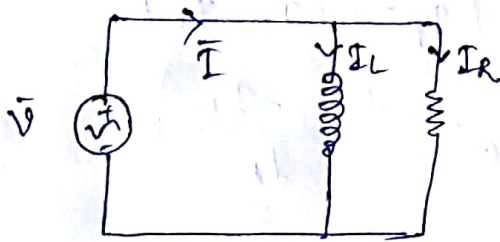

$$|I| = \sqrt{I_R^2 + I_L^2}$$

$$\phi = \tan^{-1} \left(\frac{I_L}{I_R} \right)$$


$$\cos \phi = \frac{I_R}{I} \text{ (Lagging)}$$

$$I_R = \frac{V}{R} \angle 0^\circ$$

$$I_L = \frac{V}{jX_L} = \frac{V}{X_L} \angle -90^\circ$$


$$I_L = \frac{V}{+jX_L} = \frac{V}{X_L} \angle -90^\circ$$

② Parallel R-C ckt :-

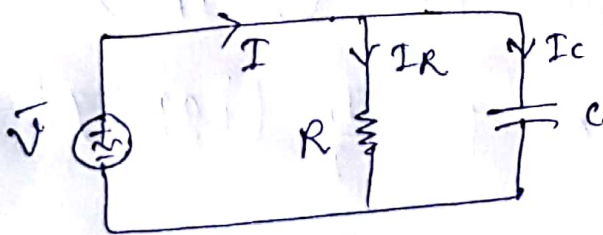

$$I_R = \frac{V}{R} \angle 0^\circ$$
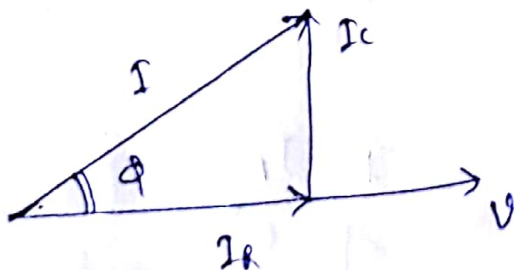
$$I_C = \frac{V}{-jX_C} = \frac{V}{X_C} \angle +90^\circ$$




$$|I| = \sqrt{I_R^2 + I_C^2}$$

$$\phi = \tan^{-1} \left[\frac{I_C}{I_R} \right]$$

$$\cos \phi = \frac{I_R}{I} \text{ (Leading)}$$

(C) Parallel R-L-C circuit :-

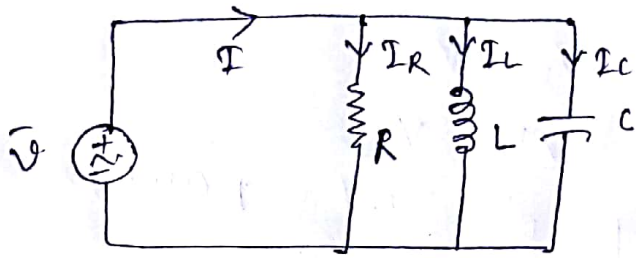


$$I_R = \frac{V}{R} \angle 0^\circ$$

$$I_L = \frac{V}{+jX_L} = \frac{V}{X_L} \angle -90^\circ$$

$$I_C = \frac{V}{-jX_C} = \frac{V}{X_C} \angle +90^\circ$$

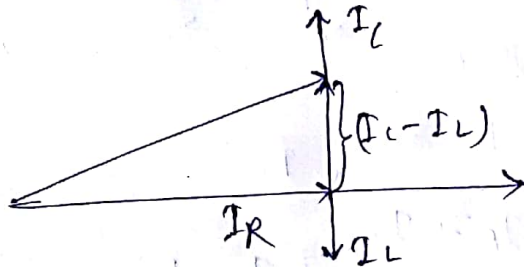Case (I) :- If $X_L > X_C \rightarrow I_L < I_C$




$$|I| = \sqrt{I_R^2 + (I_C - I_L)^2}$$

$$\Phi = \tan^{-1} \left(\frac{I_C - I_L}{I_R} \right)$$

$$\cos \Phi = \frac{I_R}{I} \text{ Leading.}$$

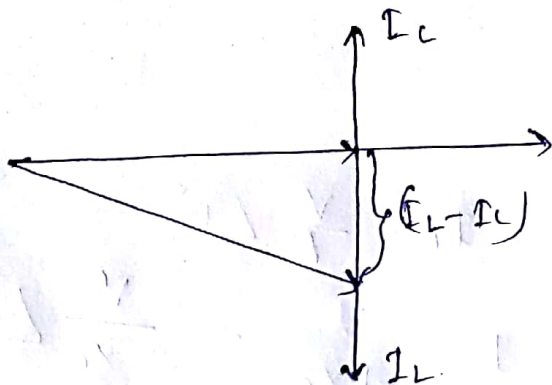Case (2) :- If $X_L < X_C \rightarrow I_L > I_C$




$$|I| = \sqrt{I_R^2 + (I_L - I_C)^2}$$

$$\Phi = \tan^{-1} \left(\frac{I_L - I_C}{I_R} \right)$$

$$\cos \Phi = \frac{I_R}{I} \text{ (Lagging)}$$

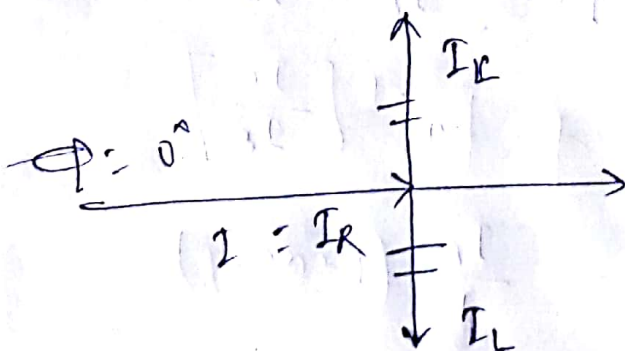Case (III) If $X_L = X_C \rightarrow I_L = I_C$



$$I = I_R$$

$$\Phi = 0^\circ$$

$$p.f. = 1 \text{ (UPF)}$$