

Behaviour of continuous and discrete timeLTI system (Linear Time invariant system)I/p = input Step response and impulse responses.I/p - o/p behaviour with aperiodic
convergent input

Let us consider R-L series ckt. in the ckt the switch is (S) closed at $t=0$. for step response the I/p excitation is $x(t) = V u(t)$. Applying KVL to the ckt.

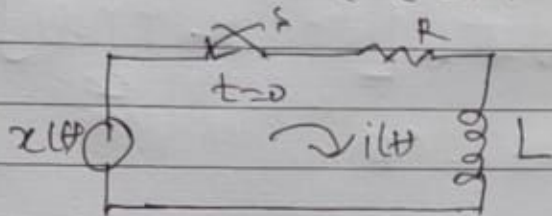


fig. R-L ckt

$$V u(t) = R i(t) + L \frac{di(t)}{dt}$$

Taking Laplace Transform on both side, we have

$$\frac{V}{s} = R I(s) + L [s I(s) - i(0^+)]$$

Since the current through Inductor cannot change instantaneously and since the current before $t=0$ is zero $i(0^+) = 0$

$$\frac{V}{s} = R I(s) + L s I(s)$$

$$= [R + Ls] I(s)$$

$$\therefore I(s) = \frac{V}{s} \cdot \frac{1}{(R + Ls)}$$

$$= \frac{V}{s(R + Ls)}$$

$$= \frac{V}{L} \cdot \frac{1}{s(s + \frac{R}{L})} = \frac{V}{L} \cdot \frac{K}{R} \left(\frac{1}{s} - \frac{1}{s + \frac{R}{L}} \right)$$

By partial fraction

$$I(s) = \frac{V}{R} \left(\frac{1}{s} - \frac{1}{s + \frac{R}{L}} \right)$$


Taking ILT, we get

$$i(t) = \frac{V}{R} \left[1 - e^{-\left(\frac{R}{L}\right)t} \right]$$

Impulse response

We know that the impulse response input excitation is $x(t) = \delta(t)$

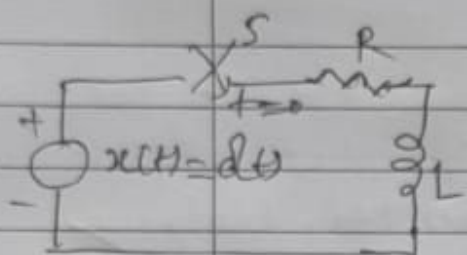The differential eqn. describing the R-L network would become



$$\delta(t) = Ri(t) + L \frac{di(t)}{dt}$$

Taking Laplace Transform on both sides, we have

$$1 = R I(s) + L [s I(s) - I(0^+)]$$

$$1 = (R + Ls) I(s)$$

$$I(s) = \frac{1}{R + Ls}$$

$$= \frac{1}{L} \cdot \frac{1}{(s + \frac{R}{L})}$$

Taking ILT on both sides.

$$i(t) = \frac{1}{L} e^{-\left(\frac{R}{L}\right)t} u(t)$$

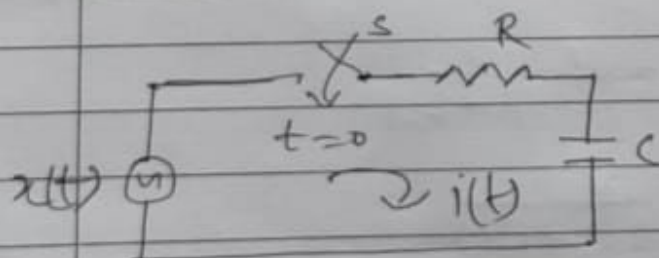
Step and Impulse responses of series R-C circuit

fig: R-C circuit

In the series R-C series circuit is shown.

Let us consider that the switch S is closed.

We know that for step response the input excitation is $x(t) = V u(t)$.

$$Ri(t) + \frac{1}{C} \int_{-\infty}^t i(t) dt = v(t)$$

$$Ri(t) + \frac{1}{C} \int_0^t i(t) dt + \frac{1}{C} \int_{-\infty}^0 i(t) dt = v(t)$$

Taking Laplace Transform on both sides, we have

$$RI(s) + \frac{1}{C} \left[\frac{I(s)}{s} \right] + \frac{1}{C} \{ L[q(t)] \} = \frac{V}{s}$$

$$RI(s) + \frac{1}{C} \left[\frac{I(s)}{s} + \frac{q(t)}{s} \right] = \frac{V}{s}$$

where $q(t)$ is the charge on the capacitor at $t=0$ if the capacitor is initially relaxed $q(t) = 0$

$$RI(s) + \frac{1}{Cs} I(s) = \frac{V}{s}$$

$$I(s) \left[R + \frac{1}{Cs} \right] = \frac{V}{s}$$

$$I(s) = \frac{V}{s} \cdot \frac{1}{R + \frac{1}{Cs}}$$

$$= \frac{V}{s} \cdot \frac{Cs}{RCs + 1}$$

$$= \frac{VC}{RC} \cdot \frac{1}{s + \left(\frac{1}{RC} \right)}$$


$$I(s) = \frac{V/R}{s + \left(\frac{1}{RC} \right)}$$

Taking ILT on both sides, we get

$$i(t) = \frac{V}{R} e^{-\frac{1}{RC} t}$$

Impulse response

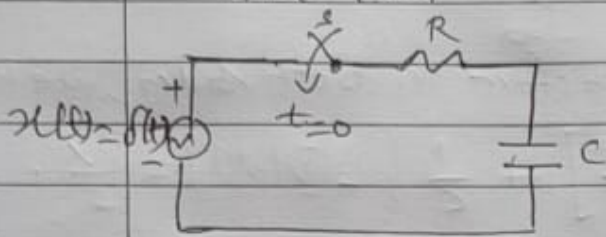We know that for the impulse response the I/P excitation $x(t) = \delta(t)$. Hence, the circuit



$$\delta(t) = Ri(t) + \frac{1}{C} \int_{-\infty}^t i(t) dt$$

$$\delta(t) = Ri(t) + \frac{1}{C} \int_0^t i(t) dt + \frac{1}{C} \int_{-\infty}^0 i(t) dt$$

Taking Laplace transform on both sides, we get

$$1 = R I(s) + \frac{1}{C} \left[\frac{I(s)}{s} \right] + \frac{1}{C} \{ \text{Initial condition} \}$$

$$1 = \left(R + \frac{1}{Cs} \right) I(s)$$

$$[q(t) = 0]$$

$$\therefore I(s) = \frac{1}{\left(R + \frac{1}{Cs} \right)} = \frac{1}{R \left[1 + \left(\frac{1}{RCs} \right) \right]}$$

$$I(s) = \frac{RCs}{R(RCs + 1)} = \frac{Cs}{RC \left[s + \left(\frac{1}{RC} \right) \right]}$$

$$= \frac{s}{R \left[s + \left(\frac{1}{RC} \right) \right]}$$

$$I(s) = \frac{1}{R} \left[\frac{s + \left(\frac{1}{RC} \right) - \left(\frac{1}{RC} \right)}{s + \left(\frac{1}{RC} \right)} \right]$$

$$I(s) = \frac{1}{R} \left[1 - \frac{1}{RC} \cdot \frac{1}{\left[s + \left(\frac{1}{RC} \right) \right]} \right]$$

Taking ILT on both sides, we get.

$$i(t) = \frac{1}{R} \left[\delta(t) - \frac{1}{RC} \cdot e^{-\frac{t}{RC}} u(t) \right]$$

Periodic signal which repeats itself at regular interval of time is called periodic signal.

and a signal which does not repeat at regular interval of time is called a non periodic or aperiodic signal.