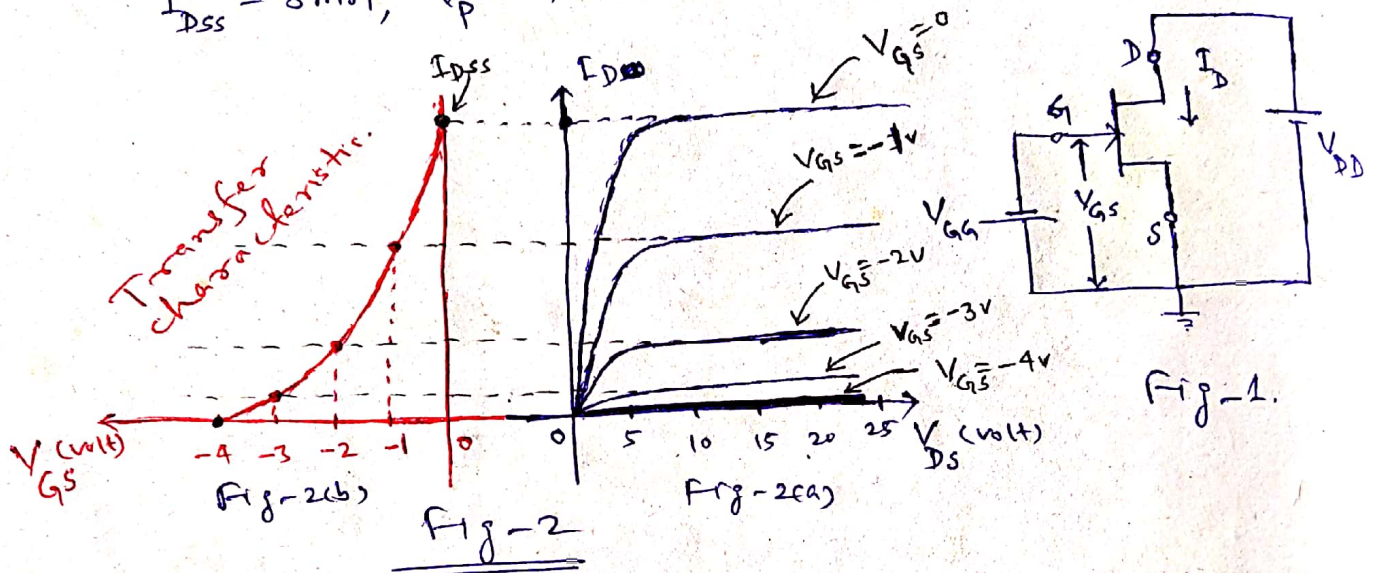


①

Obtaining of Transfer characteristic ($I_D - V_{GS}$) from Drain characteristic ($I_D - V_{DS}$) of FET

Let, us consider an example of FET with following specifications — (Fig-1)

$$I_{DSS} = 8 \text{ mA}, V_p = -4 \text{ volt}$$



From, Shockley's eqⁿ — $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$

When, $V_{GS} = 0\text{V}$, $I_D = I_{DSS} \left(1 - \frac{0}{-4}\right)^2 = I_{DSS} \Rightarrow I_D = I_{DSS} \Big|_{V_{GS}=0} = 8 \text{ mA}$

When, $V_{GS} = -1\text{V}$, $I_D = 8 \left(1 - \frac{-1}{-4}\right)^2 = 8 \times \left(\frac{3}{4}\right)^2 = 4.5 \text{ mA} \Rightarrow (V_{GS}, I_D) = (-1, 4.5)$

When, $V_{GS} = -2\text{V}$, $I_D = 8 \left(1 - \frac{-2}{-4}\right)^2 = 8 \times \frac{1}{4} = 2 \text{ mA} \Rightarrow (V_{GS}, I_D) = (-2, 2)$

When, $V_{GS} = -3\text{V}$, $I_D = 8 \left(1 - \frac{-3}{-4}\right)^2 = 8 \times \frac{1}{16} = 0.5 \text{ mA} \Rightarrow (V_{GS}, I_D) = (-3, 0.5)$

When, $V_{GS} = -4\text{V}$, $I_D = 8 \left(1 - \frac{-4}{-4}\right)^2 = 0 \text{ mA} \Rightarrow (V_{GS}, I_D) = (-4, 0)$

When, we plot I_D versus V_{GS} , we get a graph as shown in fig-2(b) which is called transfer characteristic of FET.

To draw in shorthand method, we can use —


$V_{GS} = 0$	$I_D = I_{DSS}$	$V_{GS} = V_p$, $I_D = 0$
$V_{GS} = 0.3V_p$	$I_D = I_{DSS}/2$	
$V_{GS} = 0.5V_p$	$I_D = \frac{I_{DSS}}{4}$	

FET Amplifier

②

Small signal Model. (or AC equivalent ck)

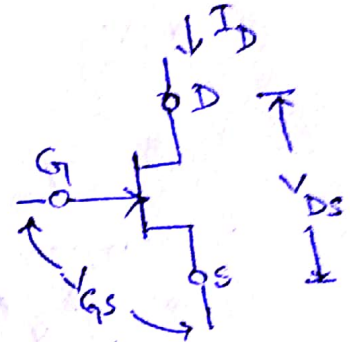We know that I_D is function of V_{DS} and V_{GS}



i.e. $I_D = f(V_{GS}, V_{DS})$

$$dI_D = \left(\frac{\partial f}{\partial V_{GS}}\right) dV_{GS} + \left(\frac{\partial f}{\partial V_{DS}}\right) dV_{DS}$$

or $\Delta I_D = \left(\frac{\Delta f}{\Delta V_{GS}}\right) V_{GS} + \left(\frac{\Delta f}{\Delta V_{DS}}\right) V_{DS}$ [for small signal]


$$\Rightarrow \Delta I_D = \left(\frac{\Delta I_D}{\Delta V_{GS}}\right) V_{GS} + \left(\frac{\Delta I_D}{\Delta V_{DS}}\right) V_{DS}$$

$\therefore g_m = \text{Transconductance} = \frac{\Delta I_D}{\Delta V_{GS}}$ and

$r_d = \text{Dynamic resistance} = \frac{\Delta V_{DS}}{\Delta I_D} = r_d$

$$\Delta I_D = g_m V_{GS} + \left(\frac{1}{r_d}\right) V_{DS}$$

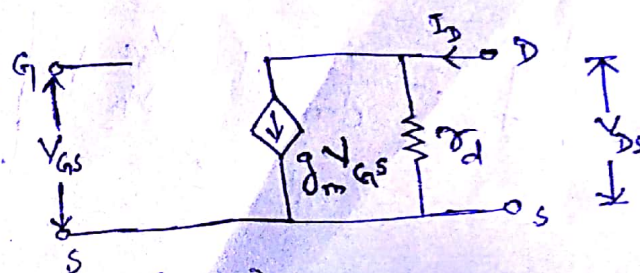
i.e. Drain current or output current represents the sum of two currents as $g_m V_{GS}$ and $\frac{V_{DS}}{r_d}$. Hence a FET can be represented as a ckt model as below —



(Fig-1)

3

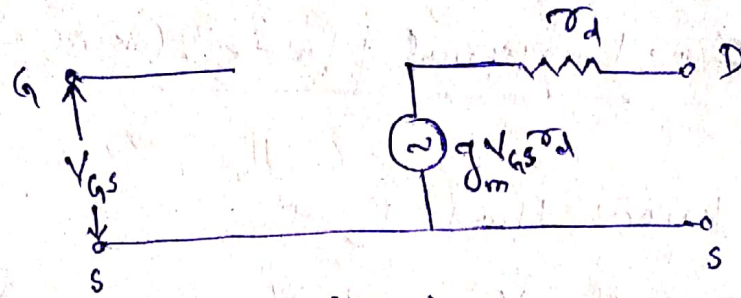The ckt model as in fig-1 can be modeled as below —




(Fig-2).

Since Amplification factor, $\mu = \frac{V_o}{V_{G_S}} = \frac{I_D r_d}{V_{G_S}}$

$$\text{or } \boxed{\mu = g_m r_d}$$

Fig-2) can be written as —

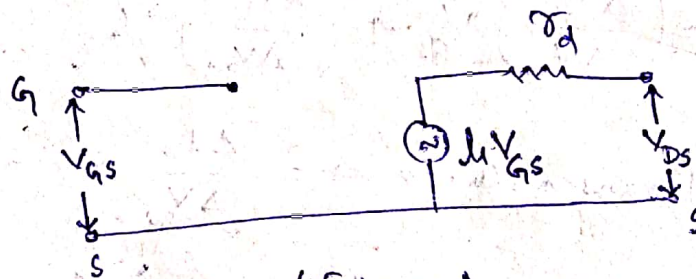

(Fig-3)

Now,

$$I_D = I_{DSS} \left(1 - \frac{V_{G_S}}{V_P}\right)^2$$

$$\text{or } \frac{dI_D}{dV_{G_S}} = - \frac{2I_{DSS}}{V_P} \left(1 - \frac{V_{G_S}}{V_P}\right) \Rightarrow g_m = - \frac{2I_{DSS}}{V_P} \left(1 - \frac{V_{G_S}}{V_P}\right)$$

When, $V_{G_S} = 0$, then —

$$g_{m0} = - \frac{2I_{DSS}}{V_P}$$

$$\therefore \boxed{g_m = g_{m0} \left(1 - \frac{V_{G_S}}{V_P}\right)}$$

Common Source FET amplifier in fixed bias Configuration (AC analysis)

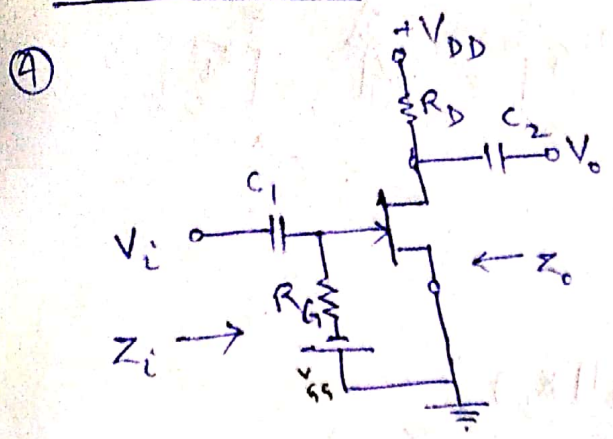


Fig-1.

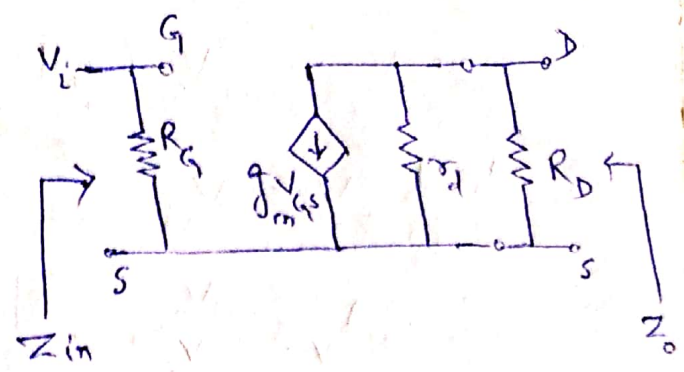


Fig-2

Above fig-1 represents common source FET amplifier. When, Ac analysis is done, all capacitors as C_1 , C_2 and various battery are assumed to be short circuited and the simplified equivalent ckt model is as shown in fig-2.

Input impedance (Z_i):

Since Gate to source is made in reverse bias, hence open-ckt equivalent impedance is given by —


$$Z_{in} = R_G$$

Output impedance (Z_o):

For calculating output impedance, we set, $V_i = 0$ which causes, $V_{GS} = 0$ and ckt is now as shown below —

$$\therefore Z_o = R_D \parallel r_d$$

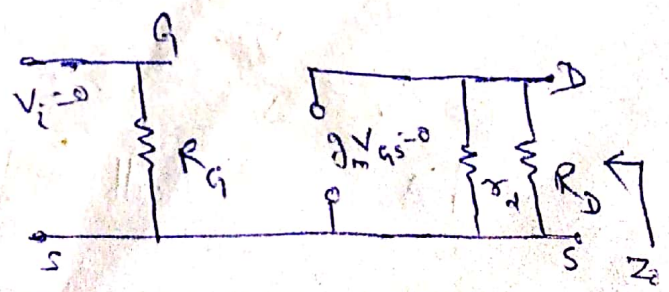If $r_d \geq 10R_D$ then $Z_o \approx R_D$.



Voltage gain (A_v) :-

⑤

$$V_o = I_D Z_o = -g_m V_{GS} Z_o$$

$$\text{or, } V_o = -g_m V_{GS} (r_d \parallel R_D)$$


$$\text{And, } V_{in} = V_{GS}$$

$$\therefore A_v = \frac{V_o}{V_{in}} = \frac{-g_m V_{GS} (r_d \parallel R_D)}{V_{GS}}$$


$$\Rightarrow \boxed{A_v = -g_m (r_d \parallel R_D)}$$

if $r_d \geq 10 R_D$


$$\text{then, } \boxed{A_v = -g_m R_D}$$

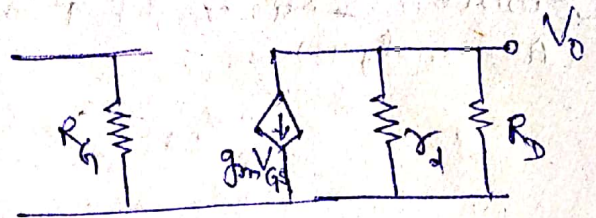

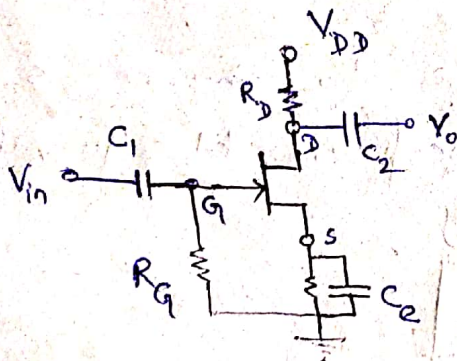
Common-source amplifier in self-bias configuration.



self-bias conf.

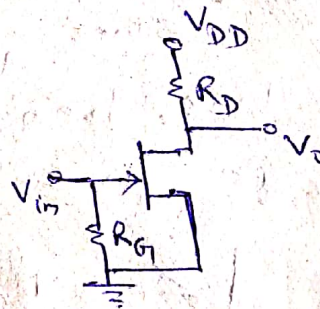

A.c equivalent

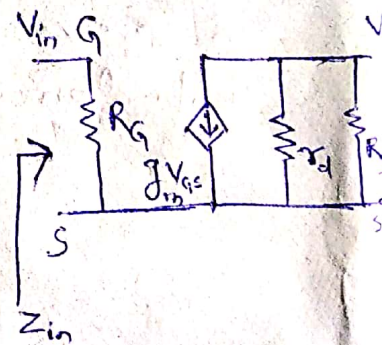

$$\boxed{Z_{in} = R_G}$$

$$Z_o = r_d \parallel R_D$$




$$A_v = \frac{V_o}{V_{in}} = \frac{-g_m V_{GS} (r_d \parallel R_D)}{V_{GS}} = -g_m (r_d \parallel R_D)$$

$$\boxed{A_v = -g_m (r_d \parallel R_D)}$$

$$\boxed{A_v = -g_m R_D} \text{ , if } r_d \geq 10 R_D$$

When, By-pass capacitor is removed—

⑥

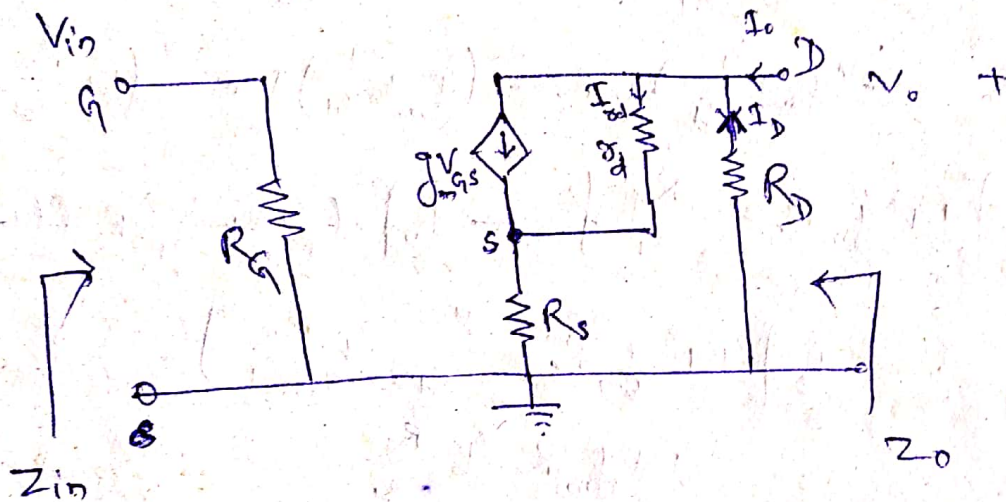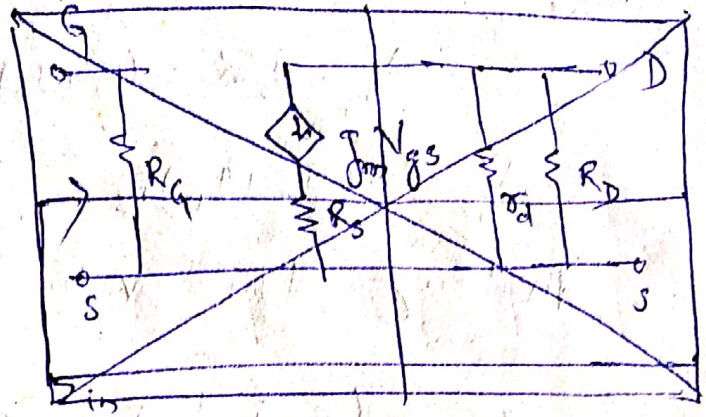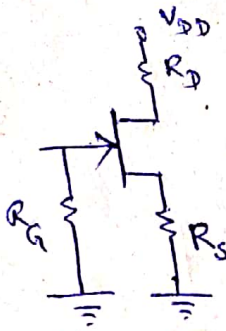

Output impedance (Z_o)

$$Z_o = \frac{V_o}{I_o} = -\frac{I_D R_D}{I_o} \quad \text{--- ①}$$

from output side—

$$I_o + I_D = g_m V_{gs} + I_{rd} \Rightarrow I_o = g_m V_{gs} + I_{rd} - I_D$$

$$\text{or, } I_o = g_m V_{gs} + \frac{V_o - V_{gs}}{r_d} - I_D \quad [\because V_g \approx 0]$$

$$I_o = g_m V_{gs} + \frac{V_o + V_{gs}}{r_d} - I_D = g_m V_{gs} + \frac{V_o}{r_d} + \frac{V_{gs}}{r_d} - I_D$$

$$I_o = (g_m + \frac{1}{r_d}) V_{gs} + \frac{V_o}{r_d} - I_D = (g_m + \frac{1}{r_d}) V_{gs} + \frac{-I_D R_D}{r_d} - I_D$$

$$\text{or, } I_o = (g_m + \frac{1}{r_d}) V_{gs} - (\frac{R_D}{r_d} + 1) I_D$$

$$\textcircled{7} \quad \text{or } I_o = \left(g_m + \frac{1}{r_d} \right) V_{gs} - \left(\frac{R_D}{r_d} + 1 \right) I_D \quad \textcircled{11}$$

Now,

$$V_{gs} = I_S R_S = (I_o + I_D) R_S$$

$$\Rightarrow V_{gs} = -(I_o + I_D) R_S$$

Putting this value in eqⁿ $\textcircled{11}$

$$\therefore I_o = - \left(g_m + \frac{1}{r_d} \right) (I_o + I_D) R_S - \left(\frac{R_D}{r_d} + 1 \right) I_D$$

$$\text{or, } I_o = - \left(g_m + \frac{1}{r_d} \right) I_o R_S - \left(g_m + \frac{1}{r_d} \right) I_D R_S - \left(1 + \frac{R_D}{r_d} \right) I_D$$

$$\text{or, } I_o \left[1 + g_m R_S + \frac{R_S}{r_d} \right] = - I_D \left[\left(g_m + \frac{1}{r_d} \right) R_S + \left(1 + \frac{R_D}{r_d} \right) \right]$$

$$\text{or, } I_o = \frac{- I_D \left[1 + g_m R_S + \frac{R_S}{r_d} + \frac{R_D}{r_d} \right]}{1 + g_m R_S + \frac{R_S}{r_d}}$$

$$\therefore Z_o = - \frac{I_D R_D}{I_o} = \frac{- I_D R_D}{\frac{- I_D \left[1 + g_m R_S + \frac{R_S}{r_d} + \frac{R_D}{r_d} \right]}{1 + g_m R_S + \frac{R_S}{r_d}}}$$

$$Z_o = \left(\frac{1 + g_m R_S + \frac{R_S}{r_d}}{1 + g_m R_S + \frac{R_S}{r_d} + \frac{R_D}{r_d}} \right) R_D$$

if $\left(1 + g_m R_S + \frac{R_S}{r_d} \right) \gg \frac{R_D}{r_d}$ then

$$Z_o = \frac{\left(1 + g_m R_S + \frac{R_S}{r_d} \right)}{\left(1 + g_m R_S + \frac{R_S}{r_d} \right)} \cdot R_D \approx R_D$$

$$\boxed{Z_o = R_D}$$


Voltage gain (A_v)

⑧

$$A_v = \frac{V_o}{V_{in}} = \frac{-I_D R_D}{V_{in}} \quad \text{--- (11)}$$

$$V_{in} = V_{G_S} + V_{R_S} \Rightarrow V_{G_S} = V_{in} - V_{R_S}$$

from small signal model —

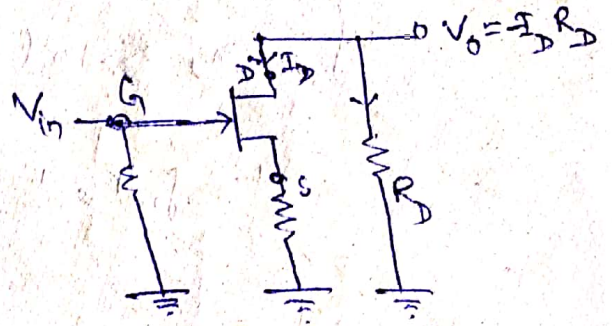

$$I_D = g_m V_{G_S} + \left(\frac{1}{r_d} \right) V_{D_S}$$

$$\text{or, } I_D = g_m V_{G_S} + \frac{1}{r_d} (V_o - V_{R_S}) = g_m V_{G_S} + \frac{-I_D R_D - I_D R_S}{r_d}$$

Putting $V_{G_S} = V_{in} - V_{R_S}$, we get —

$$\begin{aligned} I_D &= g_m (V_{in} - V_{R_S}) - \frac{I_D R_D + I_D R_S}{r_d} \\ &= g_m V_{in} - g_m I_D R_S - \frac{I_D (R_D + R_S)}{r_d} \\ &= g_m V_{in} - I_D \left(g_m R_S + \frac{R_D + R_S}{r_d} \right) \end{aligned}$$

$$\text{or, } I_D \left(1 + g_m R_S + \frac{R_D + R_S}{r_d} \right) = g_m V_{in}$$

$$\text{or, } I_D = \frac{g_m V_{in}}{1 + g_m R_S + \frac{R_D + R_S}{r_d}}$$

Putting the value of I_D into eqⁿ (11)

$$A_v = - \frac{R_D}{V_{in}} \cdot \frac{g_m V_{in}}{1 + g_m R_S + \frac{R_D + R_S}{r_d}} = - \frac{g_m R_D}{1 + g_m R_S + \frac{R_D + R_S}{r_d}}$$

$$\textcircled{9} \quad \therefore A_v = - \frac{g_m R_D}{1 + g_m R_S + \frac{R_D + R_S}{r_d}}$$

if $r_d \gg 10(R_D + R_S)$ then

$$1 + g_m R_S + \frac{R_D + R_S}{r_d} \approx 1 + g_m R_S$$

$$\therefore A_v = - \frac{g_m R_D}{1 + g_m R_S} \quad \checkmark$$

Common-source amplifier is voltage-divider biased.

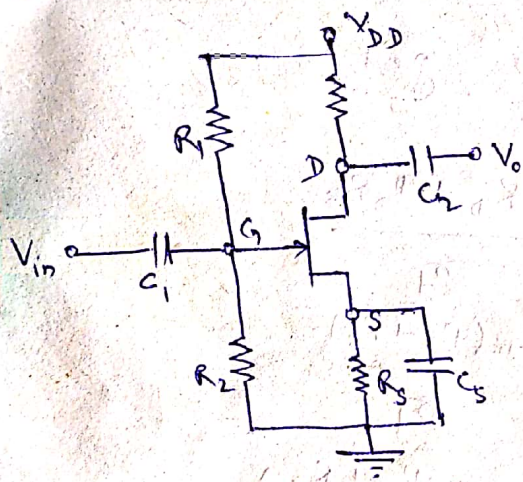


Fig-1.

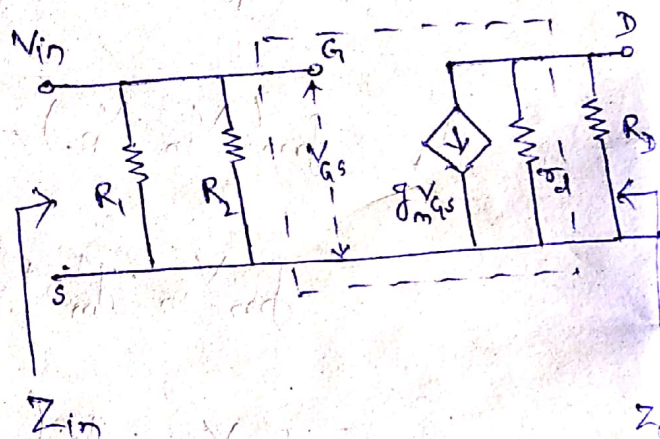


Fig-2


Fig-1. represents FET amplifier in voltage divider biasing configuration. Figure-2 represent its equivalent a.c model by shorting all d.c components.

Input impedance (Z_{in})

$$Z_{in} = R_1 \parallel R_2$$

Output impedance (Z_o) :-

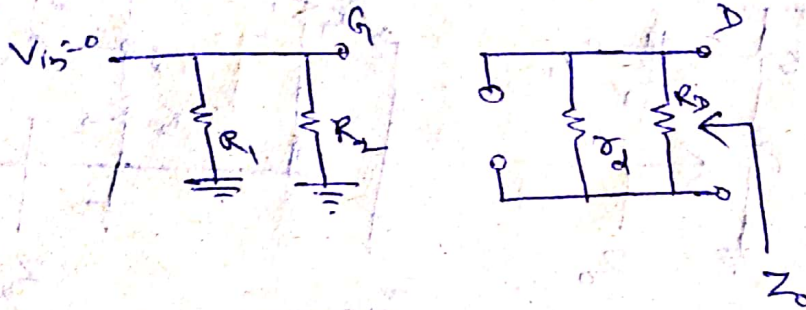- ⑩ For calculating output impedance, we set input as $V_{in} = 0$. that causes V_{GS} to 0. Thus, simplified ckt is _____



$$Z_o = r_d \parallel R_D$$

if $r_d \gg 10 R_D$ then $Z_o \approx R_D$

Voltage gain (A_v) :-

$$A_v = \frac{V_o}{V_{in}} = \frac{-I_D Z_o}{V_{GS}}$$

$$\text{or } A_v = \frac{-g_m V_{GS} (r_d \parallel R_D)}{V_{GS}} = -g_m (r_d \parallel R_D)$$

$$\therefore A_v \approx -g_m (r_d \parallel R_D)$$

if $r_d \gg 10 R_D$ then —

$$A_v = -g_m R_D$$

Common-Drain (Source follower) amplifier

(11)

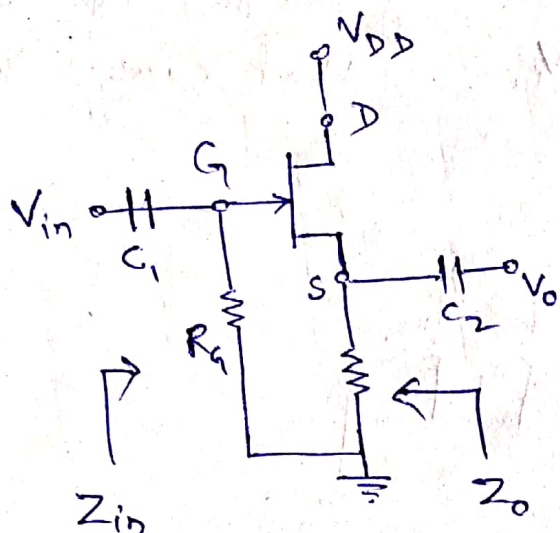


Fig-1.

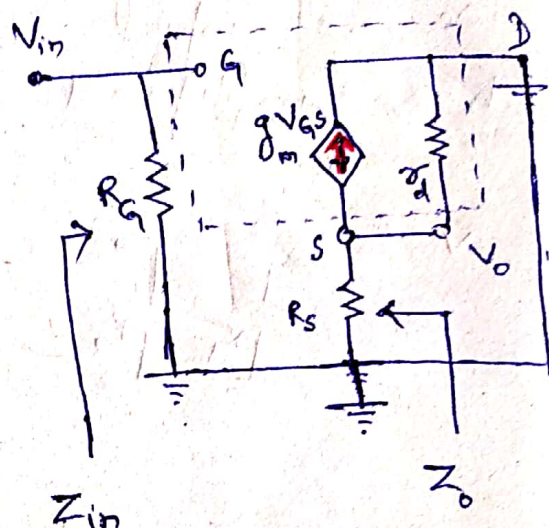


Fig-2. A-c equivalent model.

Input impedance (Z_{in})

$$Z_{in} = R_g$$

Output impedance (Z_o) :-


$$Z_o = \frac{V_o}{I_o}$$

Here $V_o = V_{Rs} = V_{SG} = -V_{GS}$

$$\Rightarrow V_o = -V_{GS} \quad \text{--- (1)}$$

This is the fact due to which current source is reversed

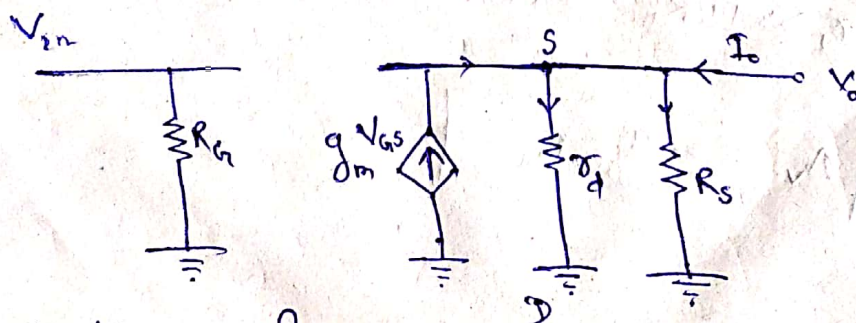Now, ckt as in fig-2 can be modeled as below



Applying KCL at s

$$I_o + g_m V_{GS} = I_{sd} + I_{Rs}$$

(12) or, $I_o + g_m V_{GS} = \frac{V_o}{r_d} + \frac{V_o}{R_s}$

or, $I_o = V_o \left(\frac{1}{r_d} + \frac{1}{R_s} \right) - g_m V_{GS}$

Putting value of V_{GS} from eq (1)

$$I_o = V_o \left(\frac{1}{r_d} + \frac{1}{R_s} \right) - g_m (-V_o) = V_o \left[\frac{1}{r_d} + \frac{1}{R_s} + g_m \right]$$

$$\therefore \frac{V_o}{I_o} = \frac{V_o}{V_o \left(\frac{1}{r_d} + \frac{1}{R_s} + g_m \right)} = \frac{1}{\frac{1}{r_d} + g_m + \frac{1}{R_s}}$$

$$\Rightarrow Z_o = \frac{1}{\frac{1}{r_d} + \frac{1}{R_s} + g_m}$$

$$\Rightarrow Z_o = r_d || R_s || \frac{1}{g_m}$$

if $r_d \gg 10 R_s$ then, $Z_o = R_s || \frac{1}{g_m}$

$$Z_o = \frac{1}{g_m + \frac{1}{R_s}} = \frac{R_s}{1 + g_m R_s}$$

Voltage gain (A_v) :-

$$V_{in} = V_{GS} + V_{R_s} \Rightarrow V_{in} = V_{GS} + V_o$$

or, $V_o = V_{in} - V_{GS} \Rightarrow V_{GS} = V_{in} - V_o$

But, $V_o = (g_m V_{GS}) (r_d || R_s) = g_m (V_{in} - V_o) (r_d || R_s)$

or, $V_o [1 + g_m (r_d || R_s)] = g_m V_{in} (r_d || R_s) \Rightarrow \frac{V_o}{V_{in}} = \frac{g_m (r_d || R_s)}{1 + g_m (r_d || R_s)}$

$$\Rightarrow A_v = \frac{g_m (r_d || R_s)}{1 + g_m (r_d || R_s)} \Rightarrow A_v = \frac{g_m R_s}{1 + g_m R_s} \text{ if } r_d \gg 10 R_s$$