

Measurement of Resistance

(46)

The resistance is classified only for the purpose of measurements

(i) Low resistance ($< 1 \Omega$), armature wdg resi, series field wdg, ^{Compensal} wdg resi


(ii) Medium resistance ($1 - 100 k\Omega$) (or) ($1 - 0.1 M\Omega$)

(iii) High resistance ($> 100 k\Omega$)

→ ammeter shunt resistance, diode forward bias resistance, link resistance (Lead n).
slide wire resistance.

→ shunt field wdg resistance, resistance of heating elements (heaters)
all electrical appliance equipment resistors in domestic purposes.
(daily life).

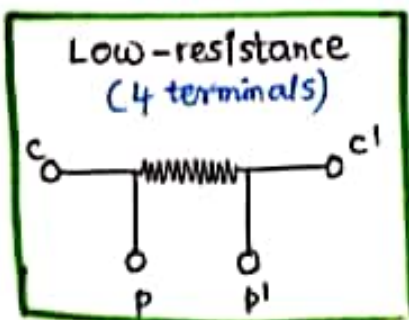→ insulation resistance of underground cable, insulators (power system).
insulation resistance of dielectrics, power diode - reverse bias resistance.
Series multiplier resistance of voltmeter, input resistance of CRO.
Op-amp, FETs ... etc.



CC' - current terminals



PP' - voltage/potential "

$$R = \frac{V_{PP'}}{I_{CC'}}$$

4 probe method.

Errors :- (Difficult)

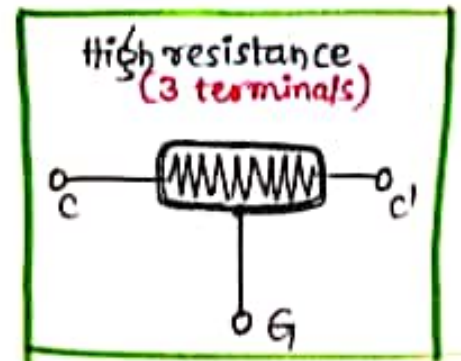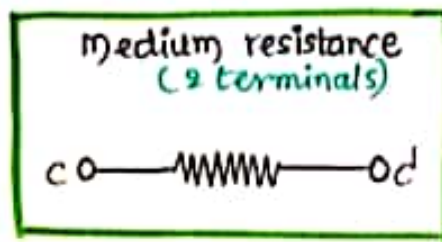1. Due to contacts
2. Due to leads
3. Due temperature change
4. Due to thermal emf



G (Guard terminal).

Difficulties faced in measurement of highresi
(or) Errors :-

1. Error due to leakage currents (these can be avoided by using guard wire)
2. Error due to Specimen capacitance.
3. i.e. Error due to electro-static field effect

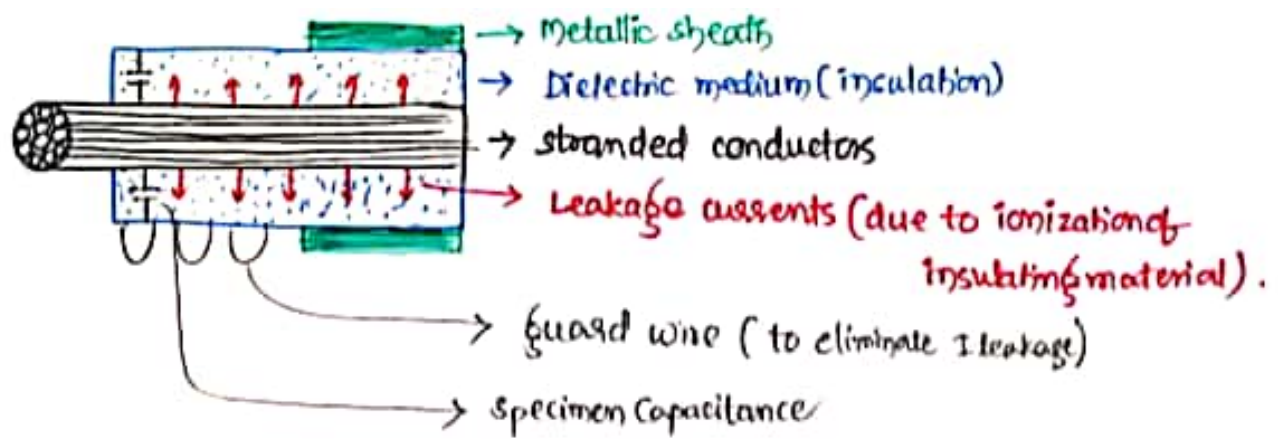


Fig: Underground power cable cross-sectional view
pertaining to difficulties of high resistance measurement.

Low resistance can be measured by

- (i) $\text{A}-\text{V}$ method
- (ii) Potentiometer
- (iii) Kelvin double bridge $\rightarrow$ most accurate ($R \Rightarrow 0.1 \mu\Omega$ to 1Ω).
- ✓(iv) All above..

Measurements can be measured by (medium)


- (i) $\text{V}-\text{A}$ method
- (ii) Substitution method
- (iii) Ohmmeter $\begin{cases} \rightarrow \text{Series type.} \\ \rightarrow \text{Shunt type.} \end{cases}$
- (iv) Wheatstone Bridge. $\rightarrow$ accurate more

High-resistance measured by

- (i) Loss of charge
- (ii) Direct deflection method
- (iii) Megger device
- (iv) Mega-ohm Bridge method $\rightarrow$ most accurate.

Voltmeter-Ammeter Method :-

(47)

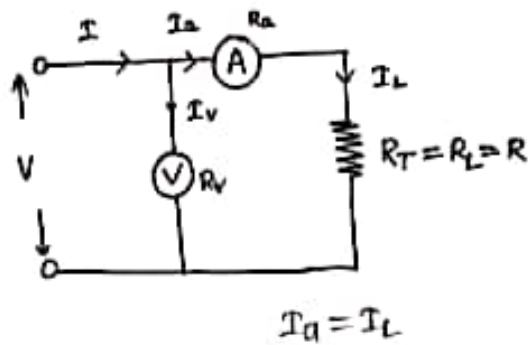

$$R_{\text{measured}} = R_m = \frac{V}{I_a} = \frac{V_{\text{supply}}}{I_a}$$

$$= \frac{I_a R_a + I_L R_L}{I_a}$$

$$R_m = (R_a + R_L)$$

$$R_m = R_T + R_a$$

$$\text{Error} = (A_m - A_T) = R_m - R_T = R_a$$

$$\therefore \text{Error} = +ve ; \Rightarrow (\text{measured}) > (\text{true value}) \therefore R_m > R_T$$


$$\% \text{ Error} = \frac{R_m - R_T}{R_T} \times 100 = \frac{R_a}{R_T} \times 100$$

Ideally $\Rightarrow$ If we try $(R_a \rightarrow 0 \Omega)$

Note :- voltmeter-ammeter is best suitable for measurement of large value of resistance in a medium resistance range.

The produced error is positive b/c of ammeter connected on load side. Ideally ammeter resistance is zero but practically it is never possible, it is only known as loading effect of ammeter.

Ammeter-voltmeter Method :-

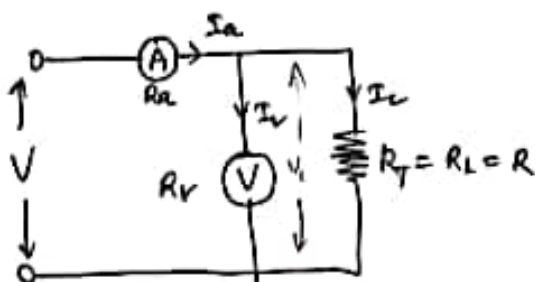

$$R_m = \frac{V}{I_a} = \frac{I_L R_L}{I_a} = \frac{V_L}{I_a}$$

$$= \frac{I_L R_L}{I_L + I_v} = \frac{V_L}{\frac{V_L}{R_L} + \frac{V_L}{R_v}}$$

$$R_m = \frac{R_L R_v}{R_L + R_v}$$

$$\frac{1}{R_m} = \frac{1}{R_L} + \frac{1}{R_v}$$

$$R_m = \frac{R_L R_V}{R_V \left(1 + \frac{R_L}{R_V}\right)} \Rightarrow R_m = \frac{R_L}{\left(1 + \frac{R_L}{R_V}\right)}$$

$$R_m = R_L \left(1 + \frac{R_L}{R_V}\right)^{-1}$$

$$R_m = R_L \left(1 - \frac{R_L}{R_V} + \left(\frac{R_L}{R_V}\right)^2 - \frac{R_L^3}{R_V^3} + \dots\right)$$

$$R_m \approx R_L \left(1 - \frac{R_L}{R_V}\right)$$

$$\therefore R_m = R_L - \frac{R_L^2}{R_V}$$

$$\text{Error} = R_m - R_T = -\frac{R_L^2}{R_V}$$

$$\text{Error} = -ve \Rightarrow (\text{measured}) < (\text{true value})$$

$$\therefore \% \text{ Error} = \frac{R_m - R_T}{R_T} \times 100 = -\frac{R_T}{R_V} \times 100. \quad (\because R_L = R_T = R)$$

ideally $R_V \Rightarrow \infty$ (error $\rightarrow 0$). never possible.

Note:- ① Ammeter-voltmeter method is best suitable for measurement of low resistances, the produced error is negative, error is because of voltmeter connected on load side. Ideally voltmeter resistance is ∞ , practically it is not possible it is only known as Loading Effect of voltmeter.

② To get same error in both the methods

$$\therefore \text{error}_{(A)-V} = \text{error}_{V-(A)}$$

$$\left| -\frac{R_L}{R_V} \right| = \left| +\frac{R_A}{R_L} \right|$$

$$\therefore R_L^2 = R_A R_V \Rightarrow$$

$$\boxed{R_L = \sqrt{R_A R_V}}$$