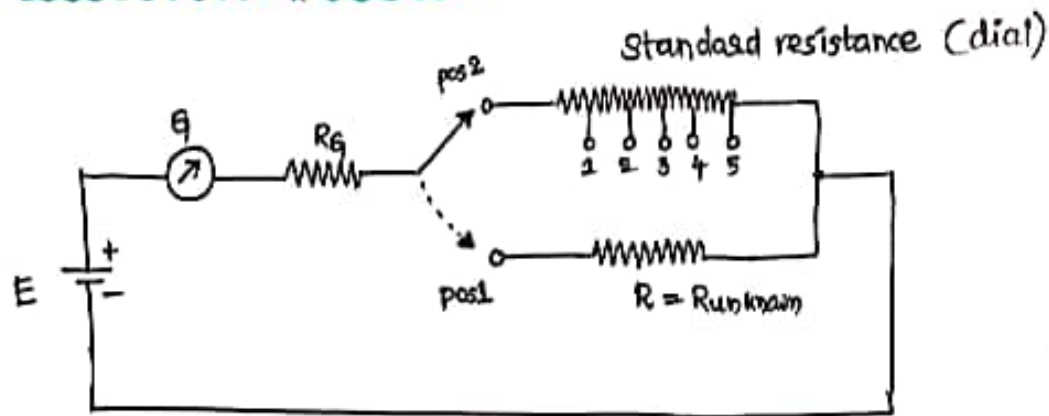


Substitution Method :-



case (i) :- Switch is moved to position '1'. $\Rightarrow I_G = I_1$

$$\therefore I_1 = \frac{E}{(R_G + R)} \quad \text{--- (1)}$$

case (ii) :- Switch is moved to position '2' $\Rightarrow I_G = I_2$

adjust the dial on standard resistance box...

ensure .. $I_2 = I_G = I_1$

$$\therefore I_2 = \frac{E}{(R_G + R_{\text{switch}})} = I_1 = \frac{E}{(R_G + R)} \quad \text{--- (2)}$$

$\therefore$ Unknown resistance (R) = R_{switch} (reading on dial resistance)

advantage :- One of the best method to measure resistance (practical)

disadvantages :- * Choice of availability of standard resistance box

* For long time measurement in laboratories, standard battery may be changed.



$\rightarrow$ Let $\theta_1 \rightarrow$ deflection of G with unknown resistance

$$\theta_1 \propto \frac{1}{(R_G + R)} \quad \rightarrow (3)$$


Let $\theta_2 \rightarrow$ deflection of G with standard resistance.

$$\frac{\theta_1}{\theta_2} = \frac{R_g + S}{R_g + R}$$

$$\therefore R = \frac{\theta_2}{\theta_1} (R_g + S) - R_g$$

$E = \text{constant (assumed)}$.

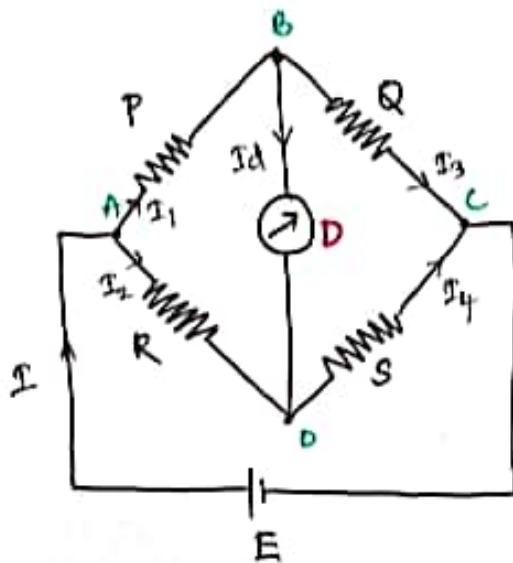Wheatstone Bridge :-
(Comparison method).



$P, Q, S \Rightarrow$ known resistances

$R \Rightarrow$ unknown resistance

$E \Rightarrow$ DC battery.

$P, Q, R, S \Rightarrow$ ratio arms resistance.

$\Rightarrow$ Diagonal galvanometer detector.

$$e = V_{BD} = V_{BA} + V_{AD}$$

$$= V_{AD} - V_{AB}$$

$$e = I_2 R - I_1 P$$

$$\Rightarrow I_1 P = I_2 R$$

$$\Rightarrow \frac{I_1}{I_2} = \frac{R}{P} \quad \text{--- (1)}$$

$$\text{(or)} \quad e = V_{BD} = V_{BC} + V_{CD} \\ = V_{DC} - V_{BC}$$

$$e = S I_4 - I_3 Q \Rightarrow \frac{I_4}{I_3} = \frac{Q}{S} \quad \text{--- (2)}$$

Under bridge balance condition; $e = 0$, $I_d = 0$.

$$\therefore I_1 = I_3 \quad \& \quad I_2 = I_4$$

$$\therefore \frac{I_1}{I_2} = \frac{I_3}{I_4} \Rightarrow \therefore \text{from (1) \& (2)}$$

$$\frac{P}{R} = \frac{S}{Q} \Rightarrow \boxed{\frac{P}{Q} = \frac{R}{S}}$$

$$\text{Detector sensitivity} = \text{voltage sensitivity} = \frac{\text{change in deflection}}{\text{change in voltage across detector}}$$

$$\therefore S_V = S_D = \frac{\Delta \theta}{\Delta V} = \frac{\Delta \theta}{e} \Rightarrow \Delta \theta = e S_V$$

$$\text{Bridge sensitivity} = \frac{(\text{change in deflection})}{(\text{unit change in resistance})} = \frac{\Delta \theta}{\left(\frac{\Delta R}{R}\right)} = S_B$$

$$\therefore \Delta \theta = S_B \left(\frac{\Delta R}{R} \right)$$

$$\therefore e S_V = S_B \left(\frac{\Delta R}{R} \right) \Rightarrow \boxed{S_B = \frac{R e S_V}{\Delta R}}^{**}$$

at unbalanced point ($R' = R + \Delta R$)

$$e = V_B = V_{oc} = V_{AD} - V_{AB} = V_B - V_D$$

$$\boxed{e = E \left(\frac{R'}{R+S} - \frac{P}{P+Q} \right)}^{**} \quad (or)$$

$$e = E \left(\frac{R'}{R'+S} - \frac{P}{P+Q} \right)$$

$$R' = R + \Delta R$$

$$e = E \left(\frac{(R + \Delta R)}{(R+S) + \Delta R} - \frac{P}{P+Q} \right)$$

$$e = E \left(\frac{R + \Delta R}{(R+S) + \Delta R} - \frac{R}{R+S} \right)$$

$$= E \left[\frac{(R + \Delta R)(R+S) - R[(R+S) + \Delta R]}{(R+S)^2 + \Delta R(R+S)} \right]$$

$$= E \left[\frac{\cancel{R^2} + RS + \cancel{\Delta R R} + \Delta R \cdot S - \cancel{SR} - \cancel{R^2} - \cancel{R \Delta R}}{(R+S)^2 + \Delta R(R+S)} \right] = \frac{E(\Delta R \cdot S)}{(R+S)^2 + \Delta R(R+S)}$$

at balance point

$$\frac{P}{Q} = \frac{R}{S}$$

$$\frac{Q}{P} = \frac{S}{R}$$

$$\frac{Q}{P} + 1 = \frac{S}{R} + 1$$

$$\frac{P+Q}{P} = \frac{R+S}{R}$$

$$e = \frac{S \cdot \Delta R \cdot E}{(R+S)^2 + \Delta R(R+S)}$$

$$(R+S)^2 \gg \Delta R(R+S)$$

$$\therefore e = \frac{S \cdot \Delta R \cdot E}{R^2 + S^2 + 2SR} = \frac{(\Delta R) E}{\frac{R}{RS} (R^2 + S^2 + 2RS)}$$

$$e = \frac{R \Delta R \cdot E}{R \left(\frac{R}{S} + \frac{S}{R} + 2 \right)}$$

$$\Delta V = e = \frac{\left(\frac{\Delta R}{R} \right) E}{\frac{R}{S} + 2 + \frac{S}{R}} \quad (\text{or}) \quad e = \frac{\left(\frac{\Delta R}{R} \right) E}{\frac{P}{Q} + 2 + \frac{Q}{P}}$$

$$S_V = \frac{\Delta \theta}{\Delta V} ; \Rightarrow S_V = \frac{\Delta \theta}{e} ; S_B = \frac{\Delta \theta}{\left(\frac{\Delta R}{R} \right)}$$

$$\therefore e S_V = \left(\frac{\Delta R}{R} \right) S_B$$

$$\frac{\left(\frac{\Delta R}{R} \right) E \cdot S_V}{\frac{P}{Q} + 2 + \frac{Q}{R}} = \left(\frac{\Delta R}{R} \right) S_B$$

$$\therefore S_B = \frac{e S_V}{\left(\frac{\Delta R}{R} \right)} = \frac{E \cdot S_V}{\frac{P}{Q} + 2 + \frac{Q}{R}}$$

$$S_{B \max} ; \text{ if } \frac{P}{Q} = \frac{Q}{P} = 1 \quad \text{i.e. } R = S = P = Q$$

$$\therefore S_{\text{Bmax}} = \frac{S_V E}{4}$$

(50)

condition for obtaining max. bridge sensitivity, it is possible if the ratio of ratio arm resistances of ratio of arm (or) equal to unity. i.e. $P=Q=R=S$, the value is $\frac{E}{4}$ times that of detector sensitivity.

$$e = V_{th} = V_{oc} = \frac{E \left(\frac{\Delta R}{R} \right)}{\frac{P}{Q} + 2 + \frac{Q}{P}} = \frac{E \left(\frac{\Delta R}{R} \right)}{\frac{R}{S} + 2 + \frac{S}{R}} \quad (or)$$


$$\theta = E \left(\frac{R + \Delta R}{R + \Delta R + S} - \frac{P}{P + Q} \right)$$

$$R_{th} = S \parallel (R + \Delta R) + P \parallel Q$$


$$R_{th} = \frac{PQ}{P+Q} + \frac{S(R+\Delta R)}{R+S+\Delta R}$$

if $\Delta R = 0$
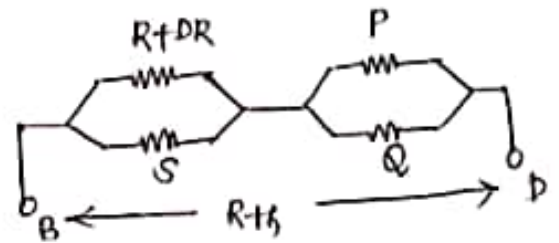
$$R_{th} = \frac{PQ}{(P+Q)} + \frac{RS}{(R+S)}$$



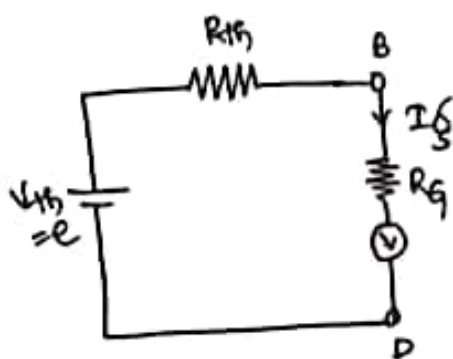Thevenin's equivalent ckt of Wheatstone Bridge



$$R_{th} = \frac{PQ}{(P+Q)} + \frac{RS}{(R+S)}$$

$$V_{th} = e = \frac{\left(\frac{\Delta R}{R} \right) E}{\frac{R}{S} + 2 + \frac{S}{R}}$$

$$I_{th} = I_g = \frac{V_{th}}{R_{th} + R_g}$$

For ideal (G) ; $R_g = 0$ $I_{th} = I_g = \frac{V_{th}}{R_{th}}$

→ If all arms are wheatstone Bridges of equal resistances Then

$$R = P = Q = S.$$


$$R_{th} = P \parallel Q + R \parallel S = R \parallel R + R \parallel R = \frac{R}{2} + \frac{R}{2} = R.$$

$$\therefore R_{th} = R, \quad V_{th} = V_{OC} = 0.$$

$$S_{B_{max}} = \frac{S_V E}{4}$$


→ $P = Q = S = R$; but one of the arm is under stress (strain).

case(i) :-

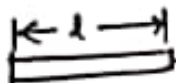 tensile force

length ↑ ; area ↓

but volume = constant.

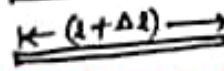 $\rightarrow (R + \Delta R)$

(compressive force)

 $\rightarrow (R - \Delta R)$

$$R_{th} = \frac{(R + \Delta R)S}{(R + S + \Delta R)} + \frac{PQ}{P + Q}$$

$$V_{th} = E \left(\frac{(R + \Delta R)A}{(R + R + \Delta R)} - \frac{R}{R + R} \right)$$


$$= \frac{(R + \Delta R)R}{(R + R + \Delta R)} + \frac{R \cdot R}{R + R}$$

$$= E \left(\frac{R^2 + R\Delta R}{2R + \Delta R} - \frac{1}{2} \right)$$

$$R_{th} = \frac{(R + \Delta R)R}{(2R + \Delta R)} + \frac{R}{2}$$

$$= E \left[\frac{2R^2 + 2R\Delta R - 2R - \Delta R}{2(2R + \Delta R)} \right]$$
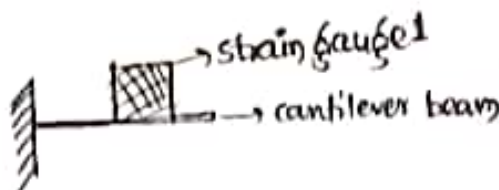
$$= E \frac{\Delta R}{2(2R + \Delta R)}$$



$$V_{th}' = E \left(\frac{\Delta R}{4R + 2\Delta R} \right)$$

$$4R \gg 2\Delta R.$$

$$\therefore V_{th} = \frac{E \Delta R}{4R}$$

(Quarter bridge) equation
 $R = P = Q = S$; one arm $(R + \Delta R)$.

$$\therefore V_{th} = \frac{E}{4} \left(\frac{\Delta R}{R} \right)$$

$$S_Q = \left(\frac{\Delta V}{\left(\frac{\Delta R}{R} \right)} \right) = \frac{V_{th}}{\frac{\Delta R}{R}} = \frac{E}{4}$$