
 
 


 ii) D-Latch and D-flip-flop:- D or Delay flop.

flop has one input and two output lines. When an inverter is connected betⁿ s and R input line of S-R flip-flop, thus obtained flip-flop is called D-flip flop. D-flip flop basically consist of two NAND gates.

The fig. as gives below shows the block diagram and logic ckt of D-flip-flop.



Truth table


CLK	D	Q_{n+1}	Action
0	0	Q_n	NC
0	1	Q_n	NC
1	0	0	Reset
1	1	1	Set

Present state - Next state table

Q_n	D	Q_{n+1}	Action
0	0	0	Reset
0	1	1	Set
1	0	0	Reset
1	1	1	Set

characteristic eqⁿ —

$$Q_{n+1} = D$$


 


Excitation table

Q_n	Q_{n+1}	Excitation 'D'
0	0	0
0	1	1
1	0	0
1	1	1

  iii) J-K latch and flip-flop :- J-K flip-flop is improved version of basic S-R flip-flop where the indeterminate output corresponding to $S=1, R=1$ has been overcome. J-K flip-flop has two inputs J and K and two outputs Q and $\bar{Q}$. A J-K flip-flop is implemented by connecting J and K inputs to two AND gates augmenting

two AND gates with inputs J, $\bar{Q}$ and KQ as to a basic S-R flip-flop as shown in fig. as below —



Block diagram.

Truth table —


J	K	S	R	Q_{n+1}	Action
0	0	0	0	Q_n	NC
0	1	0	Q_n	0	Reset
1	0	$\bar{Q}_n$	0	1	Set
1	1	$\bar{Q}_n$	Q_n	$\bar{Q}_n$	Toggle

Present state - Next state table.

Q_n	Input		Q_{n+1}	Action
	J	K		
0	0	0	0	NC
0	0	1	0	Reset
0	1	0	1	Set
0	1	1	1	Toggle
1	0	0	1	NC
1	0	1	0	Reset
1	1	0	1	Set
1	1	1	0	Toggle

characteristic eqⁿ —

$$Q_{n+1} = J\bar{Q}_n + \bar{K}Q_n$$

 

Excitation table

Q_n	Q_{n+1}	Excitation i/p	
		J	K
0	0	0	d(0,1)
0	1	1	d(0,1)
1	0	d(0,1)	1
1	1	d(0,1)	0

iv) T-Latch and flip-flop :- This is the flip-flop which has single input and two outputs which is obtained by using J-K flip-flop. When J and K inputs ~~are~~ lines are shorted, then such a ckt gives output either No-change or 'toggle' in corresponds to the inputs 0 or 1 respectively. Hence such type of flip-flop is called T-flip-flop or toggle flip-flop. A basic block diagram is shown in fig-1

 


Fig-1.

Truth table —

CLK	T	Q_{n+1}	Action
0	0	Q_n	
0	1	Q_n	
1	0	Q_n	NC
1	1	$\bar{Q}_n$	Toggle


Present state - Next state table

Q_n	T	Q_{n+1}	Action
0	0	0	NC
0	1	1	Toggle
1	0	1	NC
1	1	0	Toggle

characteristic eqⁿ

$$\therefore Q_{n+1} = Q_n \bar{T} + \bar{Q}_n T$$


$$Q_{n+1} = Q_n \oplus T$$

 

v> Master-slave flip-flop: - (Discussion About Race-around)

As we know that the operation of action of a latch is modified or controlled by applying an external clock pulse or triggering. There are two types of triggering
a> Edge triggering and b> Level triggering.


Before the development of edge triggering of flip-flop, there exist a problem in level triggering which is termed as Race-around condition. This can be understood in better way by following example. Let, us consider a J-K flip-flop is level triggered when $J=K=1$. Then in this case J-K execute "toggling", i.e. if previously $Q=0$, then $Q_{n+1}=1$ and if $Q_n=1$ then $Q_{n+1}=0$. But, there is a delay through NAND gate (propagation delay). Let a clock pulse of width t_p and period 'T' is given to J-K flip-flop to make flip-flop active

 

Let, ' Δt ' is propagation delay time

through gate, then after delay time Δt ,
 with $J=K=1$, output (Q) changes from 0 to 1.
 And, again after time Δt , output changes
 from 1 to 0. This back and forth
 change of output from 0 to 1 and 1 to 0
 takes place during ϕ clock-pulse width
 t_p . And, hence at the end of clock
 pulse, the value of Q is ambiguous.
 This situation is called race-around
 condition. To remove this, $t_p \leq \Delta t < T$.
 This condition has been removed by
 Master-slave flip-flop. [OR to avoid
 race around condⁿ, $2t_p < \Delta t < T \Rightarrow t_p < \frac{\Delta t}{2} < \frac{T}{2}$]

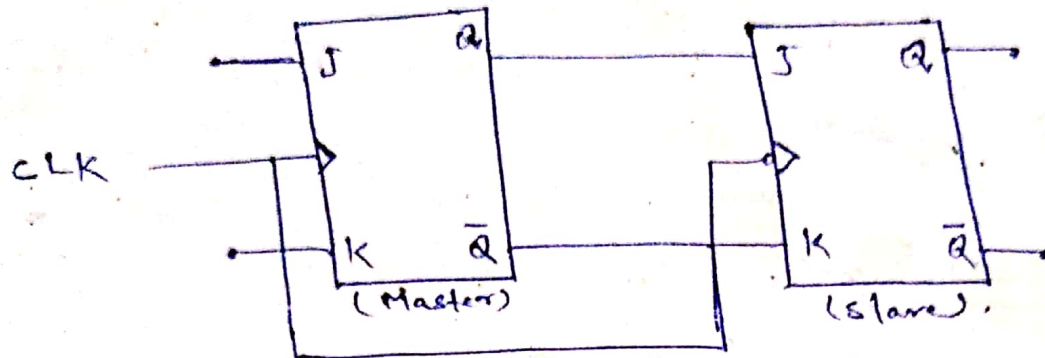Master-slave flip flop :- Master-slave flip flop is constructed by using two J-K flip-flops connected as shown in fig. as below —



Master-slave J-K flip-flop

The first flip-flop which is driven by applying +ve edge triggering, is called Master and the 2nd flip-flop driven by -ve edge triggering of clock pulse is called Slave. And hence entire arrangement is called Master-slave flip-flop.

When clock pulse has +ve edge, the Master operates or acts according to the J and K inputs but at that very time slave does not respond. Again, when clock pulse has -ve edge, Master flip-flop does not respond but Slave acts in accordance to Master previous outputs Q and $\bar{Q}$ which are inputs for slave.

A logic ckt diagram using NAND gates of Master-slave flip-flop is shown in fig. as below —

