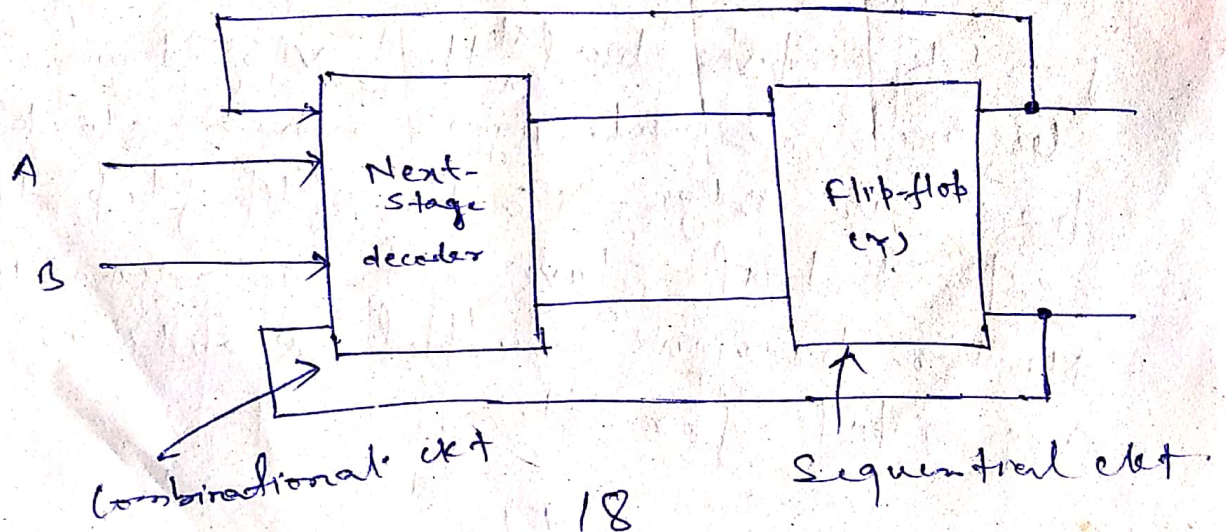


Realisation of one flip-flop Using another flip-flop

It is possible to implement a flip-flop using another flip-flop. A basic block diagram for such a realisation is shown in fig. a below —



Working Rule for implementation:-

- i> Find present-state next state table of the flip-flop (X) that is to be realized or implemented.
- ii> Find excitation table of given flip-flop (Y)
- iii> Using K-map simplify the logic expression for excitation table.

Realization of D-flip-flop Using S-R flip-flop.

Step:- I PS-NS table for D-flip-flop.



Q_n	D	Q_{n+1}
0	0	0
0	1	1
1	0	0
1	1	1

$\boxed{Q_{n+1} = D}$ ← characteristic equation.


Step-II: Excitation table on the basis of PS-NS table of D-flip-flop —

Q_n	D	Q_{n+1}	Excitation table	
			S	R
0	0	0	0	1(0,0)
0	1	1	1	0
1	0	0	0	1
1	1	1	1(0,1)	0

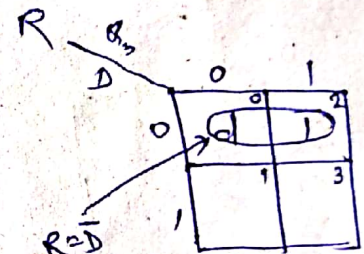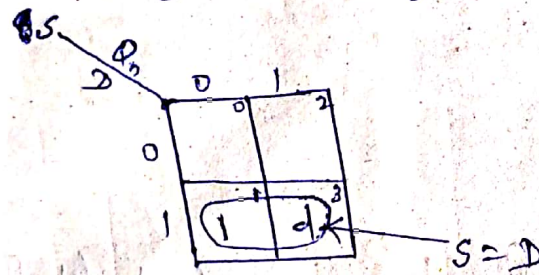Step-III K-map simplification for S-input —



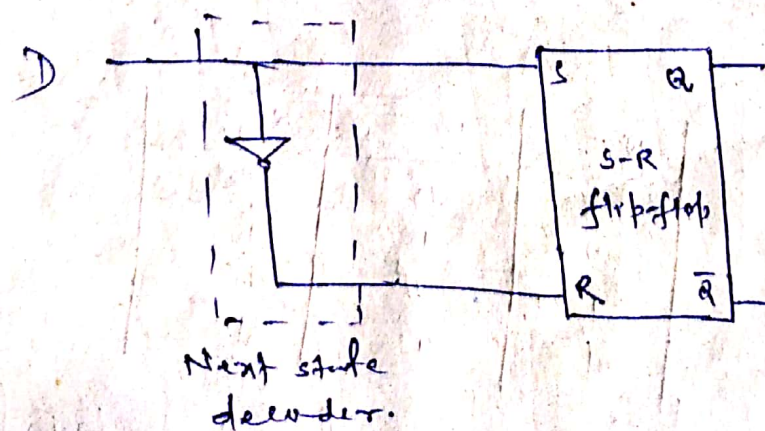From above K-map simplification, we can realize D-flip-flop by S-R flip-flop as below —



Realisation of J-K flip-flop by using S-R flip-flop.

Step:- I.

PS-NS table of J-K flip-flop.


Q_n	J	K	Q_{n+1}	Action
0	0	0	0	NC
0	0	1	0	Reset
0	1	0	1	Set
0	1	1	1	Toggle
1	0	0	1	NC
1	0	1	0	Reset
1	1	0	1	Set
1	1	1	0	Toggle

Step - II.


Excitation table of S-R flip-flop corresponding to PS-NS of J-K flip-flop.

Q_n	J	K	Q_{n+1}	Excitation inputs	
				S	R
0	0	0	0	0	d(0,1)
0	0	1	0	0	d(0,1)
0	1	0	1	1	0
0	1	1	1	1	0
1	0	0	1	d(0,1)	0
1	0	1	0	0	1
1	1	0	1	d(0,1)	0
1	1	1	0	0	1

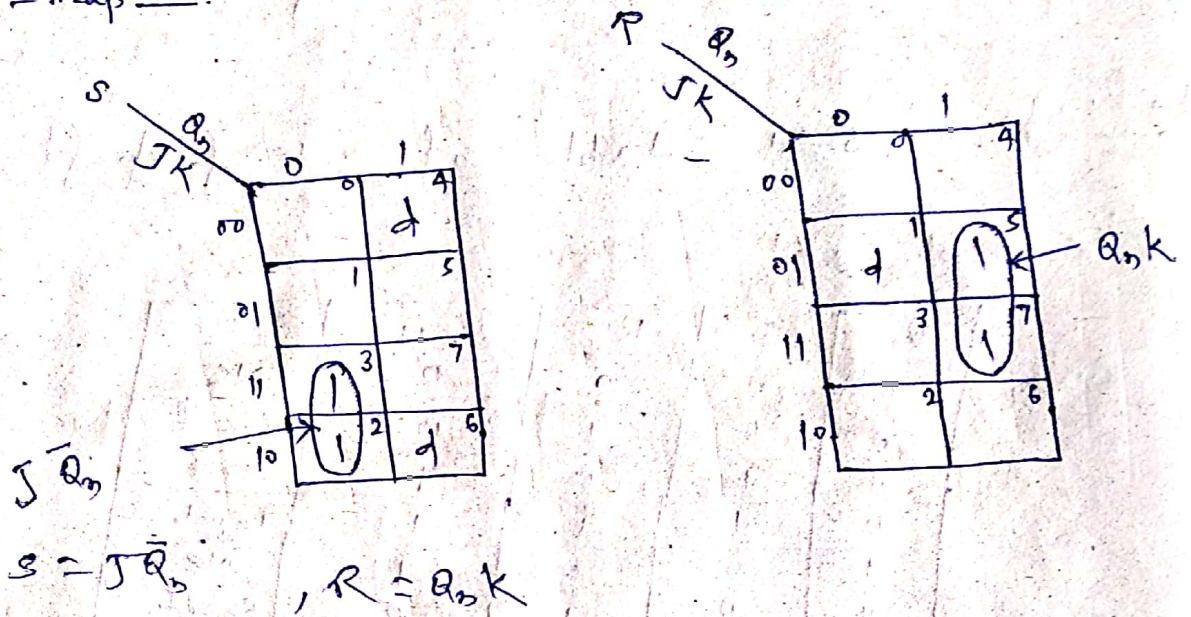Step-III. Simplification of boolean expression by using K-map —



Implementation —

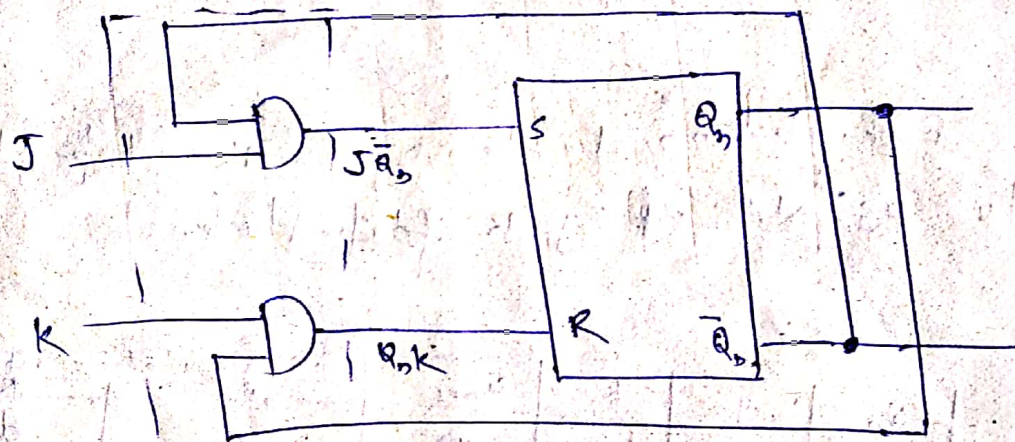

Next state decoder.

Realisation T-flip-flop by using S-R flip-flop

Step-I PS-NS of T-flip-flop

Q_n	T	Q_{n+1}
0	0	0
0	1	1
1	0	1
1	1	0

Step-II Excitation table of S-R corresponding to PS-NS table of T-flip-flop.

Q_n	T	Q_{n+1}	Excitation input	
			S	R
0	0	0	0	$d(0,0)$
0	1	1	1	0
1	0	1	$d(0,1)$	0
1	1	0	0	1

Step-III Simplification by K-map

S

Q_n	0	1
T	0	1
0	0	d
1	1	3

①


R

Q_n	0	1
T	0	1
0	d	0
1	1	③

③

$R = Q_n T$

$S = \bar{Q}_n T$

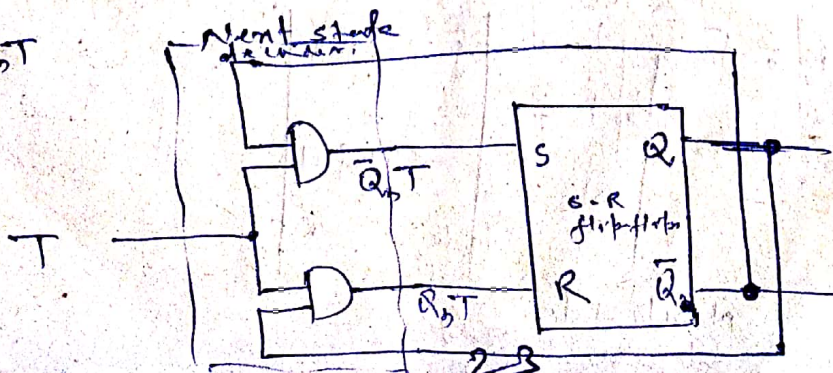

Realisation of D-flip-flop using J-K flip-flop




Step-I. PS-NS of D-flip-flop —

Q_n	D	Q_{n+1}
0	0	0
0	1	1
1	0	0
1	1	1

Step-II. Excitation table —

Q_n	D	Q_{n+1}	Excitation int	
			J	K
0	0	0	0	$d(0,0)$
0	1	1	1	$d(0,1)$
1	0	0	$d(1,0)$	1
1	1	1	$d(1,1)$	0

Step-III Simplification —

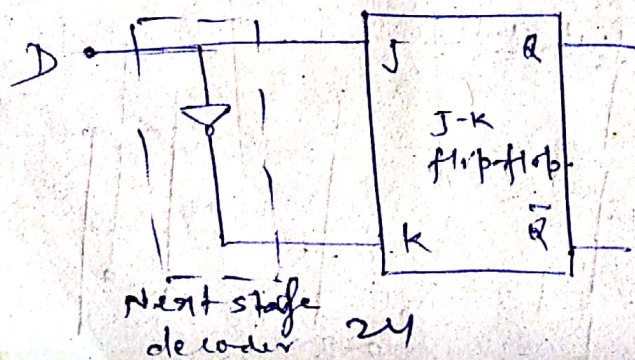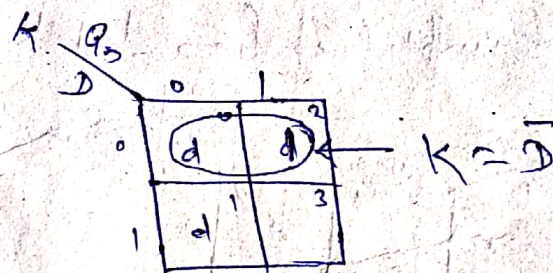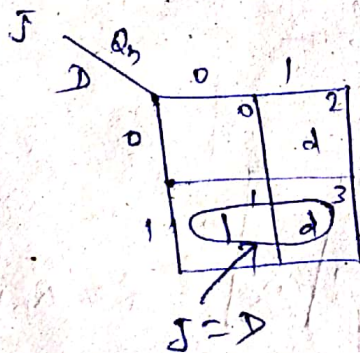

Realisation of J-K flip-flop by using D-flip-flop.


Step-I:

PS-NS of J-K flip-flop —


Q_n	J	K	Q_{n+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Step-II: Excitation table for D-flip-flop.

Q_n	J	K	Q_{n+1}	Excitation Int. D
0	0	0	0	0
0	0	1	0	0
0	1	0	1	1
0	1	1	1	1
1	0	0	1	1
1	0	1	0	0
1	1	0	1	1
1	1	1	0	0

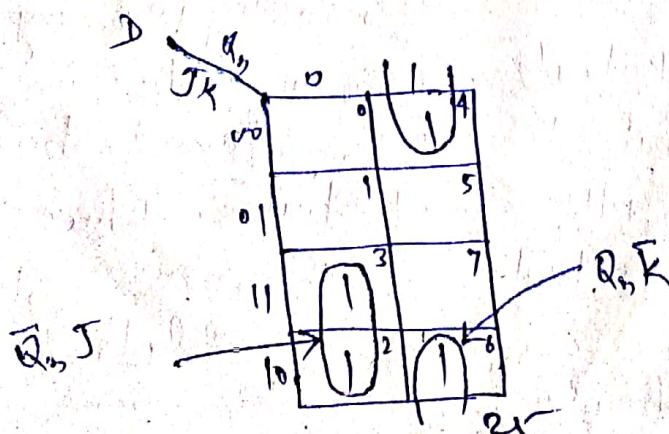

$$D = J\bar{Q}_n + Q_n\bar{K}$$

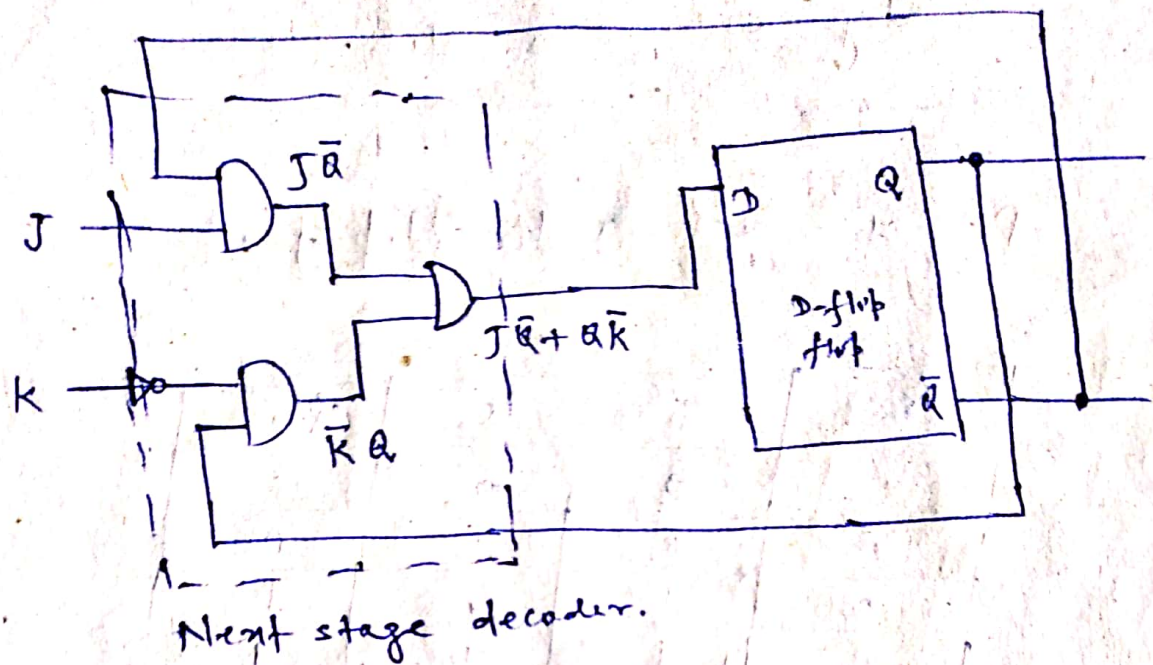

Application of flip-flops.

- i> Used as basic unit of memory element
- ii> Parallel data storage
- iii> Used for frequency division.
- iv> Used to construct counter and Register