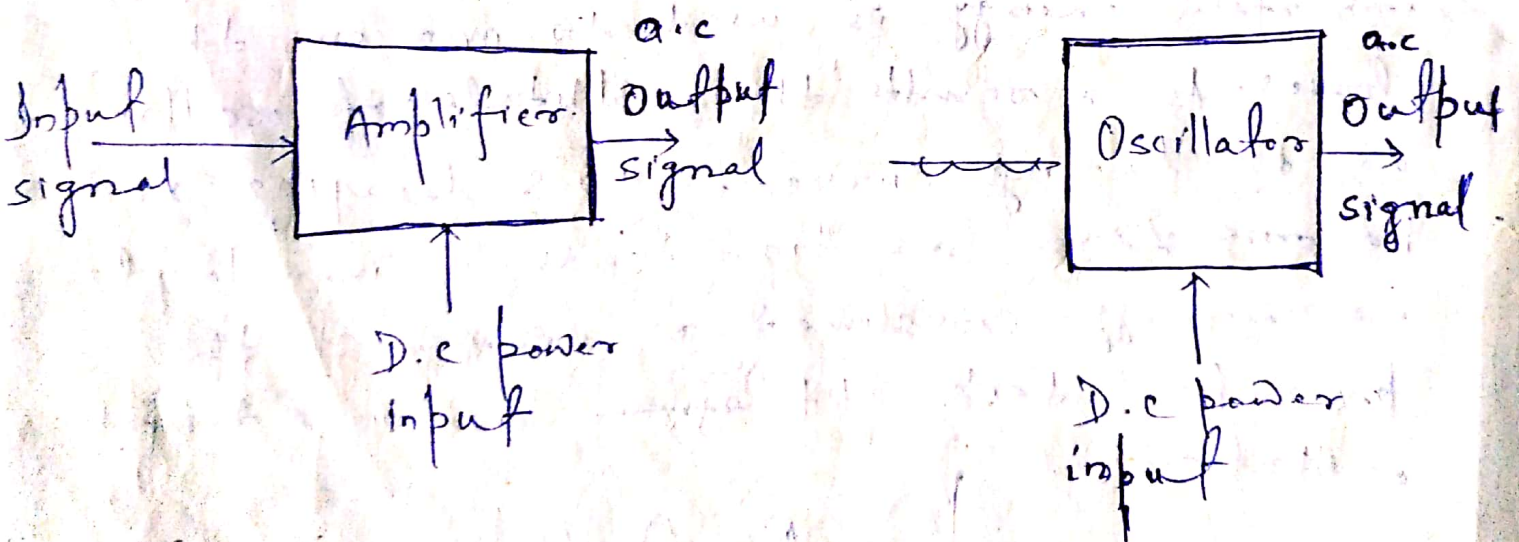



Oscillators

An electronic device which generates alternating signal ^{of desired} frequency is the device which converts the d.c input power in a.c output power without requiring any external input signal is called the Oscillator. Thus, an oscillator functions in opposite to the rectifier. The figure given below shows the block diagram of amplifier and oscillator —




The oscillatory ckt (OR tank ckt).

A circuit which provides the electrical oscillation of any desired frequency is known as oscillatory ckt or tank ckt. A tank ckt consists of parallel combination of a capacitor and inductor. The frequency produced by tank ckt is determined by the value of L and C . It should be remembered that the capacitor stores the energy in electric field in the form of electrostatic charge ($W_c = \frac{1}{2} CV^2$) whereas the inductor stores the energy in the magnetic field associated with inductor whenever current flowing through it. The fig. given below shows a tank circuit —

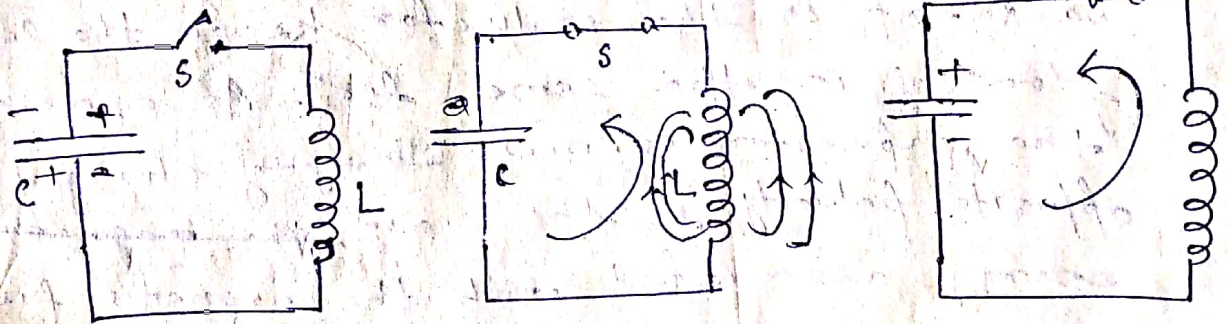


i) Let, Capacitor is fully charged from an external d.c. source. Here, the switch S is open, hence, capacitor does not discharge and corresponding to it no current flows through the ckt.

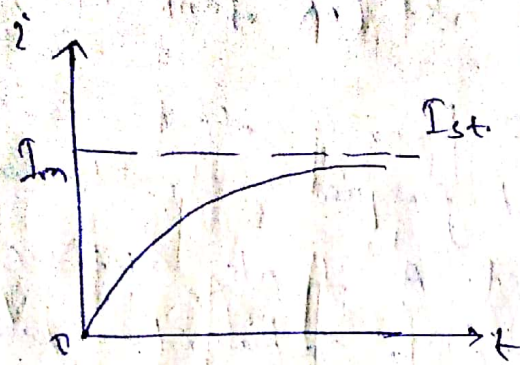ii) Now, S is closed. As soon as S is made close, capacitor starts discharging through the inductor L . We know that inductor has a property due to which it opposes any change either in direction or magnitude of current flowing through itself. Hence the current through the ckt builds up slowly ~~the~~ and max^m current



Discharging profile of RC-ckt.

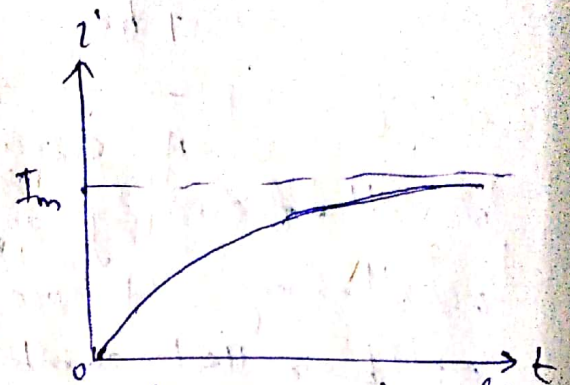

charging profile of LR ckt.

flows through the ckt when capacitor fully discharged. Thus, the electrostatic energy stored in capacitor ($W_C = \frac{1}{2} CV^2$) has been converted (or transferred) into the magnetic field energy stored in inductor ($W_L = \frac{1}{2} Li^2$).


iii) When, the capacitor is completely discharged, the magnetic field begins to collapse. The back emf in the inductor keeps the current flowing in the same dirⁿ. As a result, the capacitor is now ~~charging~~ charged with opposite polarity. In this case, ~~the magnetic~~ energy associated with the magnetic field is now again converted into electrostatic energy. If, there is no dissipative resistance, the capacitor charge to the value of its initial condition.

And, again, when capacitor is completely charge and total energy in magnetic field associated with inductor is converted into electrostatic energy then capacitor again starts discharging in opposite dirⁿ with respect to previous dirⁿ.

The sequence of charging and discharging continues i.e. interchanging of energy betⁿ L and C is repeated again and again. The situation is similar to the phenomena of oscillating phenomena where the energy keeps on interchanging from potⁿ energy to kinetic energy and kinetic energy to potⁿ energy. So, the charging and discharging of capacitor through the inductor results in oscillating current and hence oscillations are set up ~~whose~~ in LC ckt whose frequency is given by:

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$

If there were no losses in tank ckt, then interchanging of energy ~~from~~ betⁿ L and C would continue indefinitely. But, we know that a practical inductor offers some resistance and dielectric medium of capacitor has some leakage, so ^{small part of} the original ~~energy~~ imported energy is used to overcome this losses. As a result, the amplitude of oscillation or oscillating current goes decaying and become zero as time tends to infinitely large or energy consumed as losses. So the practical tank ckt ~~affers~~ produces damped oscillation.

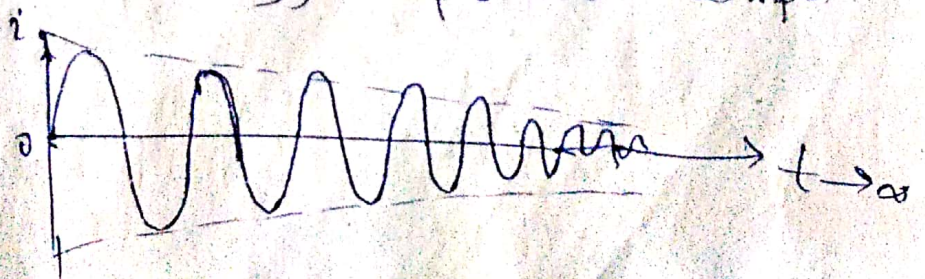

Difference betⁿ amplifier and oscillator

Amplifier

i> In an amplifier, the d.c. power supplied is converted into a.c. output power at the input signal frequency.

ii> In amplifier, the frequency, amplitude and waveform of output signal is controlled with input signal.

Oscillator

i> While, in an oscillator d.c. power is converted in a.c. power without requiring any input signal.

ii> While, the frequency, amplitude and waveform is controlled circuit-itself. And frequency of generated power output is determined by passive elements used in ckt.

Difference betⁿ alternator and Oscillator.

Oscillator

i> An oscillator is an electronic device and it has no any rotating part.

ii> It converts the d.c. energy into a.c. energy and freq. of output signal is determined by passive element of ckt.

iii> Oscillator produces the output a.c. signal at very high freq (of MHz or GHz)

Alternator

i> While, An alternator is a mechanical device as it has rotating parts.

ii> While, it converts the mechanical energy into electrical energy.

iii> While alternator produces a.c. voltage at low frequency usually 50 Hz.

iv) The operation of Oscillator is silent as it has no rotating part.

v) There is no wear and tear losses

iv) The operation of alternator is noisy as it has rotating part.

v) There exist some wear and tear losses.

Advantages of Oscillator over the alternator

There are following advantages of Oscillator over the alternator —

- i) Portable and cheap.
- ii) Since Oscillator has no any rotating part, hence there is no wear and tear loss.
- iii) The operation of oscillator is silent.
- iv) The frequency of oscillation may be varied conveniently.
- v) The voltage or current of any frequency is adjustable over wide range can be generated.
- vi) The frequency once set remains constant for a considerable period of time.
- vii) High operation frequency due to the absence of moving part.

Operation of Oscillator

The operation of Oscillator can be understood with the help of the feedback ckt as shown in fig.

Let,

A = Gain of basic amplifier

$A\beta$ = Close loop gain

β = Feedback factor

V_{in} = Input signal.

Since

$$V_o = A V_{in}$$

Let, V_f is feedback voltage to the input then,

$$V_f = \beta V_o = A\beta V_{in}$$




Let,




(a-b) is connected after feedback and the input is disconnected from the terminals simultaneously.

Case-I If, $A\beta < 1$ then $A\beta V_{in} < V_{in}$.

i.e. now the output $A\beta V_{in}$ is less than V_{in} and output signal die-out, as shown in

fig - (a)

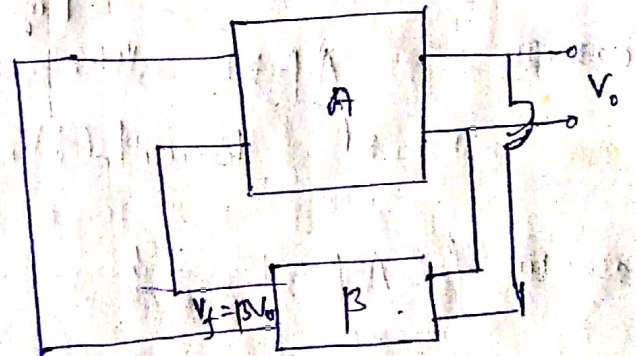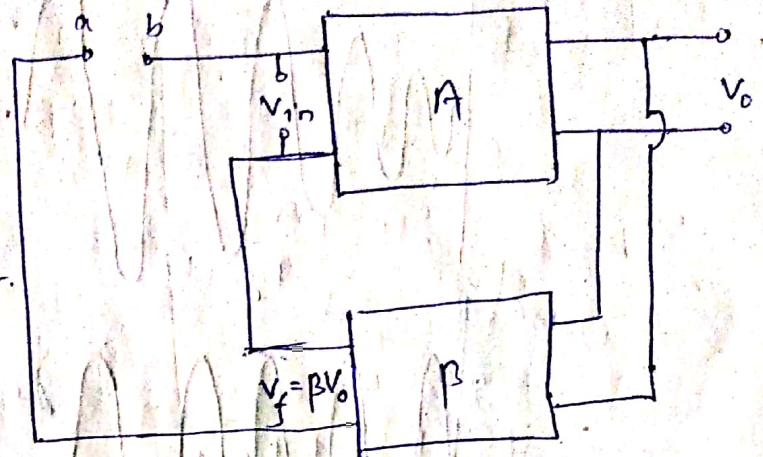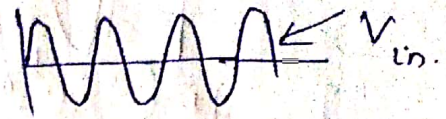

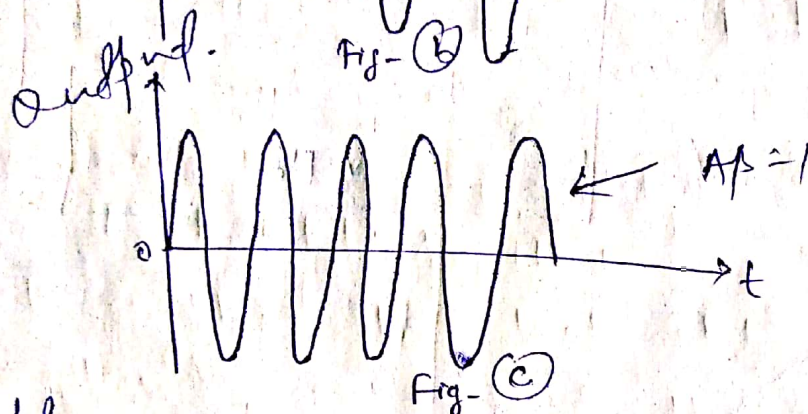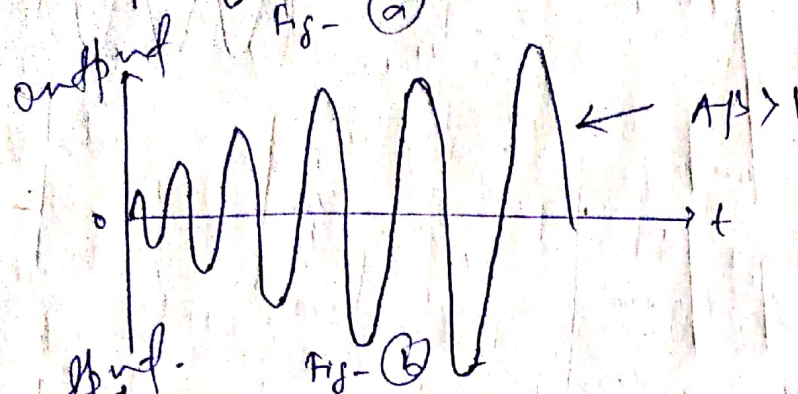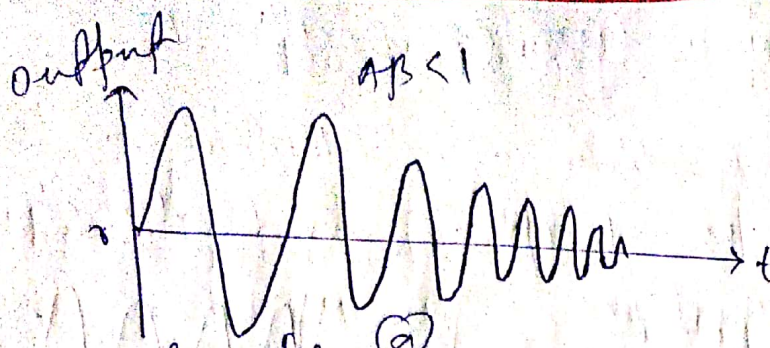

Case-II. If, $AB > 1$ then $ABV_{in} > V_{in}$ i.e. output signal builds up. as shown in fig (b)

Case-III If $AB = 1$ then $ABV_{in} = V_{in}$ i.e. frequency output signal is a steady sine wave and frequency of oscillation sustains. " $AB = 1$ " is called Barkhausen criterion.

Hence, certain condition must be ~~fulfill~~ fulfilled of frequency sustains. These conditions are —

i) The loop gain of ckt i.e. AB must be equal (or slightly greater) to unity

ii) The phase shift around the ckt must be ~~zero~~ ^{Barkhausen crit}. These two cond^s are called ~~BRANK~~ ^{criteria}.

There are two types of oscillators on the basis of nature of wave shape of generated signal —

i) Harmonic Oscillator :- An oscillator that generates a sinusoidal waveshape or near to sinusoidal waveshape of finite freq. is called Harmonic oscillator.

ii) Relaxation oscillator :- The oscillator that does not generate sinusoidal but square wave, triangular wave or saw-tooth wave etc, is called Relaxation oscillator. Schmitt trigger is an example of Relaxation oscillator.

Difference betⁿ Harmonic and Relaxation oscillator —

Harmonic osc.

i) Generated waveshape are sinusoidal of finite freq.

ii) Energy flow is always in one dirⁿ from active to passive components.

iii) Frequency of oscillation is determined by feedback path.

Relaxation osc.

i) Generated waveshape are non-sinusoidal but square, triangular, saw-tooth etc.

ii) While, energy is exchanged betⁿ active and passive components.

iii) Here frequency of oscillation is determined by basically charging and discharging time i.e. by time constant during energy exchange.