

PHASE SHIFT OSCILLATOR

Phase-shift oscillator or RC phase-shift oscillator is suitable to generate audio frequencies. Fig-1 shows a basic ckt of transistorised phase-shift oscillator. When a sinusoidal voltage of frequency f is applied to a circuit consisting of R and C , in series then alternating current in the circuit leads the applied voltage by certain angle known as phase-angle. The value of R and C may be selected in such a way that for the frequency f , the phase angle is 60° . So, using a ladder network of three R - C section (as shown in fig-1), we are able to produce 180° phase shift.

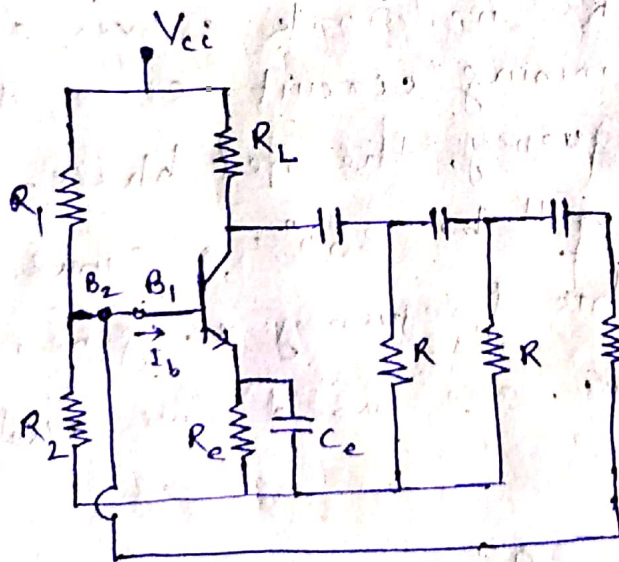


Fig-1(a)

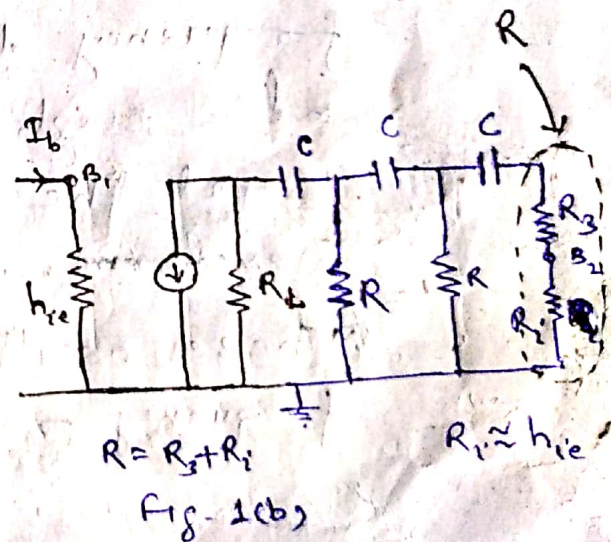


Fig-1(b)

Circuit arrangement :

Ckt shown in fig-1(a) consist of NPN transistor in CE configuration. R_1 , R_2 and R_E , C_E provides biasing and temperature stability. The output of amplifier goes to a feedback network which consist ~~a resistance~~

of three RC sections. It should be noted that the last section contain a resistance $R_3 = R - h_{ie}$ because this resistor is connected with the base of transistor, the input resistance h_{ie} of transistor is added to it to give total resistance R .

Circuit action :-

Here the three RC-ladder circuit produces a phase shift of 180° between input and output voltages. Since CE amplifier produces a phase-shift of 180° due to transistor action, the total phase shift becomes 360° (or 0°), which is the essential requirement of sustained oscillation. The RC network serves as frequency determining circuit, since, only at a single frequency, the net phase-shift around the loop will be 360° , a sinusoidal waveform at this frequency is generated. These oscillators are used for audio frequency range.

Frequency of oscillation :- There are following assumptions —

- i) $1/h_{oe}$ is much larger than R_L ,
- ii) h_{oe} is very small and $h_{oe} R_L$ can be neglected
- iii) In practice, R_L is taken equal to R
i.e. $R_L \approx R$

Now, the equivalent ckt (in - h-parameter) of fig-1(a), which is drawn in fig-1(b), can be redrawn for mathematical analysis as shown in fig-2(a), (b)

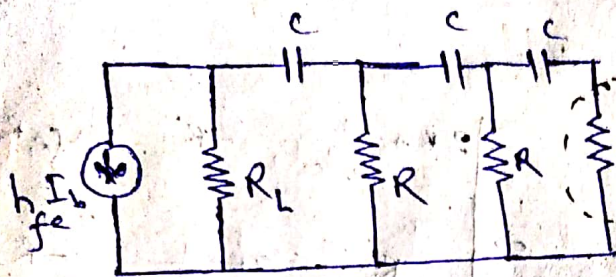


Fig-2(a)

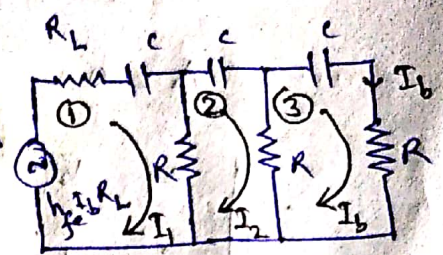


Fig-2(b)

Let, $R_L = R$,

Apply KVL in loop-① in fig-2(b)

$$h_{fe} I_b R + I_1 \left(R + \frac{1}{j\omega C} \right) + (I_1 - I_2) R = 0$$

$$\text{or, } \left(2R + \frac{1}{j\omega C} \right) I_1 - R I_2 + h_{fe} R I_b = 0 \quad \text{--- ①}$$

Again, Apply KVL in loop-②

$$(I_2 - I_b) R + (I_2 - I_1) R + I_2 \left(\frac{1}{j\omega C} \right) = 0$$

$$\text{or, } I_2 R - I_b R + I_2 R - I_1 R + I_2 \left(\frac{1}{j\omega C} \right) = 0$$

$$\text{or, } -R I_1 + \left(2R + \frac{1}{j\omega C} \right) I_2 - R I_b = 0 \quad \text{--- ②}$$

Similarly, apply KVL in loop-③

$$I_b R + (I_b - I_2) R + I_b \left(\frac{1}{j\omega C} \right) = 0$$

$$\text{or, } 0 \cdot I_1 - R I_2 + \left(2R + \frac{1}{j\omega C} \right) I_b = 0 \quad \text{--- ③}$$

Here there are three knowns as I_1, I_2, I_3 for which we solve by using Cramer's rule. It is obvious from eqⁿ (i), (ii) & (iii), these equations are homogeneous,

$$\therefore \Delta = 0$$

$$\therefore \begin{vmatrix} a_1 & b_1 & c_1 \\ a_2 & b_2 & c_2 \\ a_3 & b_3 & c_3 \end{vmatrix} = 0 \Rightarrow \begin{vmatrix} 2R + \frac{1}{j\omega C} & -R & h_{fe}R \\ -R & 2R + \frac{1}{j\omega C} & -R \\ 0 & -R & 2R + \frac{1}{j\omega C} \end{vmatrix} = 0$$

$$\text{or } \begin{vmatrix} 2R - jX_c & -R & h_{fe}R \\ -R & 2R - jX_c & -R \\ 0 & -R & 2R - jX_c \end{vmatrix} = 0, \text{ where } X_c = \frac{1}{j\omega C}$$

$$\text{or, } (2R - jX_c)[(2R - jX_c)(2R - jX_c) - (-R)(-R)] - (-R)[(-R)(2R - jX_c) - 0] + h_{fe}R[(-R)(-R) - 0] = 0$$

$$\text{or, } (2R - jX_c)[3R^2 - j4RX_c - X_c^2] - R^2(2R - jX_c) + h_{fe}R^3 = 0$$

$$\text{or } 6R^3 - j8R^2X_c - 2RX_c^2 - 3jR^2X_c - 4RX_c^2 + jX_c^3 - 2R^3 + jR^2X_c + h_{fe}R^3 = 0$$

$$\text{or } 4R^3 + jX_c^3 - j10R^2X_c - 6RX_c^2 + h_{fe}R^3 = 0$$

Equating imaginary part to zero

$$X_c^3 - 10R^2X_c \quad \text{or } X_c^2 = 10R^2 \quad \text{or } X_c = \sqrt{10}R$$

$$\text{or } \frac{1}{\omega C} = \sqrt{10}R \quad \text{or } \omega C = \frac{1}{\sqrt{10}R} \Rightarrow \boxed{f = \frac{1}{2\sqrt{10}\pi RC}}$$

If $R_L \neq R$, then from above analysis, we can show that —

$$f = \frac{1}{2\pi C \sqrt{4RR_L + 6R^2}}$$

If $R_L \ll R$, then, $f = \frac{1}{2\sqrt{6}\pi CR}$
Now, equating real to zero, we get —

$$4R^3 - 6RX_c^2 + h_{fe}R^3 = 0$$

$\therefore X_c = 10R^2$, (from above discussion),

$$\therefore 4R^3 - 6R(10R^2) + h_{fe}R^3 = 0$$

$$\Rightarrow R^3(4 - 60 + h_{fe}) = 0 \Rightarrow \boxed{h_{fe} = 56}$$

Thus, for sustained oscillation, $h_{fe} = 56$.