

Comparator

Comparator :- An electronic device that accept input of linear voltages and provides digital output which indicates one input is less than or greater than the second, is called comparator. A comparator is basically Analog to Digital converter. An op-amp is used as comparator.

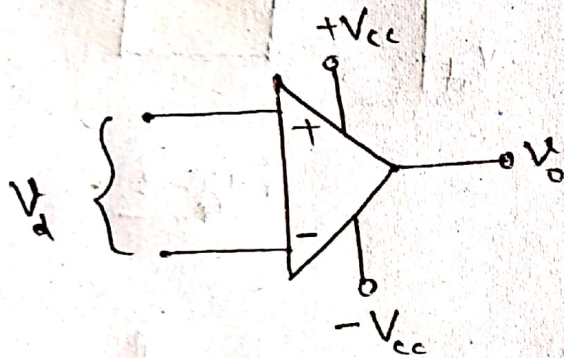


Fig-1(a)

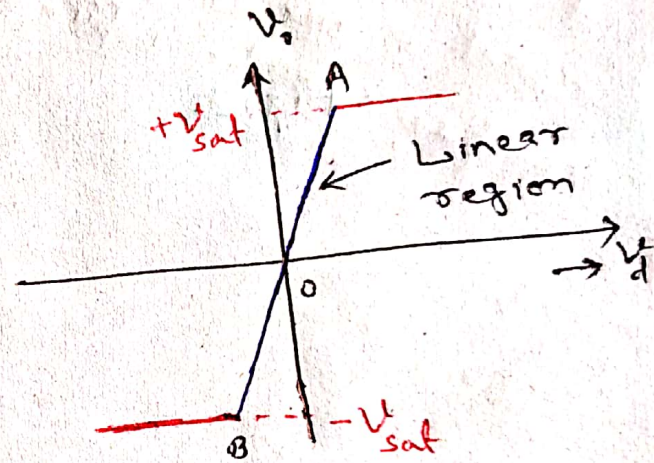


Fig-1(b) voltage transfer character.

Fig-1(b) shows, op-amp can operate in three mode depending on applied differential input voltage V_d

Three operating modes are —

- i) Positive saturation $+V_{sat}$
- ii) Negative " $-V_{sat}$
- iii) Linear region, $-V_{sat} \leq V_o \leq +V_{sat}$, (AB)

Let, us consider, a non-inverting op-amp, with open loop configuration shown in fig-2. The output voltage is saturated due to open-loop configuration and large (ideally infinitely large) voltage gain

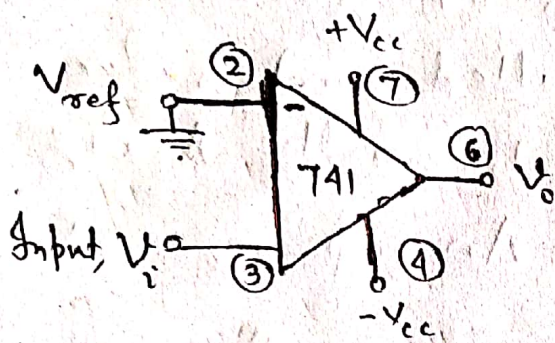


Fig-2.

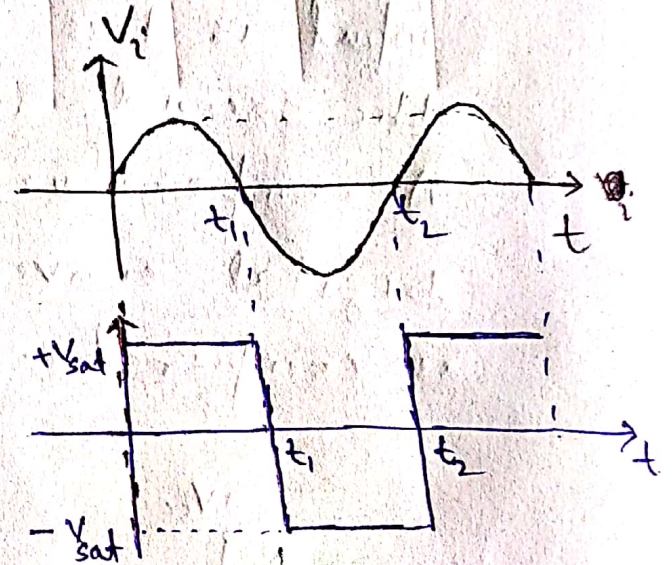


Fig-3.

From - fig-2 & 3, we see that, when a reference voltage given at pin no-2 is set to 0 volt, a sinusoidal signal applied to non-inverting input - pin-(3) will cause the output to switch between its two output states $+V_{sat}$ and $-V_{sat}$ as shown in fig-3. The applied input voltage V_i going, even a fraction of a mV above ~~over~~ 0-volt reference, level (given pin-(2)) will

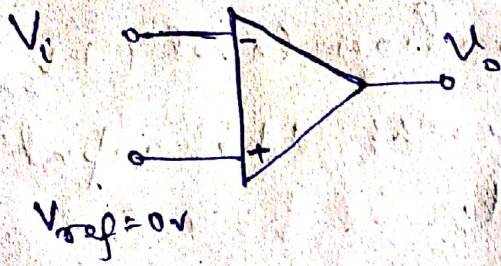


Fig-4

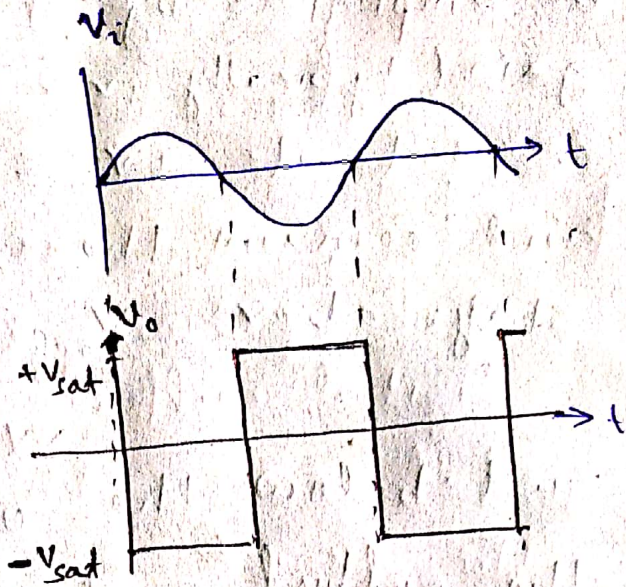


Fig-5

Here, input V_i is applied to inverting terminal, hence output signal is inverted in comparison to input signal.

IC-555 Timer

In op-amp ckt, and applications, we require a circuit which produces timing interval. The IC-555 timer is most versatile linear integrated circuit used for this purpose. IC-555 timer can be used in variety of applications as - mono-stable and astable multivibrators d.c to d.c converters.

IC-555 timer is available as 8-pin metal can, or a 14-pin DIP (Dual-In-Package) IC-556). 14-pin IC-556 consist of two IC-555 timer.

PIN diagram and internal config of IC-555 timer

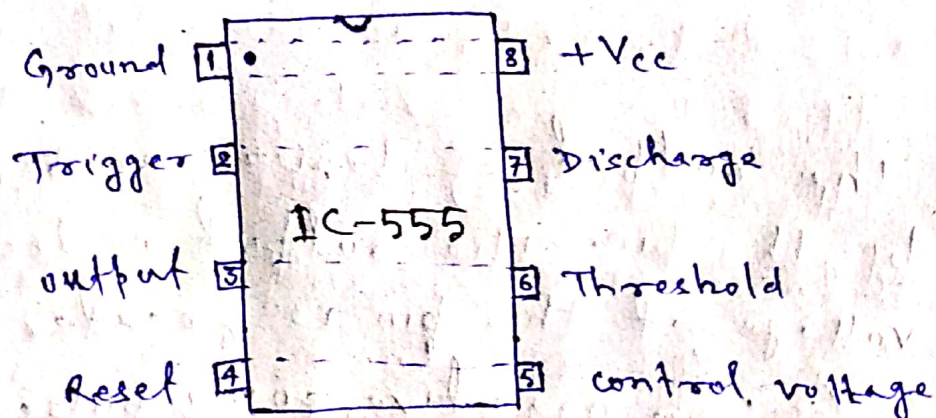


Fig-1.

Above fig-1. shows the various pins of IC-555 timer. Fig-2 shows internal structure.

Pin:-1. It is the chip ground and all voltages (ground) are measured with respect to this terminal.

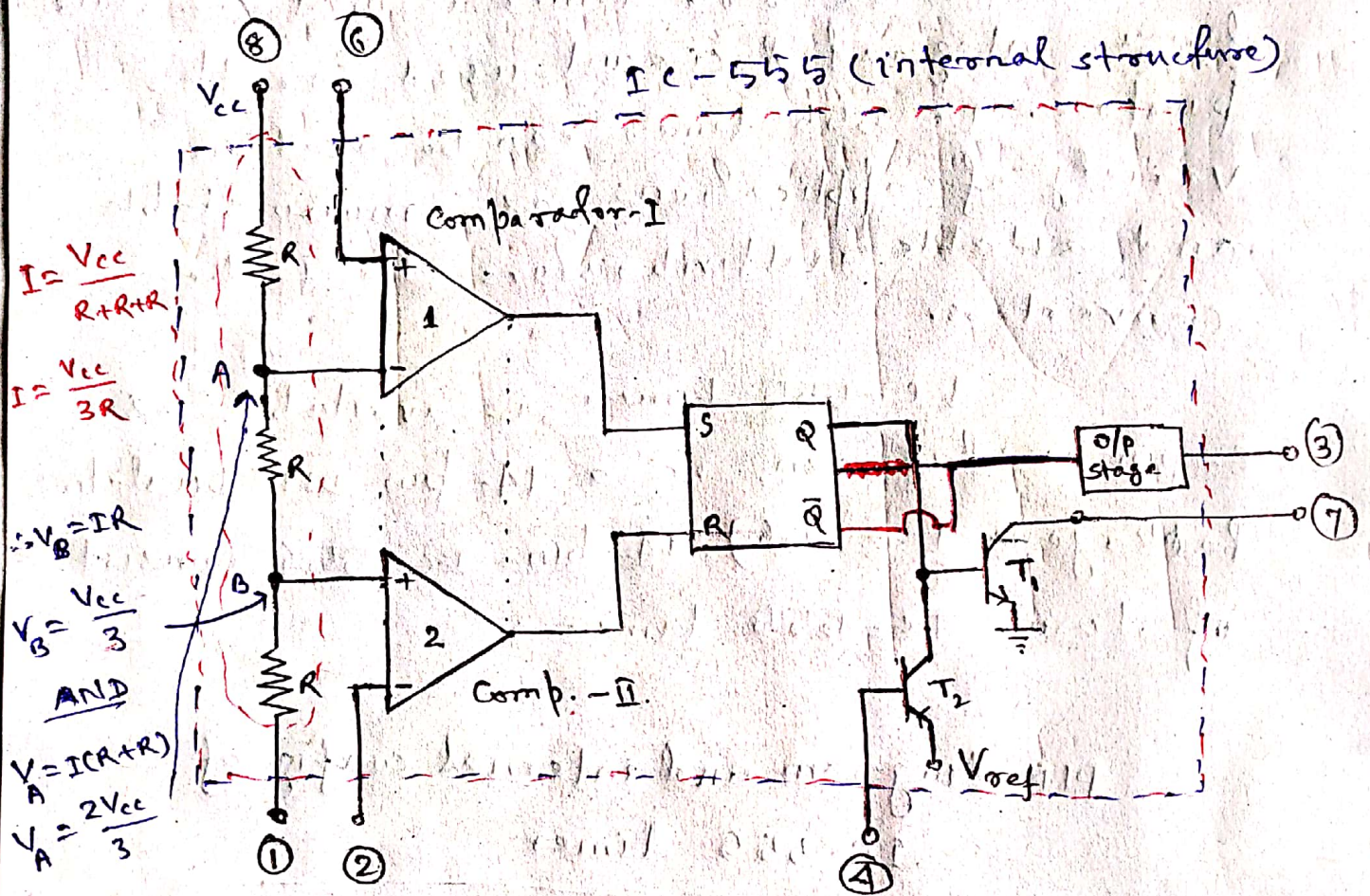


Fig-2

Pin-2. The output of timer can be controlled (Triggers) by this pin. The output is low if the voltage at this pin is greater than $\frac{2V_{cc}}{3}$. In negative going pulse of amplitude larger than $\frac{V_{cc}}{3}$, is applied to this pin, comparator-II output goes LOW, which in turn

make the output high. The output will remain high as long as the trigger terminal has a low voltage.

Pin-3 :- The complementary signal out ($\bar{Q}$)
(Output) of the flip-flop goes through an output stage and becomes o/p of timer.

Pin-4 :- In most of the applications, Pin-4 is
(Reset) not used and this pin is connected to supply $+V_{cc}$ to avoid any false triggering.

Pin-5 :- The pulse width of output
(Control voltage) waveform can be varied by imposing a voltage at this pin. In most application, this pin is not required and a capacitor (0.01 μF) is connected at this pin and ground to prevent noise problem in ckt.

Pin-6 :- When, voltage at this pin is greater
(Threshold) than $\frac{2V_{cc}}{3}$, the output of comparator goes HIGH which makes the output of timer LOW, (as o/p taken from $\bar{Q}$)

Pin-7 :- A capacitor is connected externally to
(Discharge) ground at this pin. Internally the collector of discharge transistor is coming at this pin. Now a high $\bar{Q}$ -output from flip-flop makes transistor T_1 - OFF. i.e. open-ckt

and the external capacitor charges at the rate determined by external RC network. When, the output Q is LOW, transistor gets saturated and external capacitor discharges.

Pin-8
(Supply $+V_{cc}$) : The IC-555 timer works with voltage +5 volt to +18 volt with respect to Pin-4. V_{cc} is applied at Pin-8.