

Assignment on passive filters

①

- ① Design a constant K-low pass filter having $f_c = 2\text{kHz}$ and design impedance $R_0 = 600\Omega$. Obtain the value of attenuation at ~~4000~~ 4kHz .

Page No-762: (A. data book)

- ② Design a constant K-high pass filter, having $f_c = 4\text{kHz}$ and design impedance $R_0 = 600\Omega$.

- ③ Design an R-L HP filter with $f_c = 2\text{kHz}$ and having $R = 2k\Omega$.

- ④ In a series LCR type BPF, $L = 50\text{mH}$, $C = 127\mu\text{F}$ and $R_F = 63\Omega$. Determine

- (i) the resonance frequency
- (ii) the band width.
- (iii) the cut-off frequencies.

- ⑤ In a LCR type band stop filter $R = 1k\Omega$, $L = 115\text{mH}$, $C = 400\text{pF}$, Determine (i) the bandwidth (ii) cut-off frequency (iii) Output voltage at f_1 , f_2 and f_0 .

- ⑥ In a series resonance type BPF, $C = 18\text{pF}$, $L = 25\text{mH}$, $R_F = 52\Omega$ and $R_L = 9k\Omega$. Find f_0 and BW.

Solution:-

(1)

(1) The values of the elements of constant-K-low pass filter are.

The series arm inductance.

$$L = \frac{R_0}{\pi f_c} = \frac{600}{\pi \times 2 \times 10^3} \text{ H} = 95.493 \text{ mH}$$

The shunt capacitance,

$$C = \frac{1}{\pi f_c R_0} = \frac{1}{\pi \times 2 \times 10^3 \times 600} \text{ F} = 0.265 \mu\text{F}$$


Let attenuation at 4 kHz be α , where α is

given by relation,

$$\alpha = 2 \cosh^{-1} \left(\frac{f_x}{f_c} \right)$$

$$= 2 \cosh^{-1} \left(\frac{4000}{2000} \right) \text{ nepers} = 2.634 \text{ nepers}$$

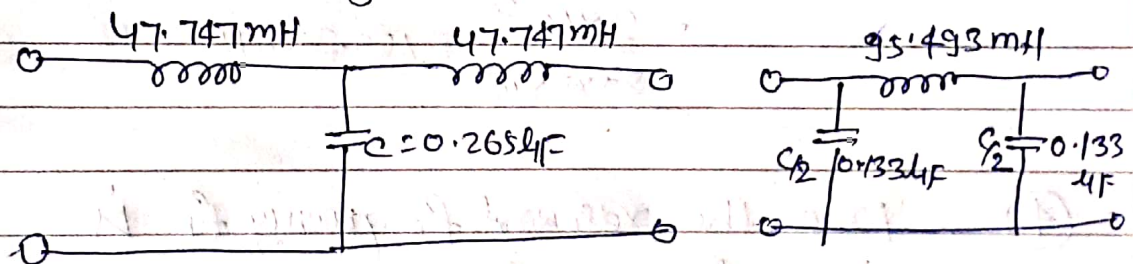The required T and π -section low pass filters are shown in fig. below.



(2) From the theory of high pass filter, the series arm capacitance (C) and shunt arm inductance (L) are given by


$$C = \frac{1}{4\pi R_0 f_c} = \frac{1}{4 \times \pi \times 600 \times 4000} \text{ F} = 0.033 \mu\text{F}$$

$$\text{and } L = \frac{R_0}{4\pi f_c} = \frac{600}{4 \times \pi \times 4000} \text{ H} = 11.937 \text{ mH}$$

P.T.O

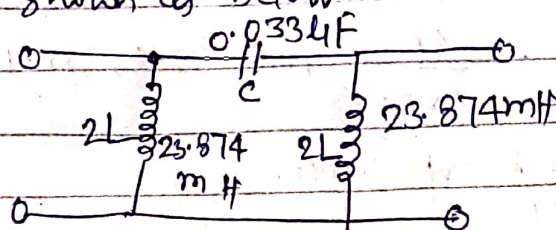(3)

The required constant K π -section high pass filter is shown as below



Constant K π -section HPF

(3) From the equation of R-L HP filter

$$L = \frac{R}{2\pi f_c}$$

$$= \frac{2 \times 10^3}{2\pi \times 2 \times 10^3}$$

$$= \frac{2 \times 10^{-3}}{2\pi \times 2 \times 10^3} = 159.25 \text{ mH}$$

(4) From the resonant frequency f_r is given by

$$f_r = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

$$= \frac{1}{2\pi\sqrt{50 \times 10^{-3} \times 127 \times 10^{-9}}} = 2 \text{ KHz}$$

Again, $R = \frac{R_F \times R_L}{R_F + R_L} = \frac{63 \times 600}{63 + 600} = 57 \Omega$

$$\therefore \text{BW (band width)} = \frac{f_r}{Q} = \frac{2 \times 10^3}{11} = 181.8 \text{ Hz}$$

$$\left[Q = \frac{\omega_r L}{R} = \frac{2\pi \times 0.05}{57} = 11 \right]$$

(4)

f_1 = lower cut-off frequency

$$= f_r - \frac{BW}{2}$$

$$= 2 \times 10^3 - \frac{182}{2} = 1909 \text{ Hz}$$

$\therefore f_2$ = Higher cut-off frequency

$$= f_r + \frac{BW}{2}$$

$$= 2 \times 10^3 + \frac{182}{2} = 2091 \text{ Hz}$$

(5)

We know that

$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.155 \times 400 \times 10^{-12}}} \\ = 20.50 \text{ KHz}$$

However, $Q = \frac{W_r L}{R}$

$$= \frac{2\pi(20.55 \times 10^2) \times 0.155}{1 \times 10^3} = 20 \text{ Hz}$$

But it is evident that $Q = \frac{f_r}{BW}$

$$\therefore BW = \frac{f_r}{Q} = \frac{20.50 \times 10^3}{20} = 1025 \text{ Hz}$$

$$\text{Also, } f_1 = f_r - \frac{BW}{2} = 20 \times 10^3 - \frac{1025}{2} \\ = 19.49 \text{ KHz}$$

(5)

~~The requi~~

$$\text{and } f_2 = f_r + \frac{BW}{2} = 20 \times 10^3 + \frac{1025}{2}$$

$$= 20.51 \text{ KHz.}$$

We observe that for the BSF given in the question

$$|Z| = |X_L - X_C|$$

$$\& |Z_T| = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\text{at } f_r, X_L = X_C$$

$$|Z| = 0 \& |Z_T| = R$$

This gives $V_0 = V_i \frac{0}{R} = 0$ at f_r

i.e. at $f = f_r$ the signal is completely attenuated
at $f = f_1$

$$\therefore X_L = 2\pi \times 19.49 \times 10^3 \times 0.155 = 18.97 \text{ k}\Omega$$

$$X_C = \frac{1}{2\pi \times 19.49 \times 10^3 \times 400 \times 10^{-12}}$$

$$= 20.4 \text{ k}\Omega$$

$$\therefore |X_L - X_C| = -1410 \Omega$$

$$V_0 = V_i \frac{\sqrt{(-1410)^2}}{\sqrt{(1000)^2 + (-1410)^2}} = 0.81 \text{ V (volts)}$$

$$\text{at } f = f_2$$

$$X_L = 2\pi \times 20.51 \times 10^3 \times 0.155 = 19.97 \text{ k}\Omega$$

$$X_C = \frac{1}{2\pi \times 20.51 \times 10^3 \times 400 \times 10^{-12}} = 19.45 \Omega$$

$$\therefore |X_L - X_C| = 1150 \Omega$$


$$\therefore V_0 \text{ at } f = f_2 \text{ is } V \frac{\sqrt{(1150)^2}}{\sqrt{(1000)^2 + (1150)^2}} = 0.75 V_i \text{ volts}$$

i.e. 75% of the signal will pass at $f = f_2$.

Ideally 70.7% signal should have passed through for $f = f_1$ or f_2 .

The error has come due to negligence of resistance in the inductance coil which should be taken into account for all accurate calculations.

(6)

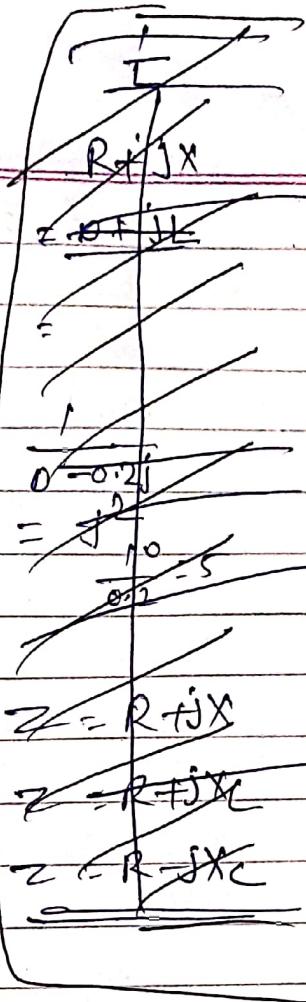

(6)

We know that-

$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi \times 0.025 \times 1.8 \times 10^{-12}} = 751 \text{ KHz}$$

$$\text{and } R = \frac{R_F \times R_L}{R_F + R_L} = \frac{52 \times 9000}{52 + 9000} = 52 \Omega$$

$$\therefore Q_{\text{factor}} = \frac{\omega_r L}{R} = \frac{2\pi \times 751 \times 25 \times 10^{-3}}{52} = 2270$$

$$\text{Thus } BW = \frac{f_r}{Q} = \frac{751 \times 10^3}{2270} = 331 \text{ Hz}$$

f_1 and f_2 can also be found out as

7

$$f_1 = f_r - \frac{BW}{2} = 751 \times 10^3 - \frac{331}{2}$$

$$= 750.849 \text{ KHz}$$

Ans) $f_2 = f_r + \frac{BW}{2} = 751.162 \text{ KHz}$