

Envelope Detector:-


An envelope detector is a simple and yet highly effective device that is well-suited for the demodulation of AM signal, for which the percentage modulation is less than 100%. ($m < 1$).

Ideally, an envelope detector produces an output signal that follows the envelope of the i/p signal waveform exactly; hence the name.


Envelope for some standard signals:-

- | <u>ED i/p</u> | <u>ED o/p</u> |
|---|---------------------|
| 1. $V_m \cos 2\pi f_m t$
or
$V_m \sin 2\pi f_m t$ | V_m |
| 2. $A_c(1 + k_a m(t)) \cos 2\pi f_c t$ | $A_c(1 + k_a m(t))$ |
| 3. $A \cos 2\pi f_1 t + B \sin 2\pi f_2 t$ | $\sqrt{A^2 + B^2}$ |

Ckt diagram:-

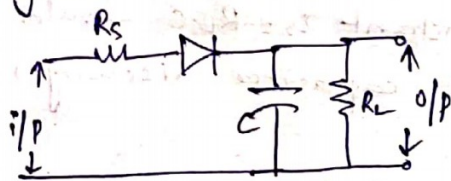


Let's apply i/p as $V_i(t) = V_m \sin 2\pi f_m t$

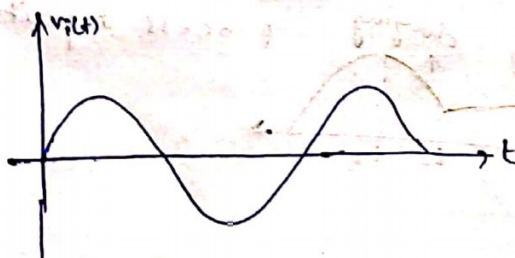

Case 1:-

For $t = 0^+$; voltage at p-side of p-n junction diode is greater than in n-side.
 $\therefore$ diode is F.B. $\Rightarrow$ short circuit


$\therefore$ equivalent ckt diagram:-

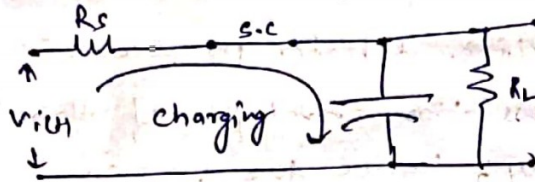

Here, the time constant $\tau_1 = R_S \cdot C$ should be very small so that capacitor rapidly charges to i/p voltage.

Case 2:-

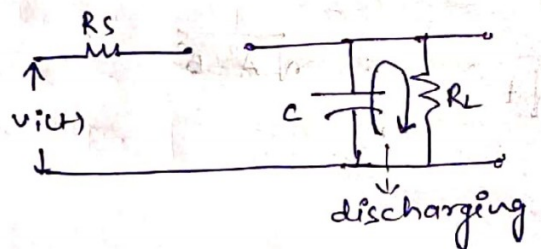
For $t = t_1^+$; voltage at p-side < voltage at n-side.
 $\therefore$ diode is R.B. $\Rightarrow$ open circuit




Here, the time constant $\tau_2 = R_L \cdot C$ should be ~~very~~ high so that capacitor discharges slowly.

Case 3:-

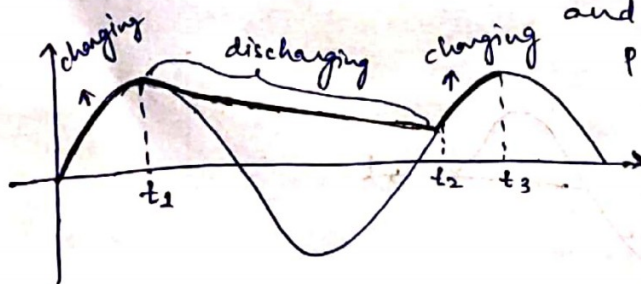
For $t = t_2^+$ to $t_3 \Rightarrow$ diode again in F.B and same charging process repeats.



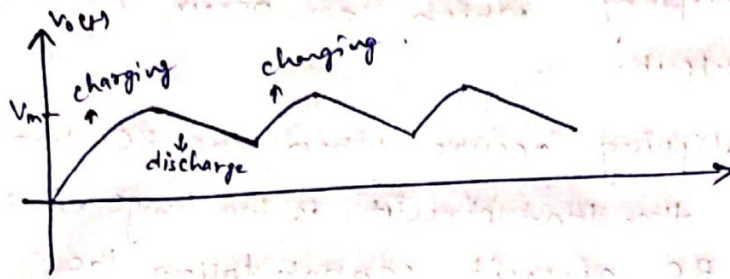Now, voltage across capacitor which will be seen at o/p.



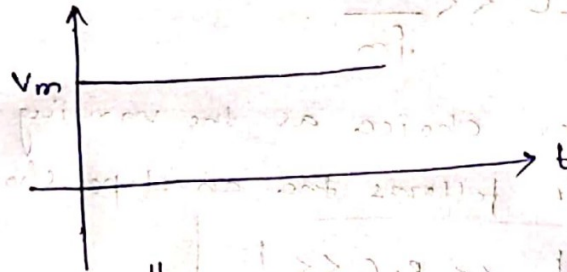
Now, we will pass this output through a smoothing filter to get smooth envelope of input.



↓
this is the final output for envelope detector

Note:- To make capacitor voltage to follow the envelope of i/p signal, $R_s C$ should be very small & $R_L C$ should be very high.

Now, for AM signal as i/p:-

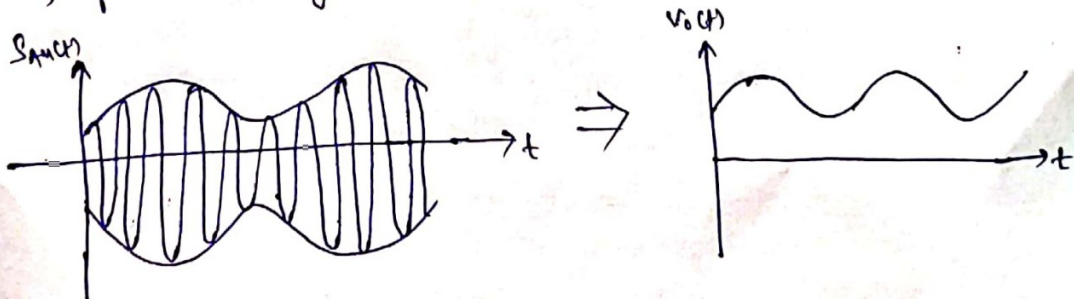

for AM signal, we have two different frequencies f_c & f_m where $f_c \gg f_m$

In Envelope detector, there is a distortion called 'diagonal clipping' which can occur in the detector output.

⇒ Diagonal clipping occurs when the RC time constant of the load circuit is too large. Due to this the RC circuit cannot follow the fast changes in the modulating envelope.

∴ To avoid diagonal clipping

$$RLC \ll \frac{1}{f_m}$$

And, proper choice as the varying voltage across R_L follows the envelope should be-

$$\left\{ \frac{1}{f_c} \ll RLC \ll \frac{1}{f_m} \right\}$$

If RLC is very small or RLC is very large, then in both cases we can't get the envelope of message signal waveform.



Q:- Determine the minimum value of 'A_c'
to get the true envelope of input amplitude
modulate wave, given as:-

$$s(t) = A_c \cos \omega_c t + 2 \cos \omega_m t \cos \omega_c t$$

$$\text{or, } s(t) = A_c \cos 2\pi f_c t + 2 \cos 2\pi f_m t \cos 2\pi f_c t$$