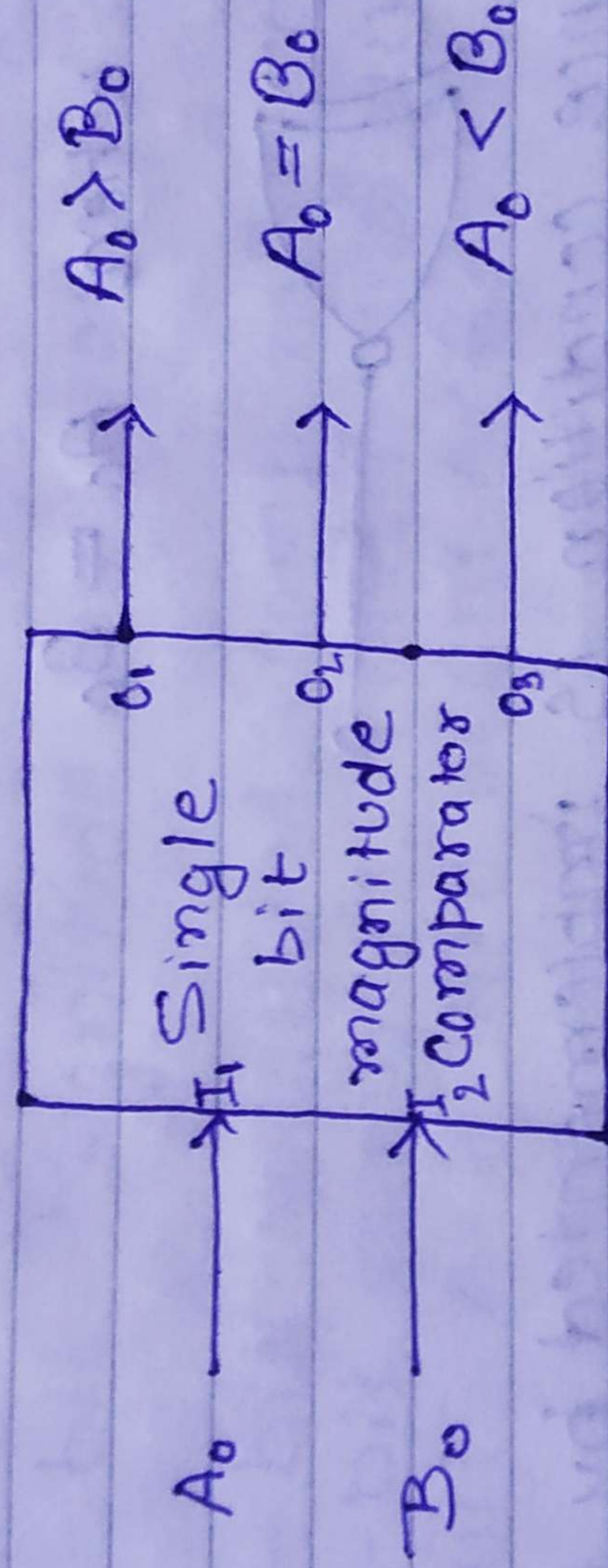


Magnitude Comparator

A Magnitude Comparator is a Combinational circuit that compares the magnitude of two numbers A and B and generate one of the following outputs: $A=B$, $A < B$ and $A > B$.

The block diagram of a Single-bit magnitude Comparator is given below



A_0 and B_0 will be provided at input port I_1 & I_2 respectively.


If A_0 is greater than B_0 , i.e. $A_0 > B_0$, then output port 1 (O_1) will be high i.e. '1'.

If A_0 is equal to B_0 , i.e. $A_0 = B_0$, then output port 2 (O_2) will be high, i.e. '1'.

If A_0 is smaller than B_0 , then output port 3 (O_3) will be high.


In order to implement the magnitude comparator

case I, when $A_0 > B_0$

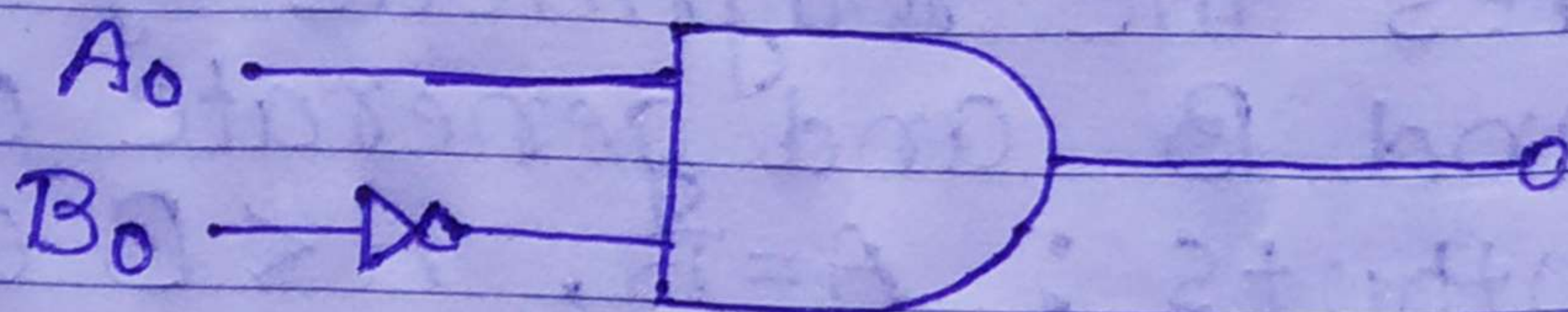

In the above logic setup output will be high only if $A_0 = 1$ and $B_0 = 0$ i.e. $A_0 > B_0$

Case II, when $A_0 = B_0$

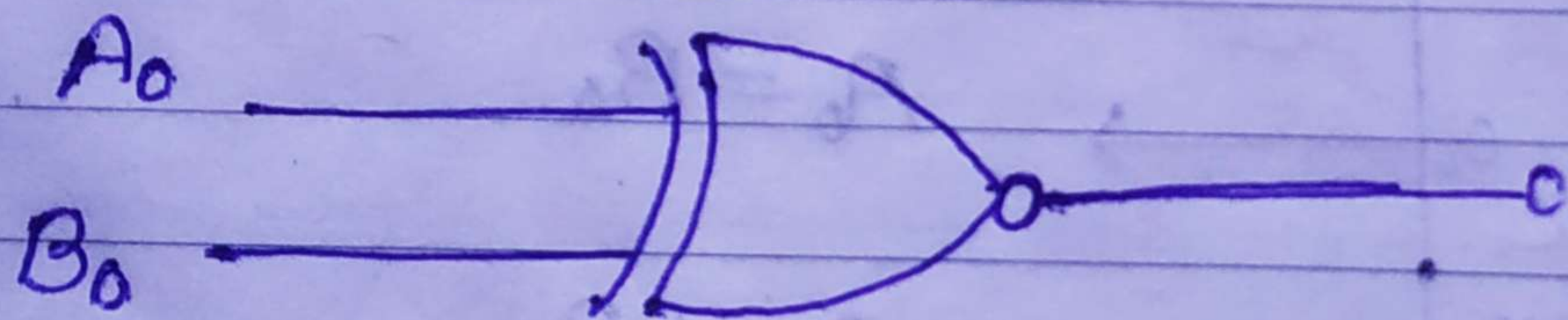


The equivalence condition is implemented by using EXNOR gate, as output of EX-NOR is '1' only when both inputs are equal.

case III, when $A_0 < B_0$



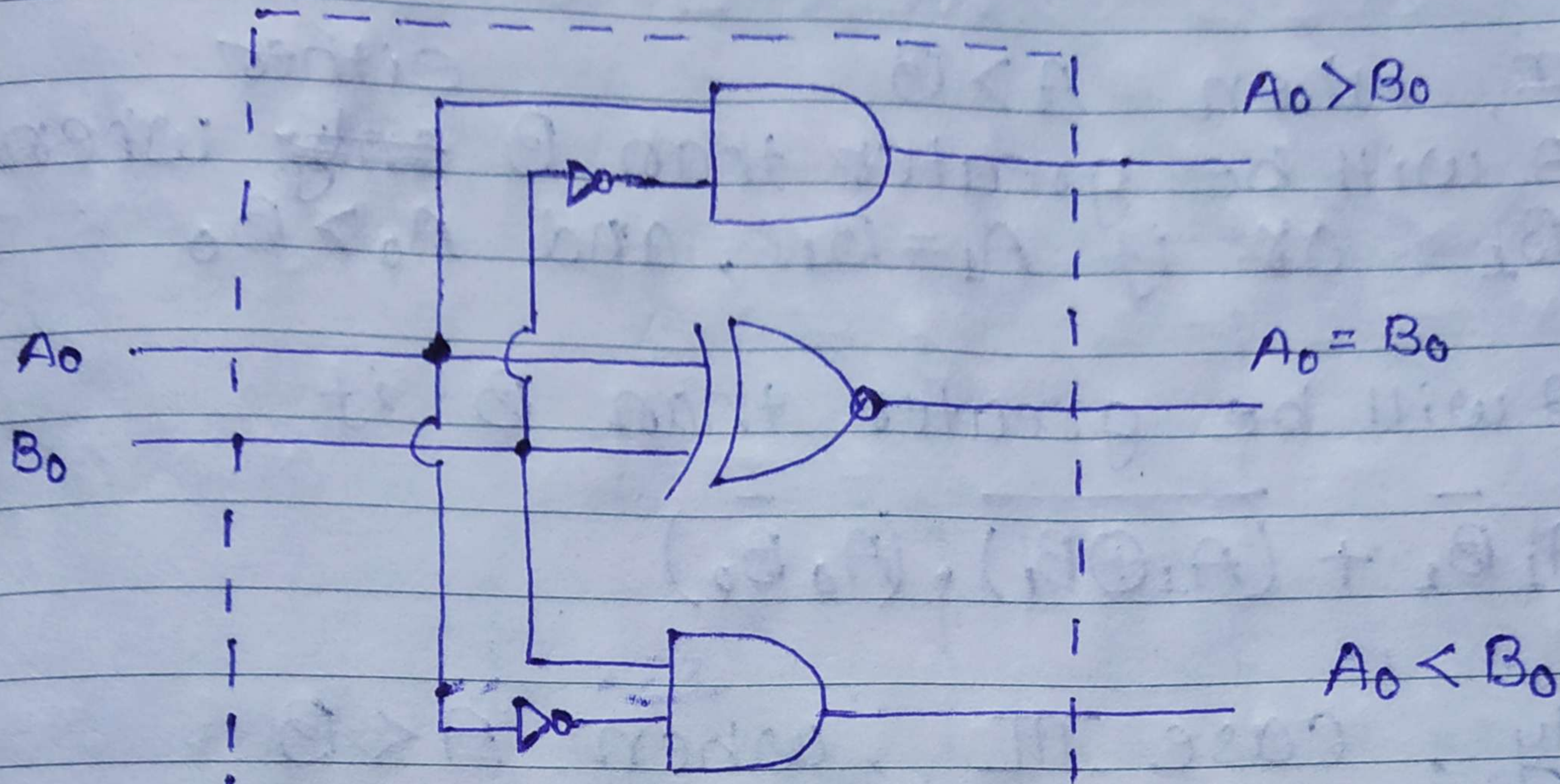In the above logic setup output will be '1' only if $A_0 = 0$ and $B_0 = 1$ i.e. $A_0 < B_0$



single bit magnitude comparator.


2-bit Magnitude Comparator.

A 2-bit magnitude comparator compares two 2-bit numbers A and B, and gives following result $A=B$, $A>B$ and $A<B$.

Let $A = \overset{\text{MSB}}{A_1} \overset{\text{LSB}}{A_0}$
 $B = B_1 B_0$

Case I, when $A=B$

$A=B$, only when $A_1=B_1$ and $A_0=B_0$

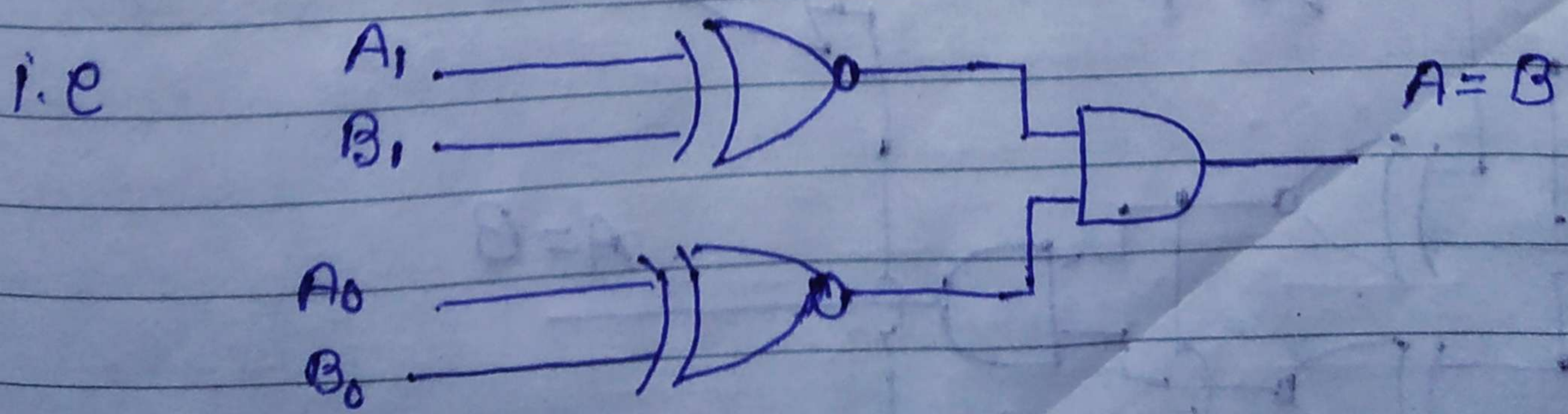

Case II, when $A > B$ either
~~A~~ A will be greater than B ~~only~~ when
 $A_1 > B_1$ or if $A_1 = B_1$, and $A_0 > B_0$

i.e A will be greater than B if

$$A_1 \bar{B}_1 + \overline{(A_1 \oplus B_1)} \cdot (A_0 \bar{B}_0)$$


Similarly, Case III, when $A < B$

Compare the MSB, if $A_1 < B_1$, then
 $A < B$

If $A_1 = B_1$, then Compare LSB or next
bit to MSB, if $A_0 < B_0$ then $A < B$

So $A < B$ if
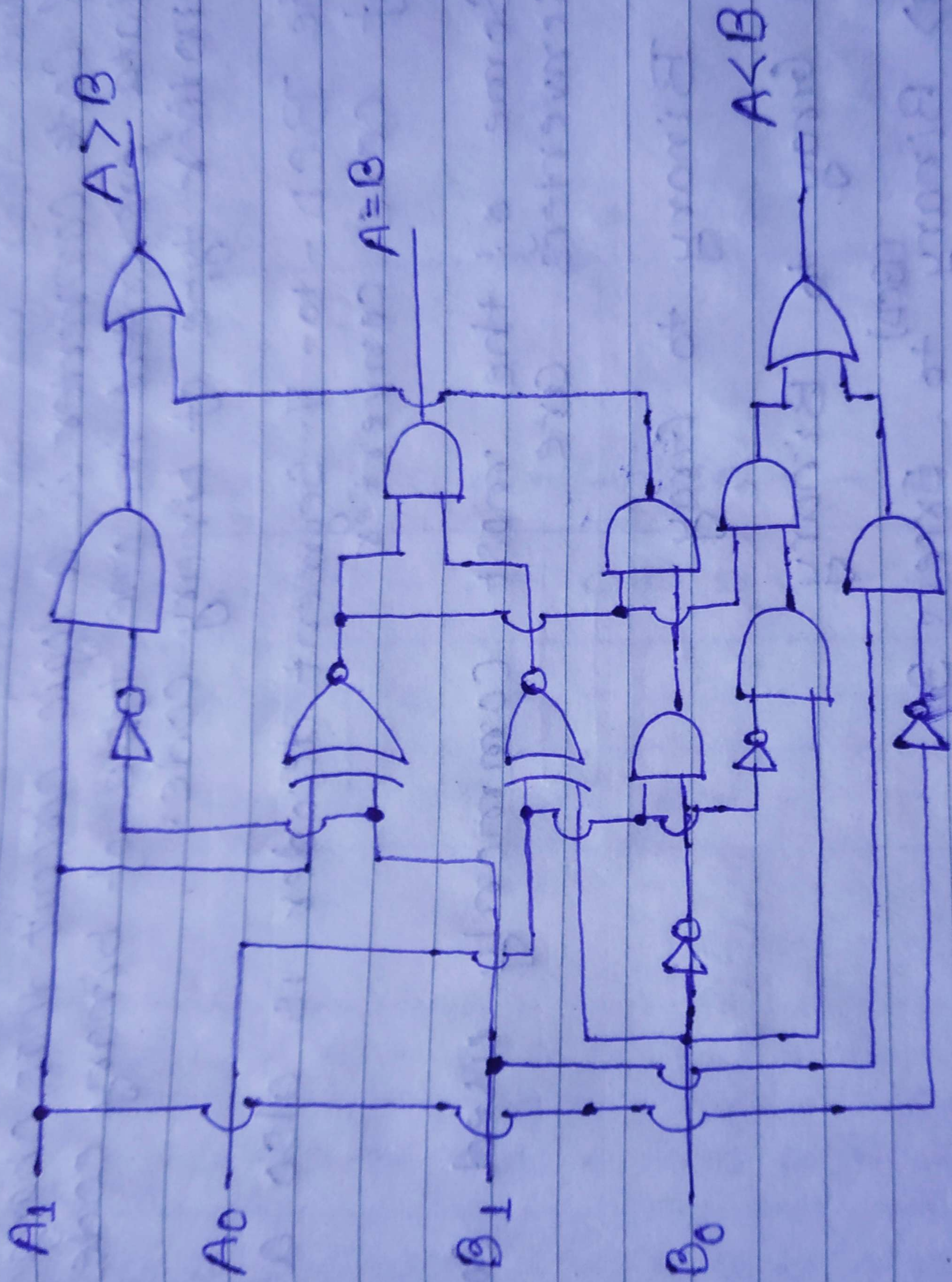
$$\bar{A}_1 B_1 + \overline{(A_1 \oplus B_1)} \cdot (\bar{A}_0 \cdot B_0)$$



2-bit Magnitude Comparator.

CODE CONVERTERS

A Code converter is a logic circuit that changes data presented in one type of binary code to another type of binary code.


The BCD-to-7-Segment decoder is also a kind of code converter.

Some of the most commonly used Code Converters are

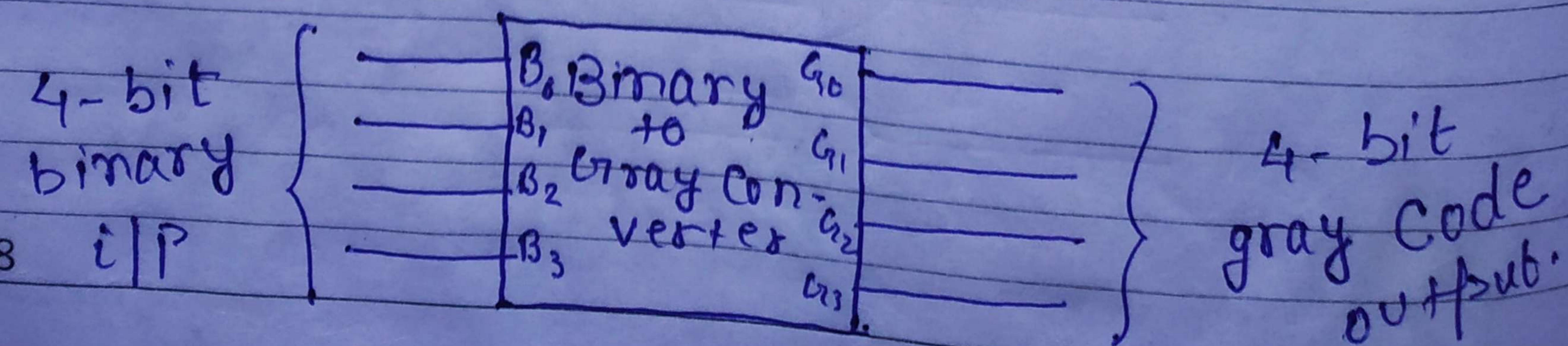- i) Binary to Gray
- ii) Gray to Binary
- iii) Binary^(BCD) to Excess 3
- iv) ~~ASCII~~ ASCII to EBCDIC etc.

Binary to Gray Code Converters

In this code converter input will be in binary form, the converter will convert the binary data into Gray code.



Truth table of binary to gray code converter

Binary 2/P					Gray Code output			
	B ₃	B ₂	B ₁	B ₀	G ₃	G ₂	G ₁	G ₀
0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	1
2	0	0	1	0	0	0	1	1
3	0	0	1	1	0	0	1	0
4	0	1	0	0	0	1	1	0
5	0	1	0	1	0	1	1	1
6	0	1	1	0	0	1	0	1
7	0	1	1	1	0	1	0	0
8	1	0	0	0	1	1	0	0
9	1	0	0	1	1	1	0	1
10	1	0	1	0	1	1	1	1
11	1	0	1	1	1	1	1	0
12	1	1	0	0	1	0	1	0
13	1	1	0	1	1	0	1	1
14	1	1	1	0	1	0	0	1
15	1	1	1	1	1	0	0	0

From the truth table above, G₀, G₁, G₂ & G₃ can be expressed in minterm as


$$G_0 = \sum m(1, 2, 5, 6, 9, 10, 13, 14)$$

$$G_1 = \sum m(2, 3, 4, 5, 10, 11, 12, 13)$$

$$G_2 = \sum m(4, 5, 6, 7, 8, 9, 10, 11)$$

$$G_3 = \sum m(8, 9, 10, 11, 12, 13, 14, 15)$$

Simplifying for G_0 , using K-map we get

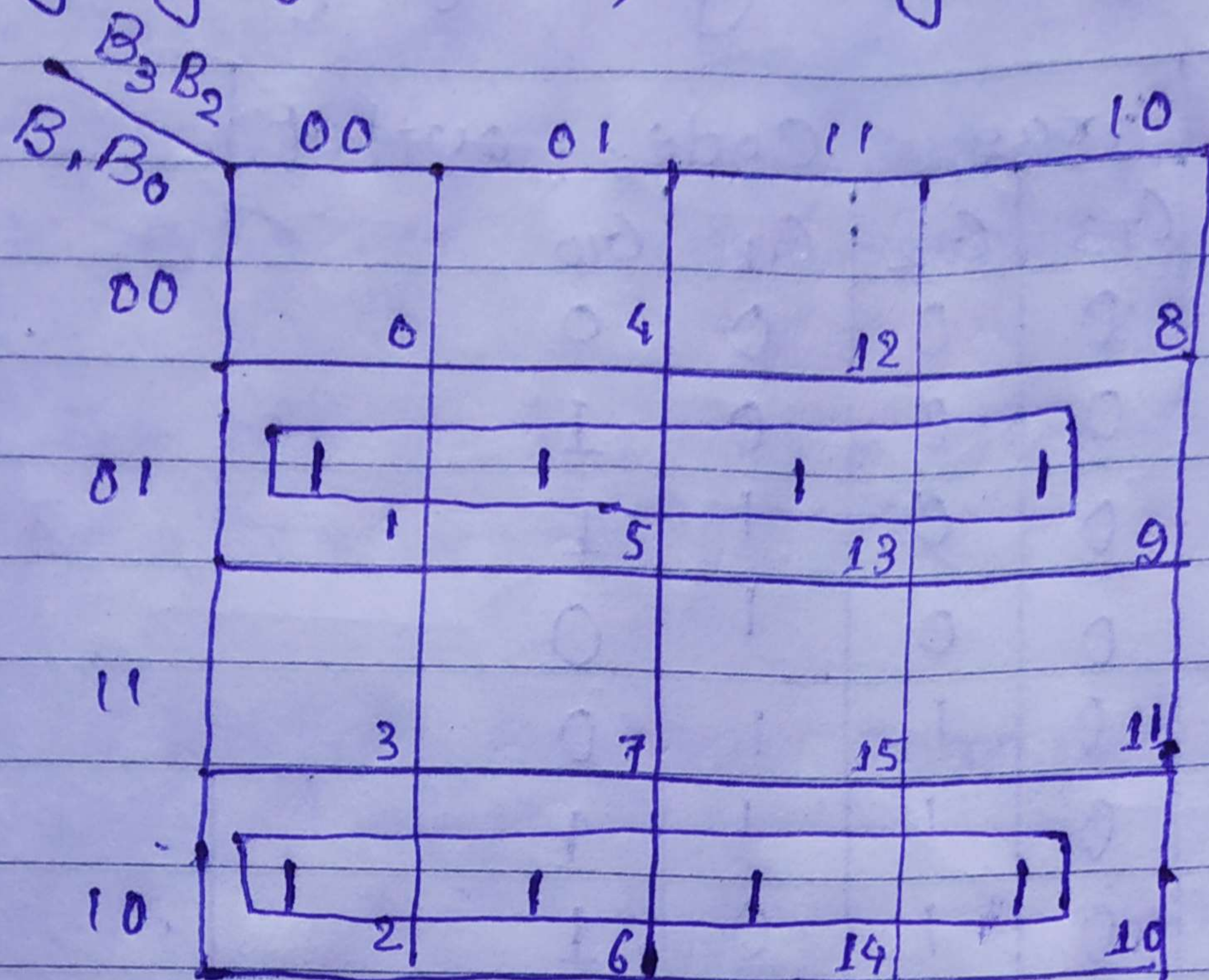


$$G_0 = \bar{B}_1 \bar{B}_0 + B_1 \bar{B}_0 = B_1 \oplus B_0$$

Similarly

$$G_1 = B_2 \oplus B_1$$

$$G_2 = B_3 \oplus B_2$$

$$G_3 = B_3$$

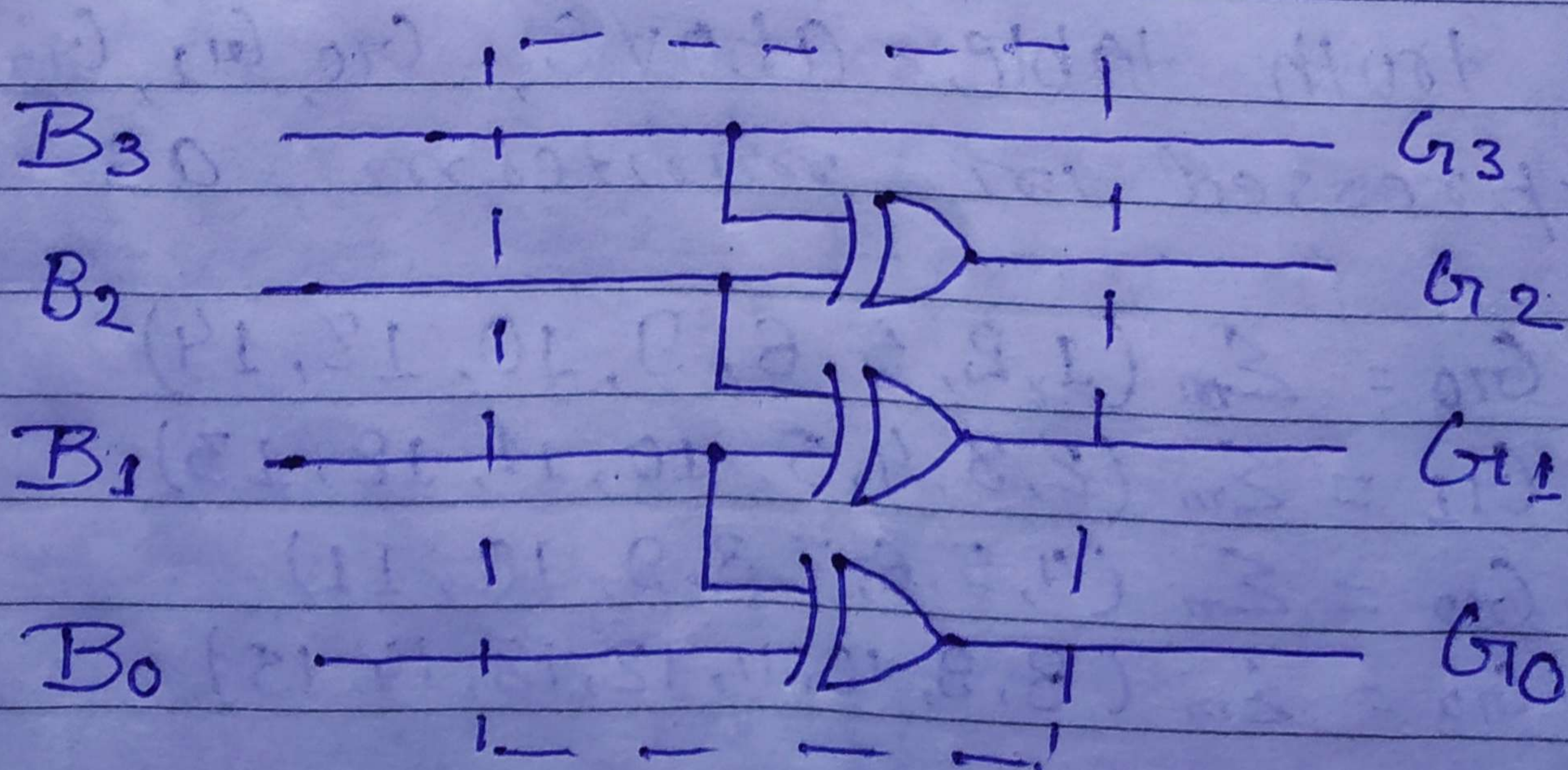

Logic diagram of 4-bit Binary to Gray Converter.

BCD to Excess-3 Code Converter

APRIL • WEDNESDAY

115-250 • WK17

Truth Table of BCD to Excess-3 Code Converter is given below

	BCD input				Excess-3 Code output			
	B_3	B_2	B_1	B_0	E_3	E_2	E_1	E_0
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0
10	1	0	1	0	d	d	d	d
11	1	0	1	1	d	d	d	d
12	1	1	0	0	d	d	d	d
13	1	1	0	1	d	d	d	d
14	1	1	1	0	d	d	d	d
15	1	1	1	1	d	d	d	d

As the input is BCD, so we need to consider the case only for 0 to 9, rest will be treated as don't care conditions.

So, E_0, E_1, E_2 & E_3 can be written in ~~dear~~ terms of minterm as

$$E_0 = \sum_m(0, 2, 4, 6, 8) + \sum_d(10, 11, 12, 13, 14, 15)$$

$$E_1 = \sum_m(0, 3, 4, 7, 8) + \sum_d(10, 11, 12, 13, 14, 15)$$

$$E_2 = \sum_m(1, 2, 3, 4, 9) + \sum_d(10, 11, 12, 13, 14, 15)$$

$$E_3 = \sum_m(5, 6, 7, 8, 9) + \sum_d(10, 11, 12, 13, 14, 15)$$

Solving E_0 , using K-map, we get

$B_3 B_2$ $B_1 B_0$	00	01	11	10
00	1 0	1 4	d 12	1 8
01	1 5	d 13		9
11	3 7	d 15	d 11	
10	1 2	1 6	d 14	d 10

$$E_0 = \overline{B_0}$$

Solving for E_1

$B_3 B_2$ $B_1 B_0$	00	01	11	10
00	1 0	1 4	d 12	1 8
01	1 5	d 13		9
11	1 3	1 7	d 15	d 11
10	2 6	d 14		d 10

$$E_1 = \overline{B_1} \overline{B_0} + B_1 B_0$$

$$= B_1 \odot B_0$$

Solving for E_2

APRIL • FRIDAY

117-248 • WK17

$B_3 B_2$	00	01	11	10
$B_1 B_0$				
00	0	1 1 4	d 12	8
01	1 1	5	d 13	9
11	3	7	d 15	11
10	2	6	d 14	10

$$E_2 = \overline{B}_2 B_0 + \overline{B}_2 B_1 + B_2 \overline{B}_1 \overline{B}_0$$

Solving for E_3

$B_3 B_2$	00	01	11	10
$B_1 B_0$				
00	0	4	d 12	8
01	1	5	d 13	9
11	3	7	d 15	11
10	2	6	d 14	10

$$E_3 = B_3 + B_2 B_0 + B_2 B_1$$

Logic diagram of BCD to Excess-3 Code converter

