

4. MAXWELL'S INDUCTANCE BRIDGE

Objective:

To determine the unknown value of inductance by comparing with a variable standard self inductance using Maxwell's Inductance bridge.

Apparatus:

Software: Lab view software.

Hardware:	Name of the apparatus	Quantity
	Transformer 230/15v	1 No
	Bread board	1 No
	Resistors	4 No
	Variable Resistor	1 No
	Inductors	2 No
	Digital Multimeter	1 No

Theory:



This bridge circuit measures an inductance by comparison with a variable standard self-inductance. The connections and the phasor diagrams for balance conditions are shown below.

Let, L_1 = unknown inductance of resistance R_1 ,

L_2 = variable inductance of fixed resistance r_2 ,

R_2 = variable resistance connected in series with inductor L_2 ,

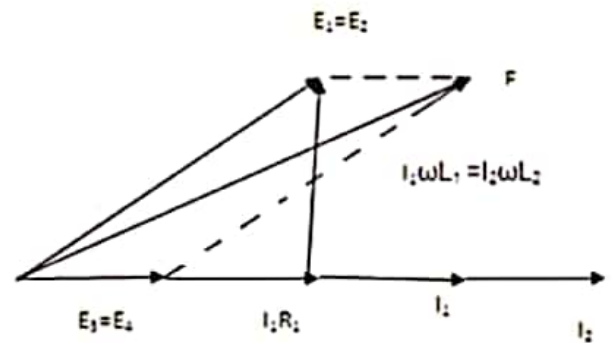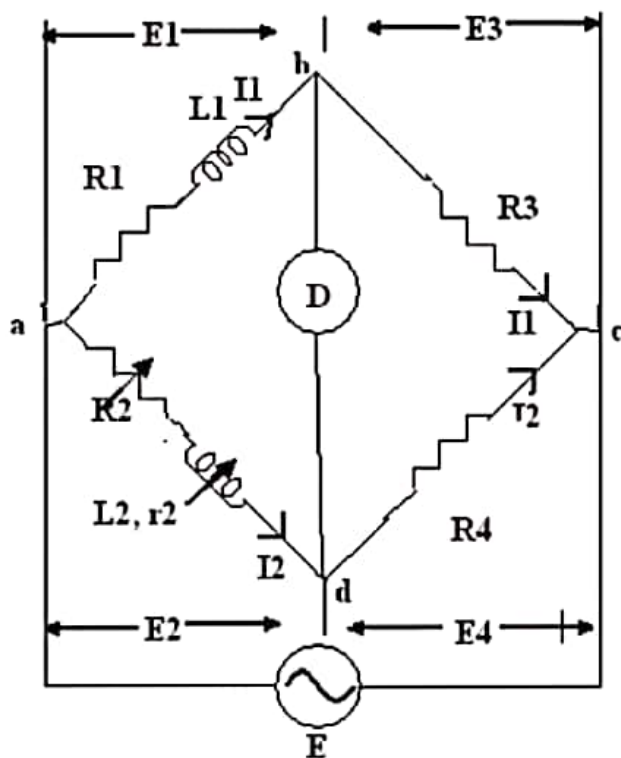R_3, R_4 = known non-inductive resistances.




At balance, $L_1 = R_3 L_2 / R_4$, $R_1 = R_3 (R_2 + r_2) / R_4$.

Procedure:


1. Connect the circuit as shown in the figure.
2. Connect the unknown inductance in L_1 .
3. Connect the multimeter between ground and output of imbalance amplifier.
4. Vary R_2 from minimum position, in clockwise direction.
5. If the selection of R_2 is correct the balance point can be obtained at minimum position.
6. Vary R_2 for fine balance adjustment.

Observation:

S.NO	R_2	R_3	C_1	$L_1 = R_3 L_2 / R_4$	True value of L_1

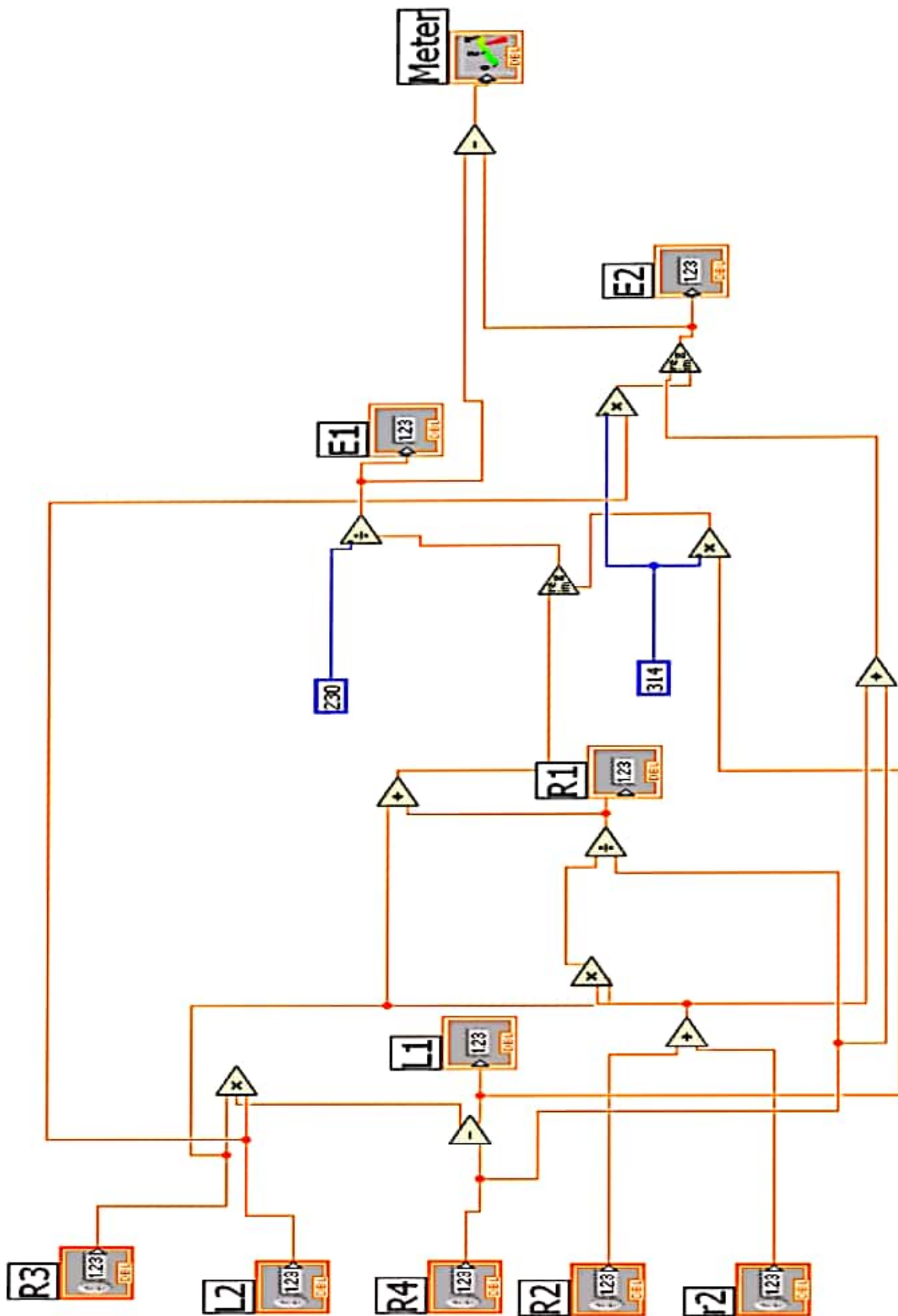

MAXWELL'S INDUCTANCE BRIDGE

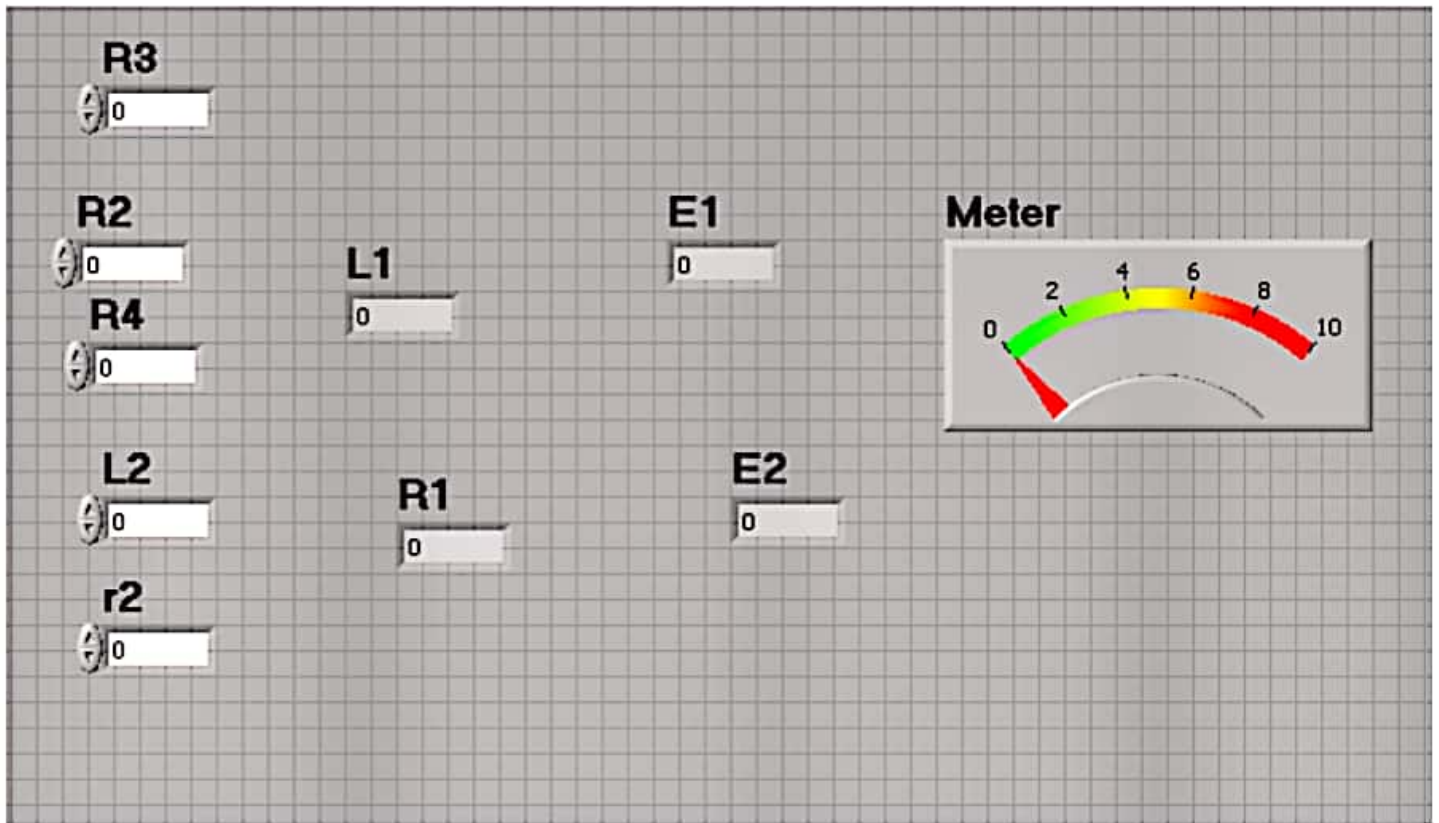

Result:

Actual and practical values of Inductances are found to be nearly equal.