

Frequency Response Curve of an Amplifier

The curve drawn for voltage versus frequency is known as frequency response curve.

The frequency response of an amplifier may be divided into three regions as —

i) Mid-band region where the gain is reasonably constant say A_0 . Here, we consider the normalized value as $A_0 \approx 1$.

ii) Low-frequency band: — Below the mid-frequency region, the voltage gain is not uniform and amplifier behaves like simple High-Pass Filter. In this low-frequency range frequency response decreases with decrease in frequency.

Low Frequency Response: —

Let, us consider a simple High-Pass Filter as shown in adjacent fig. consisting of capacitor and a resistor R .

Here, ckt 'does not allow to pass a signal of low frequency because the capacitor offers high impedance to signal of lower

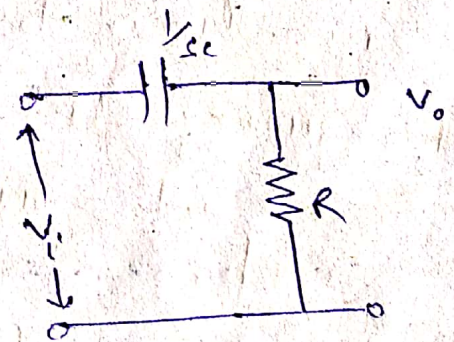


Fig-1.

frequency and no output appears across load R .

On the other hand, ckt offers very small or negligible resistive path to the frequency of high frequency signal. Hence, it HPF.

(2)

Now, applying KVL —

$$V_i = V_c + V_o = I \left(\frac{1}{j\omega C} \right) + IR$$

$$V_o = IR$$

$$\therefore \frac{V_o}{V_i} = \frac{I \left[R + \frac{1}{j\omega C} \right]}{IR}$$

$$\text{or } A_{vL} = \frac{V_o}{V_i} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{1}{1 + \frac{1}{j\omega RC}}$$

$$\text{or } A_{vL} = \frac{1}{1 - j \frac{1}{2\pi f RC}} = \frac{1}{1 - j \frac{f_L}{f}}$$

Here, $f_L = \frac{1}{2\pi RC}$ = Lower cut-off frequency

$$\therefore \boxed{A_{vL} = \frac{1}{1 - j \frac{f_L}{f}}}$$

$$|A_{vL}| = \frac{1}{\sqrt{1 + \left(\frac{f_L}{f} \right)^2}}$$

$$\angle A_{vL} = \angle(1 + 0j) - \angle\left(1 - j \frac{f_L}{f}\right)$$

$$= \tan^{-1}\left(\frac{0}{1}\right) - \tan^{-1}\left\{\frac{-\frac{f_L}{f}}{1}\right\}$$

$$\theta_L = \tan^{-1}\left(\frac{f_L}{f}\right) = \angle A_{vL}$$

$$|A_{vL}|_{dB} = 20 \log \left[1 + \left(\frac{f_L}{f} \right)^2 \right]^{-\frac{1}{2}} = -10 \log \left[1 + \left(\frac{f_L}{f} \right)^2 \right]$$

Since here $f \ll f_L$ i.e. frequency is very low

$$\therefore \frac{f_L}{f} \gg 1 \Rightarrow \left(\frac{f_L}{f} \right)^2 \gg 1$$

$$\therefore |A_{vL}|_{dB} = -10 \log \left[1 + \left(\frac{f_L}{f} \right)^2 \right] \approx -10 \log \left(\frac{f_L}{f} \right)^2 = -20 \log \left(\frac{f_L}{f} \right)$$

Low-pass filter does not have zero at origin.

$$|A_{v1}|_{dB} = -20 \log \left(\frac{f_L}{f} \right)$$

(3)

Let, $f = 0.01 f_L$, $|A_{v1}|_{dB} = -20 \log \left(\frac{f_L \times 100}{0.01 f_L} \right) = -40 \text{ dB}$

when, $f = 0.05 f_L$, $|A_{v1}|_{dB} = -20 \log \left(\frac{f_L \times 100}{0.05 f_L} \right) = -20 \log 20$
 $= -20 \log 2 - 20 \log 10 = -20 \times 0.301 - 20$
 $= -26 \text{ dB}.$

when, $f = 0.1 f_L$, $|A_{v1}|_{dB} = -20 \log \left(\frac{f_L \times 10}{0.1 f_L} \right) = -20 \text{ dB}.$

when, $f = f_L$ then $A_{v1} = \frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}}$

And, $|A_{v1}|_{dB} = 20 \log \frac{1}{\sqrt{2}} = -10 \log 2 = -10 \times 0.30 = -3 \text{ dB}.$

When, $f \gg f_L$, i.e. in mid-band region $\rightarrow \left(\frac{f_L}{f} \right)^2 \ll 1$

$$A_{v1} = \frac{1}{\sqrt{1 + \left(\frac{f_L}{f} \right)^2}} \approx \frac{1}{\sqrt{1}} \rightarrow 1$$

i.e. $A_{v1} \rightarrow 1$

which is the normalized gain in mid-band frequency region and A in this region,

$$A_{vm} \approx 1$$

$$|A_{vm}|_{dB} = 20 \log 1 = 0 \text{ dB}.$$

When, we plot these quantity on logarithmic scale taking frequency along x-axis and $|A_{v1}|_{dB}$ along y-axis, then we get a curve as shown in fig-2. This curve is called frequency response in low-freq. range.

(4)

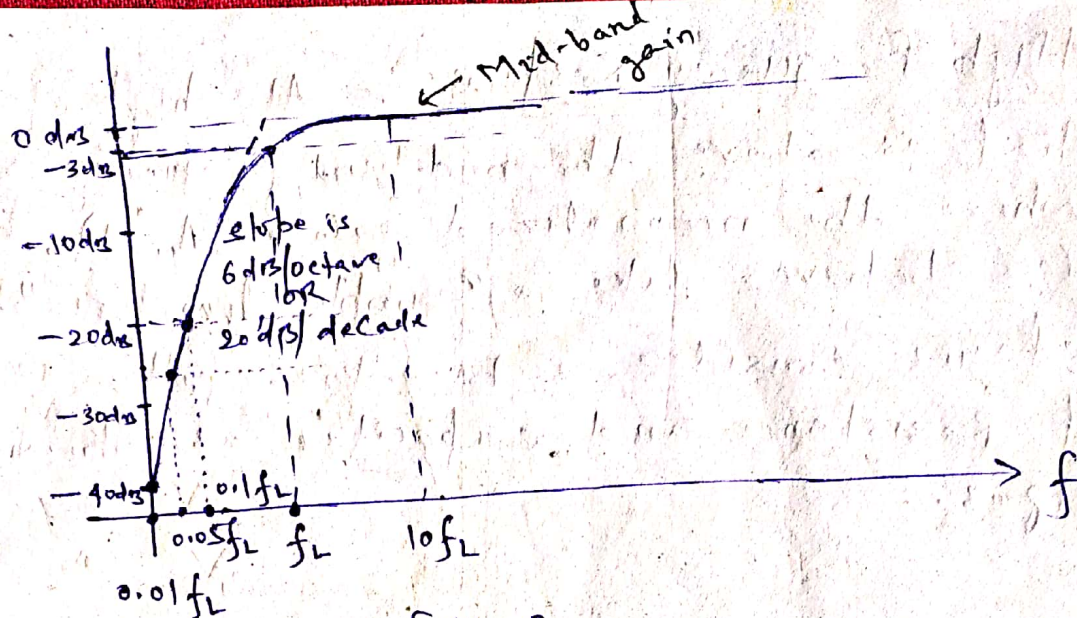


Fig-2

from curve, it is clear that lower cut-off freq. f_L is the frequency at which the gain has fallen, to $\frac{1}{\sqrt{2}}$ times of mid-band gain and corresponding to this frequency gain is -3 dB. This frequency is also known as 3 dB cut-off lower cut-off frequency. It is also obvious, that gain linearly increase and not uniform below the mid-band frequency and above the 3 dB cut-off frequency i.e. in mid-band range frequency response is constant and gain becomes 0 dB.

Note:- i) Here, when we change the frequency by 10 times then gain change by 20 dB. Hence slope is called 20 dB/decade.

ii) If we change the frequency by 2 times then gain changes by 6 dB. Hence it may also be called that slope is 6 dB/octave.