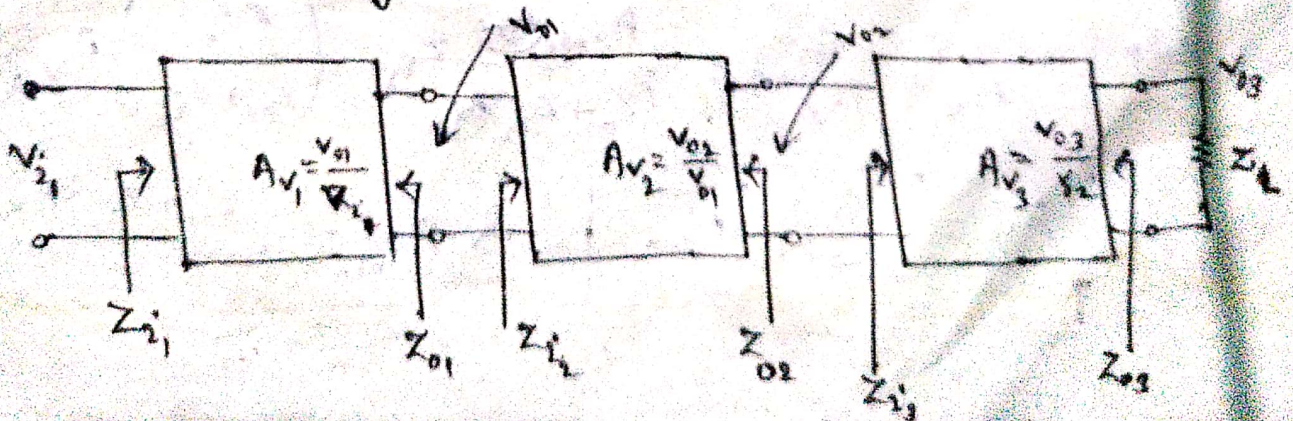



CASCADED SYSTEM

When two or more systems are connected in such a way that the input impedance of succeeding system acts a load to preceding system as shown in fig 1 as below is called cascading.



Cascaded system of effect of source impedance

(2)

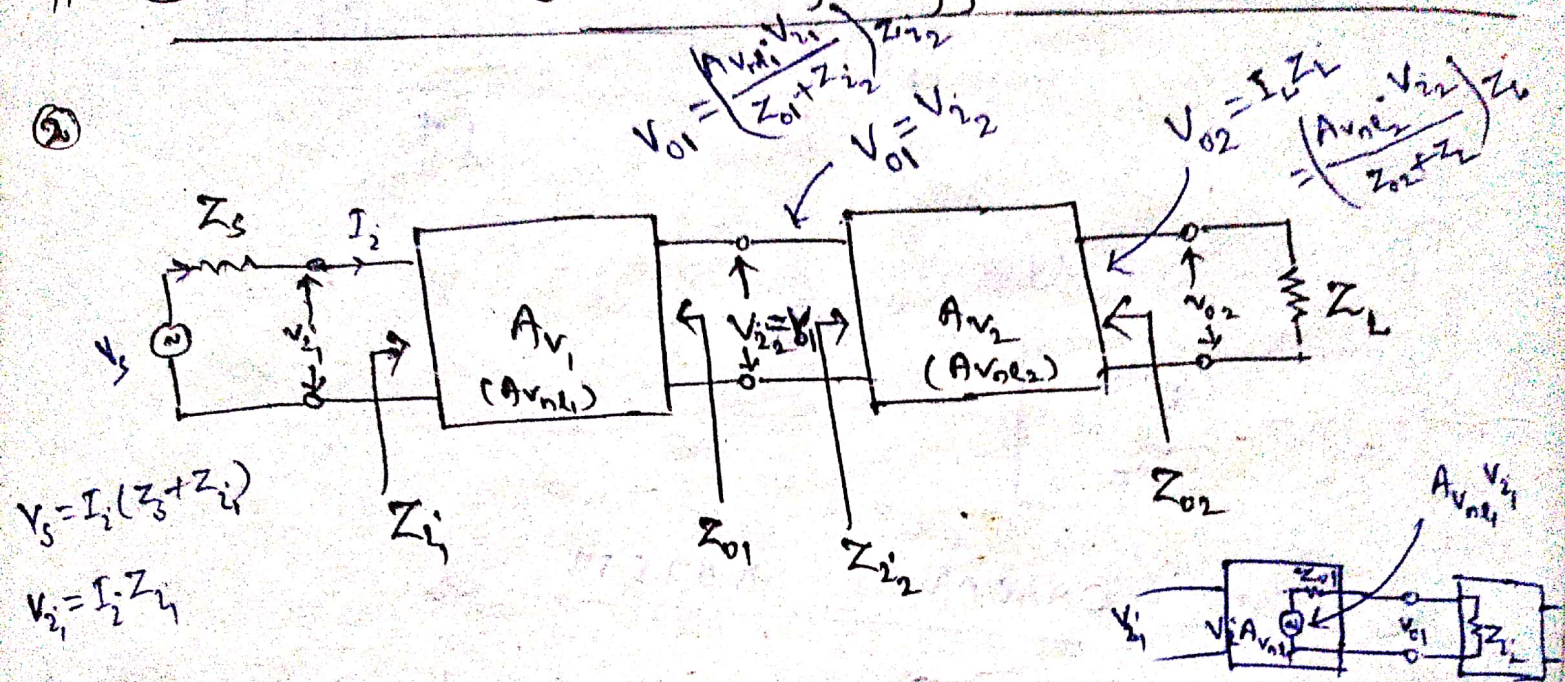

The above fig. shows cascading of two systems with no-load gain A_{vnl1} and A_{vnl2} and loaded gain A_{v1} and A_{v2} .

Now,

$$A_{v1} = \frac{V_{o1}}{V_{i1}} = \frac{A_{vnl1} \cdot V_{i1} \cdot Z_{i2}}{(Z_{o1} + Z_{i2}) \cdot V_{i1}} = \left(\frac{Z_{i2}}{Z_{o1} + Z_{i2}} \right) A_{vnl1}$$

$$\boxed{A_{v1} = \left(\frac{Z_{i2}}{Z_{o1} + Z_{i2}} \right) A_{vnl1}} \Rightarrow A_{vnl1} = \frac{(Z_{o1} + Z_{i2}) A_{v1}}{Z_{i2}} \quad \text{--- (1)}$$

Similarly —

$$A_{V_2} = \frac{V_{o2}}{V_{i2}} = \left(\frac{A_{V_{nl2}} \cdot \cancel{V_{i2}}}{Z_{o2} + Z_L} \right) \cdot Z_L \cdot \frac{1}{\cancel{V_{i2}}} = \left(\frac{Z_L}{Z_L + Z_{o2}} \right) A_{V_{nl2}}$$

$$\boxed{A_{V_2} = \left(\frac{Z_L}{Z_L + Z_{o2}} \right) A_{V_{nl2}}} \Rightarrow A_{V_{nl2}} = \frac{A_{V_2} (Z_L + Z_{o2})}{Z_L}$$

$$\Rightarrow \boxed{A_{V_T} = A_{V_1} \cdot A_{V_2}} \Rightarrow A_{V_T} = \left(\frac{Z_{i2}}{Z_{o1} + Z_{i2}} \right) \left(\frac{Z_L}{Z_L + Z_{o2}} \right) A_{V_{nl1}} \cdot A_{V_{nl2}}$$

$$\Rightarrow \boxed{A_{V_T} = \left(\frac{Z_{i2}}{Z_{i2} + Z_{o1}} \right) \left(\frac{Z_L}{Z_L + Z_{o2}} \right) A_{V_{nl1}} \cdot A_{V_{nl2}}} = A_{V_1} \left(\frac{Z_L}{Z_L + Z_{o2}} \right) A_{V_{nl1}}$$

Now, when effect of source is considered.

$$A_{V_2} = \frac{V_{o2}}{V_s} = \frac{A_{V_{nl2}} V_{i2}}{(Z_{o2} + Z_L)} \cdot Z_L \cdot \frac{1}{V_s} = \left(\frac{Z_L}{Z_L + Z_{o2}} \right) \frac{V_{i2}}{V_s} \cdot A_{V_{nl2}}$$

$$= \left\{ \left(\frac{Z_L}{Z_L + Z_{o2}} \right) A_{V_{nl2}} \right\} \cdot \frac{A_{V_{nl1}} \cdot V_{i1}}{Z_{o1} + Z_{i2}} \cdot Z_{i2} \cdot \frac{1}{V_s}$$

$$= A_{V_2} \cdot \left\{ \frac{A_{V_{nl1}} Z_{i2}}{Z_{i2} + Z_{o1}} \right\} \cdot \frac{V_{i1}}{V_s} \quad [\text{from eq ①}]$$

$$= A_{V_2} \cdot A_{V_1} \frac{Z_i(Z_{i1})}{Z_i(Z_{i1} + Z_s)} = A_{V_1} \cdot A_{V_2} \left(\frac{Z_{i1}}{Z_{i1} + Z_s} \right)$$

$$\Rightarrow \boxed{A_{V_2} = A_{V_T} \left(\frac{Z_{i1}}{Z_{i1} + Z_s} \right)}$$

$$\begin{aligned} V_{i1} &= I_{i1} Z_{i1} \\ V_s &= I_{i1} (Z_{i1} + Z_s) \end{aligned}$$

Current gain is given by —

$$A_{i_T} = -A_{V_T} \left(\frac{Z_{i1}}{Z_L} \right)$$

CASCADE CONNECTION

When two transistors are connected in different configuration, then this obtained connection is termed as cascade connection. The fig-1 and fig-2 represents cascade connection where leading transistor is in CE configuration and following transistor is in CB configuration.

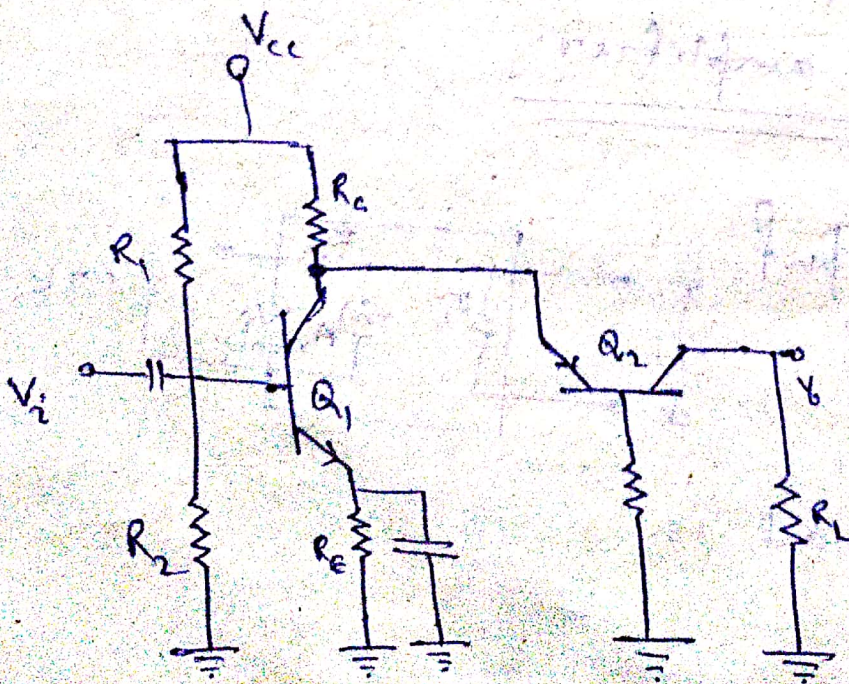


Fig-1.

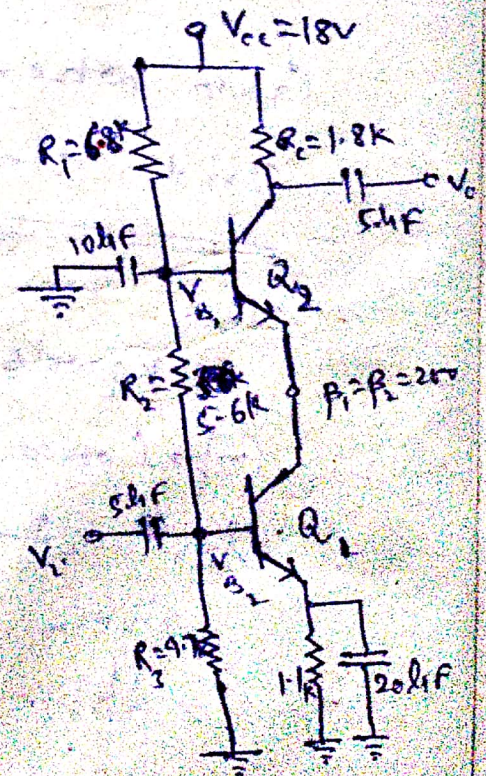


Fig-2

⑤ The biasing analysis of cascade amplifier is fig-2

It is clear that, input signal is applied to transistor Q_2 and base of Q_1 is grounded and output is taken betⁿ collector of Q_1 and ground. Hence, fig-2 consist of Q_1 leading leading by Q_2 .

for dc biasing analysis —

for Q_1 —

$$R_{Th1} = \frac{5.6 \times 10.5}{17.1} \approx 3.766 \approx \frac{12.4 \times 4.7}{17.1} \approx 3.41K$$

$$V_{Th1} = \frac{18}{17.1} \times 4.7$$

$$\approx 4.947 \text{ volt}$$

Applying KVL — to Q_1

$$V_{Th1} = I_b R_{Th1} + 0.7 + I_e R_e$$

$$\text{or } 4.947 - 0.7 = I_b R_{Th1} + (\beta + 1) I_b R_e$$


$$\text{or } I_b = \frac{4.247}{R_{Th1} + (\beta + 1) R_e}$$

$$I_b = \frac{4.294}{3.41 + 201 \times 1.1} = 0.018942 \text{ mA}$$


$$I_e = (\beta + 1) I_b \approx 3.80 \text{ mA}$$

$$V_{B1} = V_{Th1} - I_b R_{Th1} = 4.947 - 0.018942 \times 3.41 = 4.88 \approx 4.9 \text{ volt}$$

$$I_{E1} \approx I_e = 3.8 \text{ mA}$$

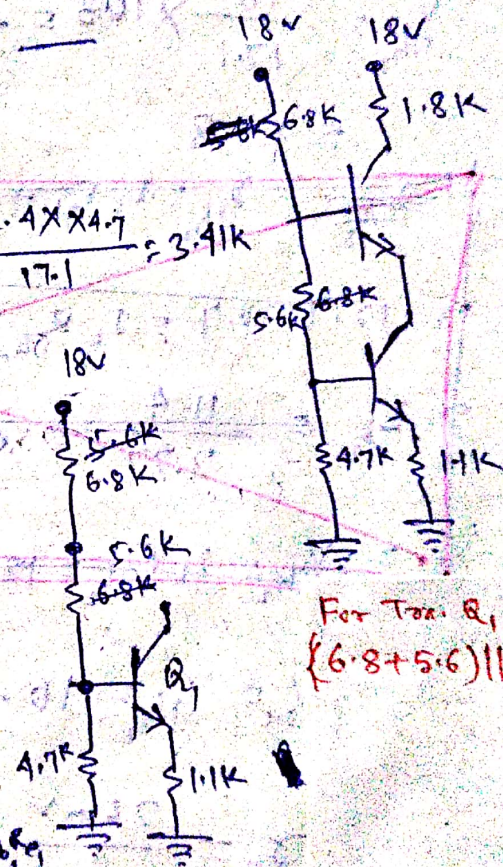

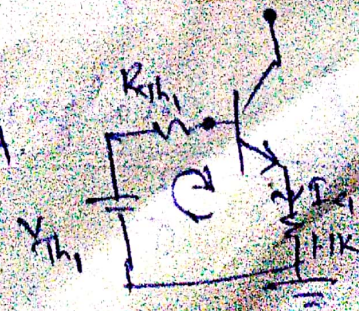For $T_{eq} Q_1$,
 $\{6.8 + 5.6\} \parallel 4.7 \Omega$



(6)

from cascade connection (Trans, Q_2)



$$I_{E2} = I_{E1} = 3.8 \text{ mA}$$

for transistor Q_2

$$R_{Th2} = \frac{6.8 \times 10^3}{17.1} = 3.786 \text{ k}\Omega$$

$$V_{Th2} = \frac{18}{17.1} \times 10^3 = 10.526 \text{ V}$$

$$= 10.8$$

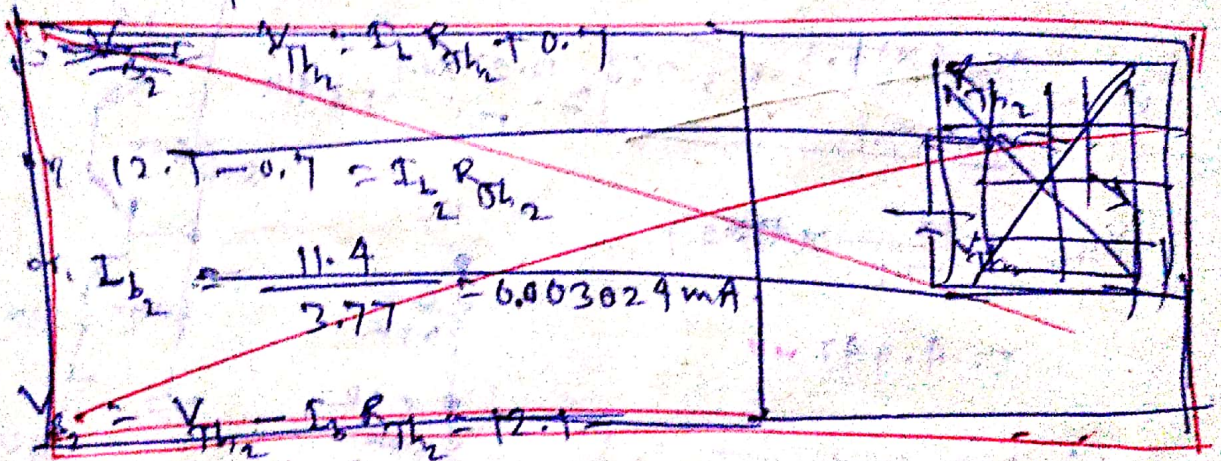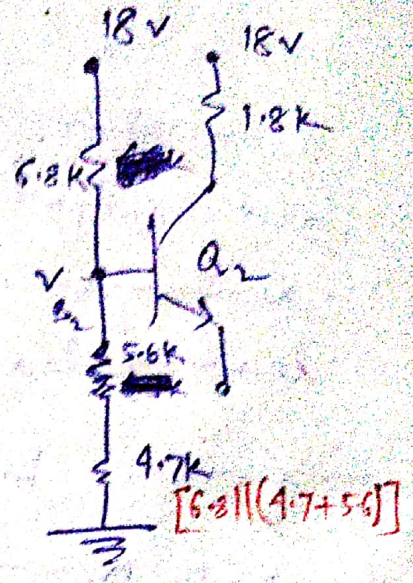


$$V_{B2} = V_{BE} = V_{Th2} = 10.8 \text{ volt.}$$

Now, $r_{e1} = \frac{26 \text{ mV}}{I_{E1}} = \frac{26}{3.8} = 6.8 \Omega$

$$r_{e2} = \frac{26 \text{ mV}}{I_{E2}} = \frac{26}{3.8} = 6.8 \Omega$$

A.C analysis

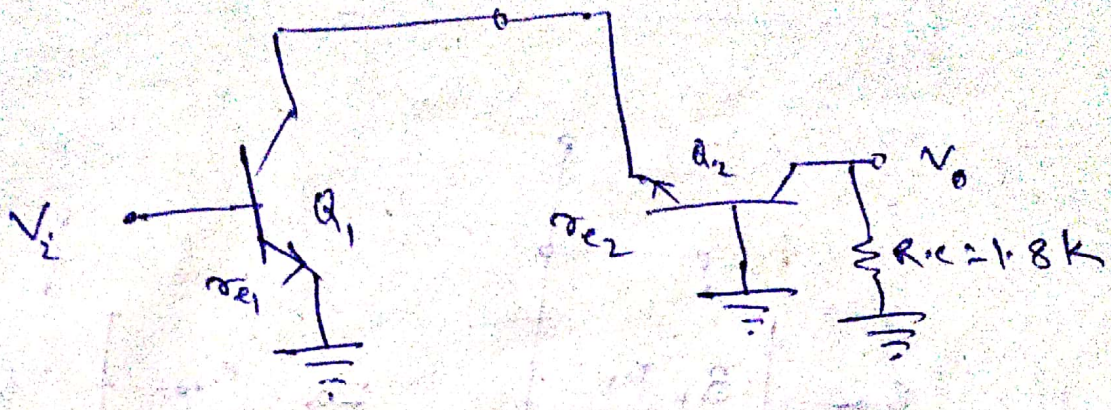In a.c analysis, all d.c components are considered as effect-less, or assumed to be removed.



Here, loading of Q_1 is dynamic resistance r_{e2} of Q_2 .

$$\therefore A_{V_{ol1}} = -\frac{R_c}{r_{e1}} = -\frac{r_{e2}}{r_{e1}} = -1, \text{ [-ve for CE]}$$

Again,

Loading of Q_2 is $R_c = 1.8 \text{ k}$.

$$\begin{aligned} \therefore A_{V_{ol2}} &= +\frac{R_c}{r_{e2}} \text{ [+ve for CB]} \\ &= \frac{1.8 \times 10^3}{6.8} = 264.7 \end{aligned}$$

$\therefore$ Over-all no-load gain,

$$A_{V_{\text{Total}}} = A_{V_{ol1}} \cdot A_{V_{ol2}} = -264.7 \quad \text{Ans.}$$