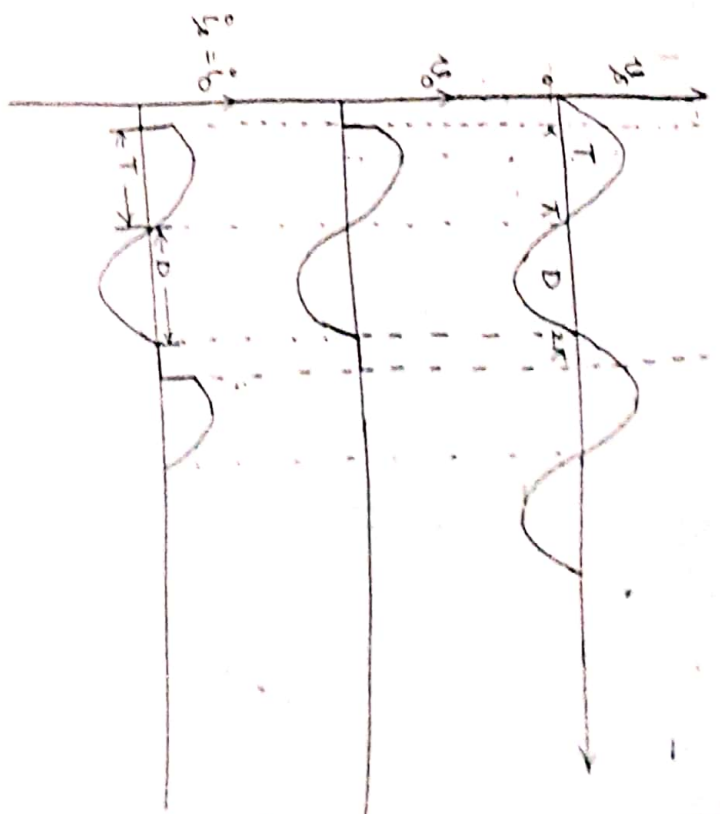


1990

 ~~$f = \text{const}$~~

Types
1. phase controlled regulators

- ## Phase Controlled Rectifier

$$1 + \frac{V_m}{2\pi R} [\cos \alpha - 1] = \frac{V_0}{R}$$


$$V_0 = \frac{1}{2\pi} \int_0^{2\pi} V_m \sin \omega t \, d(\omega t)$$

$$= \frac{V_m}{2\pi} [\cos\phi - 1]$$

$$I_{\text{sc}} = I_0 = \frac{V_0}{R} = \frac{V_m}{2R} [\cos \alpha - 1]$$

Here, the source current contains the DC component & saturates the supply. Hence, it is not generally preferred for applications.

$$V_{or}^2 = \frac{1}{2\pi} \int_{\alpha}^{2\pi} V_m^2 \sin^2 \omega t \cdot d(\omega t)$$

$$= \frac{V_m^2}{2\pi} \left[\int_{\alpha}^{2\pi} \frac{1 - \cos 2\omega t}{2} d(\omega t) \right]$$

$$= \frac{V_m^2}{4\pi} \left[2\pi - \alpha + \frac{1}{2} (\sin 2\alpha - 0) \right]$$

$$V_{or} = \frac{V_m}{2\sqrt{\pi}} \left[(2\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

$$P_{in} = V_{sr} I_{sr} \cos \phi$$


$$P_{out} = V_{or} I_{or}$$

$$P_{in} \approx P_{out}$$


$$\Rightarrow \cos \phi = \frac{V_{or} I_{or}}{V_{sr} I_{sr}} = \frac{V_{or}}{V_{sr}}$$

$$\Rightarrow \cos \phi = \frac{1}{\sqrt{2\pi}} \left[\sqrt{(2\pi - \alpha) + \frac{1}{2} \sin 2\alpha} \right] \quad (IPF)$$

2. 1- ϕ Full controlled regulator:

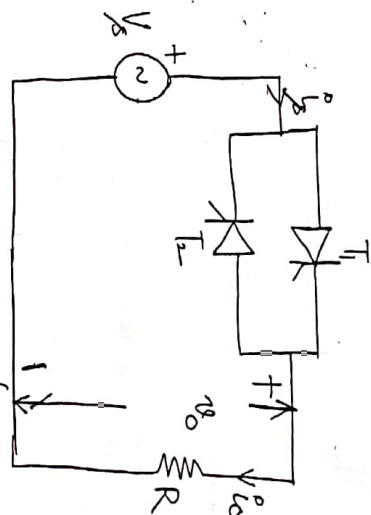

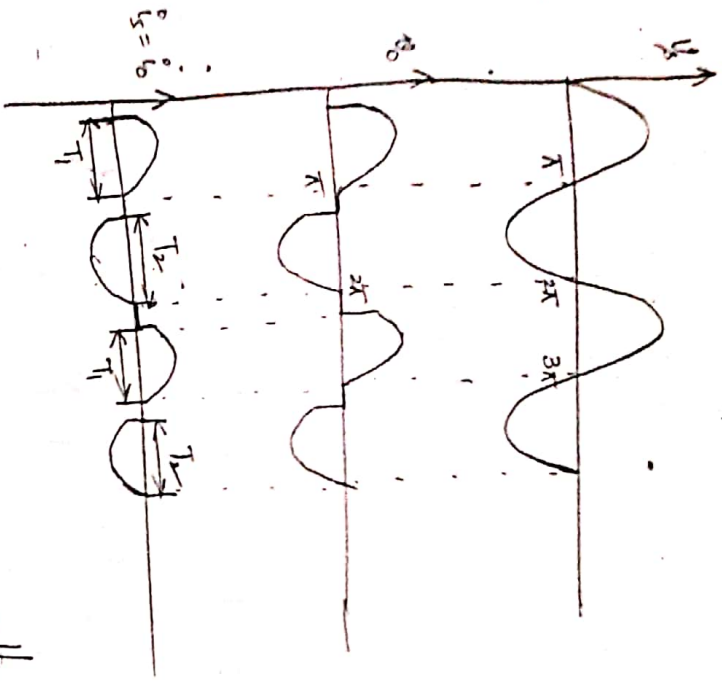I_{10} FB in +ve cycle $\rightarrow I_g(\alpha, 2\pi+\alpha, \dots)$
 I_{10} FB in -ve cycle $\rightarrow I_g(\pi+\alpha, 3\pi+\alpha, \dots)$



$$V_{or} = \left[\frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \, d(\omega t) \right]^{1/2}$$

$$= \frac{V_m}{\sqrt{2\pi}} \int_{\alpha}^{\pi} \sqrt{1 - \alpha + \frac{1}{2} \sin 2\alpha} \, d\alpha$$

$$\Rightarrow \cos \phi = \frac{V_o}{V_{or}}$$

$$= \frac{1}{\sqrt{\pi}} \sqrt{1 - \alpha + \frac{1}{2} \sin 2\alpha}$$

① RL Load

$$\text{Case: } \alpha > \phi \quad I_o \text{ lags } V_o \text{ by } \tan^{-1}\left(\frac{\omega L}{R}\right)$$


$$\text{i.e., } \phi = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

Here, α should be greater than ϕ for V_g control in the o/p

$$V_{or}^2 = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \, d(\omega t)$$

$$= \frac{V_m^2}{2\pi} \left[\pi - \alpha + \frac{1}{2} (\sin 2\alpha - \sin 2\pi) \right]$$
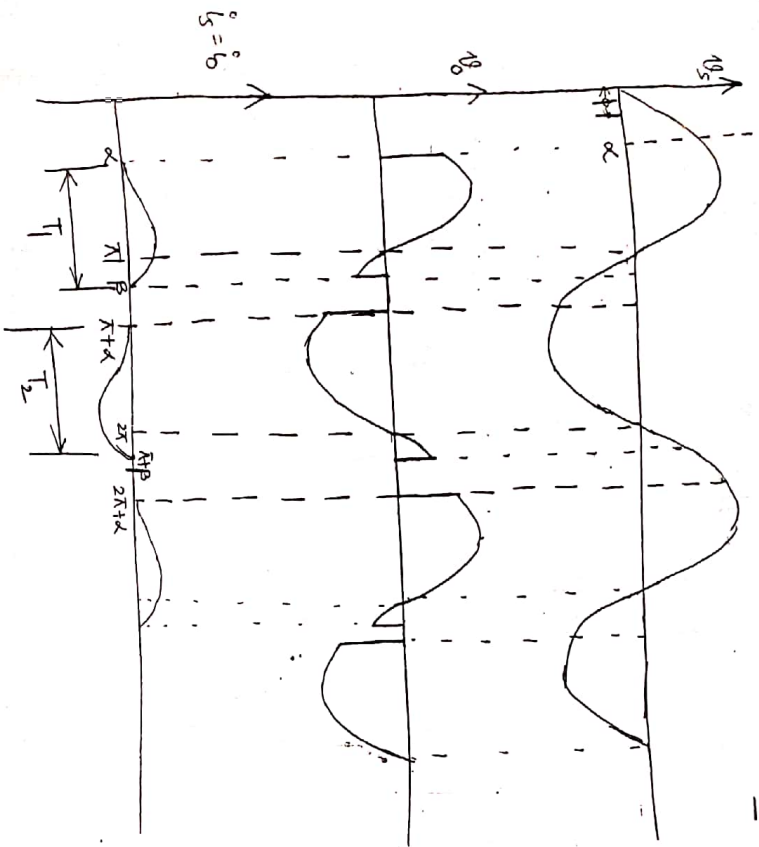
$$\Rightarrow V_{or} = \frac{V_m}{\sqrt{2\pi}} \left[(\pi - \alpha) + \frac{1}{2} (\sin 2\alpha - \sin 2\pi) \right]^{1/2}$$



$$PF = \frac{V_{or}}{V_s}$$

$$= \frac{1}{\pi \alpha} \int_{\alpha}^{\pi} [(B - \alpha) + \frac{1}{2} (\sin x - \sin \pi)] dx$$


Case 2: $\alpha \leq \phi$ (Continuous Conduction)
 By increasing inductance, ϕ increases
 & B also increases.

when $\alpha \leq \phi$, $B \rightarrow \pi + \alpha$.

Hence, $V_o = V_s$

Thyristors conduct for π radians each
 & conduct of voltage is lost

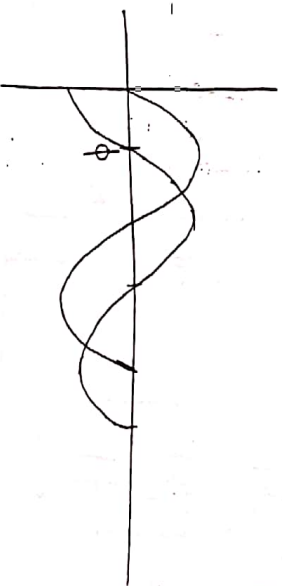(If the gate pulse high freq.
 pulse gating is provided)




$$V_{or} = V_s \quad ; \quad I_{or} = \frac{V_{or}}{|Z|} = \frac{V_{or}}{\sqrt{R^2 + (\omega L)^2}}$$


* α should be greater than ϕ for getting V_g control.

→ Here, in AC V_g regulators, we can replace the two antiparallel SCRs by a TRIAC for resistive loads. But, for inductive loads, it is not preferred.

Two stage Regulators:

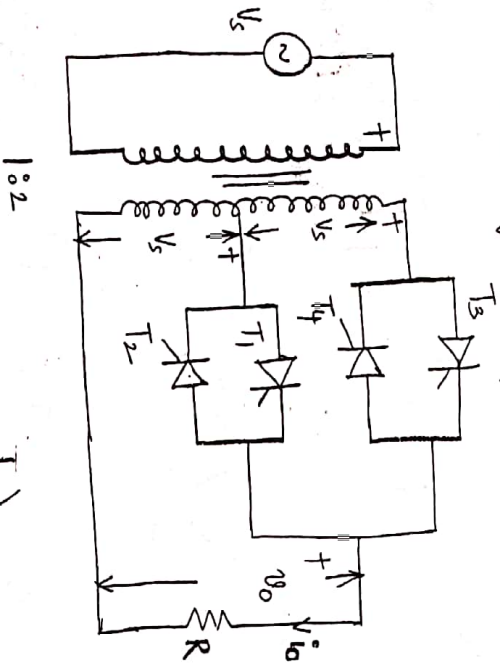

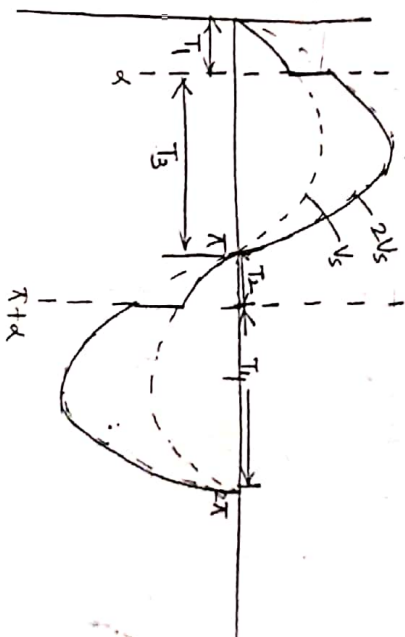T_1, T_3 FB for +ve cycle
 T_2, T_4 FB for -ve half cycle.



$T_1 \rightarrow 0^\circ$
 $T_3 \rightarrow \alpha$
 $T_2 \rightarrow \pi$
 $T_4 \rightarrow \pi + \alpha$

$$V_{or}^2 = \frac{1}{\pi} \left[\int_0^\pi V_m^2 \sin^2 \omega t d(\omega t) + \int_\pi^{2\pi} 4V_m^2 \sin^2 \omega t d(\omega t) \right]$$

$$= \frac{1}{\pi} \left[V_m^2 \int_0^\pi \frac{1 - \cos 2\omega t}{2} d(\omega t) + 4V_m^2 \int_\pi^{2\pi} \frac{1 - \cos 2\omega t}{2} d(\omega t) \right]$$

$$= \frac{V_m}{2\pi} \left[(\alpha - 0) - \frac{1}{2} \sin 2\alpha + 4 \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right] \right]$$

$$\Rightarrow V_{or} = \frac{V_m}{\sqrt{2\pi}} \left\{ \left(\alpha - \frac{1}{2} \sin 2\alpha \right) + 4 \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right] \right\}^{1/2}$$

$$(I_{T1})_{rms} = \sqrt{\frac{1}{2\pi} \left[\int_0^\pi \frac{V_m^2 \sin^2 \omega t}{R^2} d(\omega t) \right]}$$

$$= \sqrt{\frac{V_m^2}{4\pi R^2} \left[(\alpha - 0) - \frac{1}{2} \sin 2\alpha \right]}$$

$$= \frac{V_m}{2\sqrt{\pi} R} \left[\alpha - \frac{1}{2} \sin 2\alpha \right]$$


$$= (I_{T2})_{rms}$$

$$I_{bf} = (I_{T2})_{rms} = \frac{(2V_m)}{\sqrt{2\pi} \cdot 2\sqrt{\pi} \cdot R} \int (\pi - \alpha) - \frac{1}{2} \sin 2\alpha$$


$$= \frac{2V_m}{2\sqrt{\pi} \cdot R} \int \left(\pi - \alpha + \frac{1}{2} \sin 2\alpha \right)$$

$$= \frac{V_m}{\sqrt{\pi} \cdot R} \int \left(\pi - \alpha + \frac{1}{2} \sin 2\alpha \right)$$


$$= (I_{T4})_{rms}$$

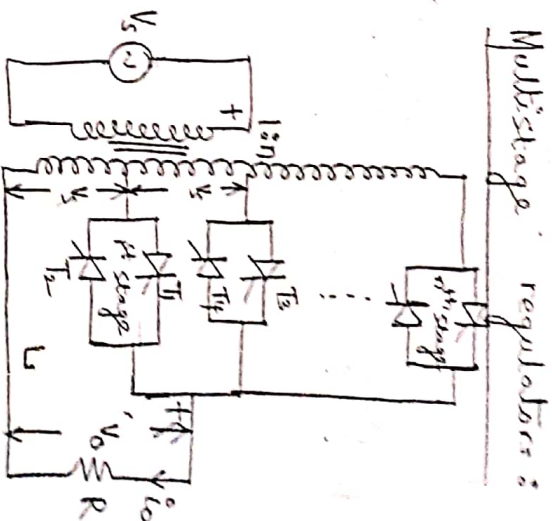

cycle
Integral control: (ON/OFF control)

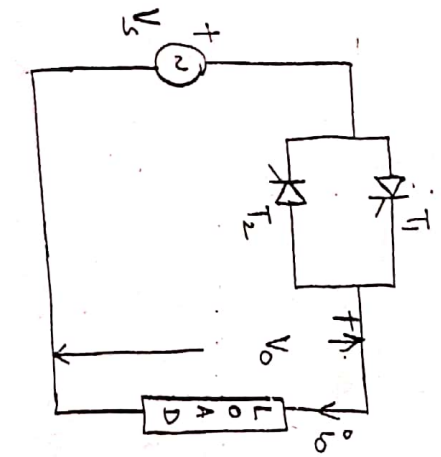

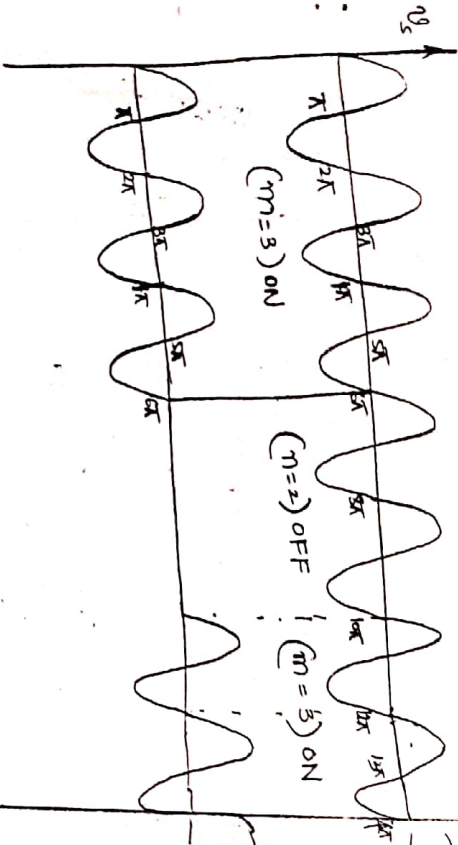m cycles $\rightarrow$ ON
 n cycles $\rightarrow$ OFF



T_1 FB (+ve cycles)
 T_2 FB (-ve cycles)

$m=3$ $T_1 \rightarrow$ FB (+ve cycle)

$\Rightarrow I_g (0, 2\pi, 4\pi, \dots)$
($m=3$)

~~$5\pi, 8\pi$~~
($n=2$)

$10\pi, 12\pi, 14\pi$

$(m'=3)$

~~$16\pi, 18\pi$~~
($n=2$)

$(n=2)$



FB (-ve cycle)

$\Rightarrow I_g (\pi, 3\pi, 5\pi, \dots)$
($m=3$)

~~9π~~
($n=2$)

$11\pi, 13\pi, 15\pi, \dots$

($m=3$)

~~$17\pi, 19\pi$~~

~~X~~

($n=2$)

$$K = \frac{m}{m+n}$$

$$V_{or} = \sqrt{K} \cdot V_{sr}$$

$$pf = \frac{V_{or}}{V_{sr}}$$

$$pf = \sqrt{k}$$

Applications:

It can be used in all applications where mech. time constant is high. For example, for rotating AC machines, it can be used for Very large size Const. associated with high mechanical time moment of inertia.

Limitation of Integral cycle control:

The range of control is limited $\therefore$ we can't increase the value of n to a very high value.

In integral cycle control, the harmonic problem in the ofp v_g & current waveform are very much reduced.