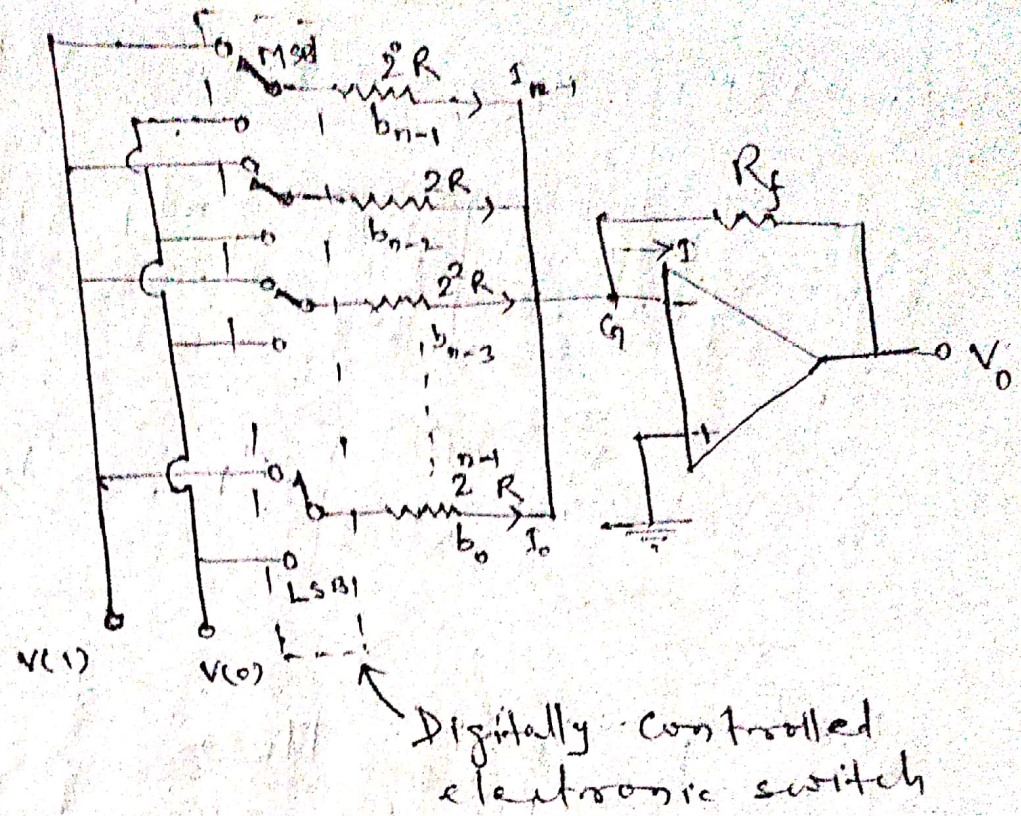


There are various type of D/A converter. Some of them are following—

- 1) Weighted-Resistor D/A.
- 2) R-2R ladder type
- 3) Voltage mode R-2R ladder type
- 4) Inverted or Current mode R-2R ladder type

1) Weighted Resistor D/A Converter :-

Let, us consider n -bit straight binary input to a resistor network which produces current I corresponding to logic 1 at MSB of n -bit binary, $\frac{I}{2}$ corresponding to logic 1 at next lower bit from MSB, $\frac{I}{2^2}$ corresponding to logic 1 at next lower^{bit}, and so on. Finally produces current $\frac{I}{2^{n-1}}$ corresponding to logic 1 at LSB. Thus, we see that total current, thus produced, is proportional to digital input. This current can be converted into a corresponding voltage by using op-amp functioning as current to voltage converter which is proportional to digital input. Such a circuit is shown in fig-4. This ckt is referred to as weighted-resistor D/A converter because ~~the~~ the value of resistors are weighted in accordance to binary weights.



Here a digitally controlled switch is used. A voltage $V(1)$ is applied to op-amp inverting terminal when switch logic is at 1 and $V(0)=0$ is applied which switch logic is 0.

Now,

$$I = I_{n-1} + I_{n-2} + I_{n-3} + \dots + I_0$$

$$I = I_{n-1} b_{n-1} + I_{n-2} b_{n-2} + I_{n-3} b_{n-3} + \dots + I_0 b_0$$

$$\therefore \frac{0 - V_o}{R_f} = \frac{V(1) - 0}{R} b_{n-1} + \frac{V(1) - 0}{2R} b_{n-2} + \frac{V(1) - 0}{2^2 R} b_{n-3} + \dots + \frac{V(1) - 0}{2^{n-1} R} b_0$$

$$\therefore -\frac{V_o}{R_f} = \frac{V(1)}{R} \left[b_{n-1} + \frac{b_{n-2}}{2} + \frac{b_{n-3}}{2^2} + \dots + \frac{b_0}{2^{n-1}} \right]$$

$$= \frac{V(1)}{R} \cdot \frac{1}{2^{n-1}} \left[2^{n-1} b_{n-1} + 2^{n-2} b_{n-2} + 2^{n-3} b_{n-3} + \dots + 2^0 b_0 \right]$$

If $V(1) = -V_R = \text{Reference Voltage then}$

$$V_0 = -\frac{R_f}{R} \left(\frac{-V_R}{2^{n-1}} \right) \left[2^{n-1} b_{n-1} + 2^{n-2} b_{n-2} + \dots + 2^0 b_0 \right]$$

$$\Rightarrow \boxed{V_0 = \frac{V_R}{2^{n-1}} \cdot \frac{R_f}{R} \left[2^{n-1} b_{n-1} + 2^{n-2} b_{n-2} + \dots + 2^0 b_0 \right]}$$

Let, $K = \frac{V_R R_f}{R \cdot 2^{n-1}}$ then

$$V_0 = K \left(2^{n-1} b_{n-1} + 2^{n-2} b_{n-2} + \dots + 2^0 b_0 \right)$$

i.e. Analog output = $K \times \text{Digital input}$

R-2R Ladder type D/A Converter

A weighted-resistor D/A converter for designing high binary bit D/A converter, we need wide range of resistor (as multiple of 2^n) which is in practice not a convenient process. For, this or to avoid this problem, we design R-2R ladder type D/A converter. R-2R ladder type D/A converter uses only two types of resistor as R and 2R which is most suited for integrated circuit (IC) fabrication.


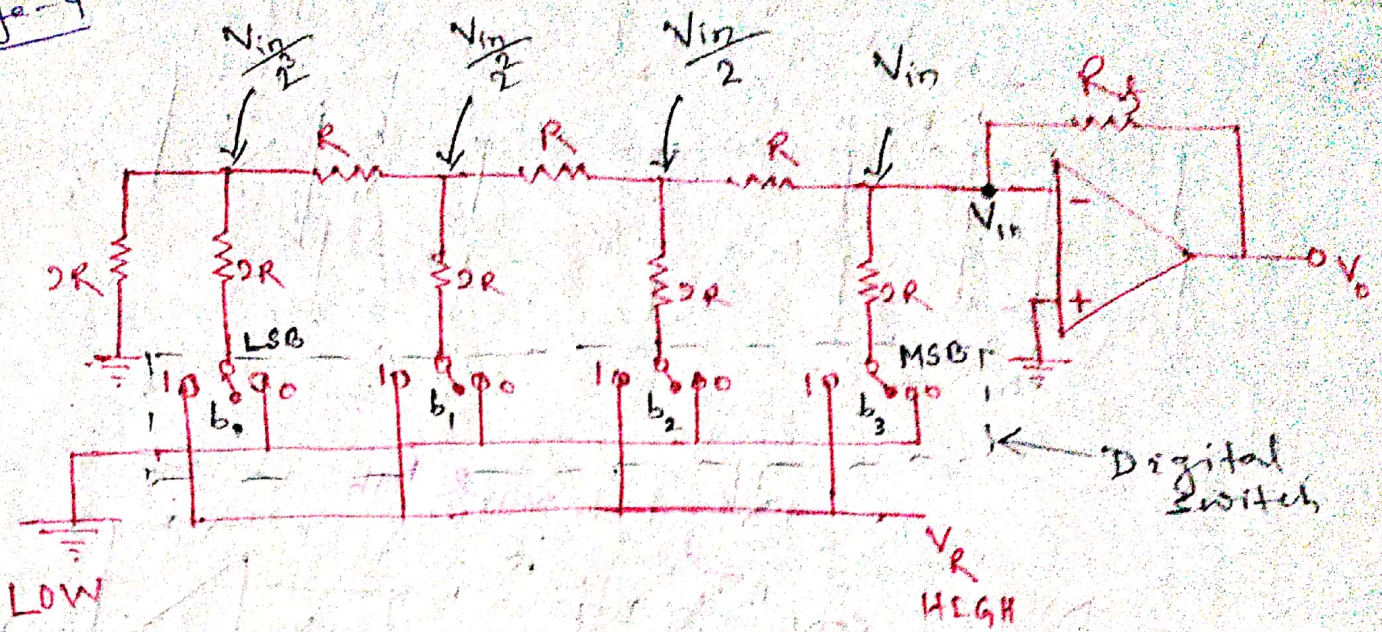
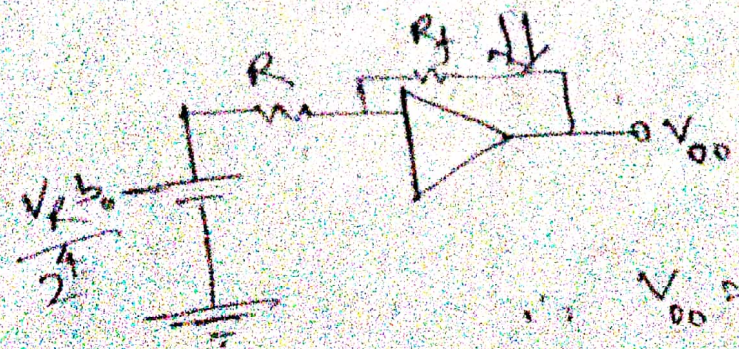
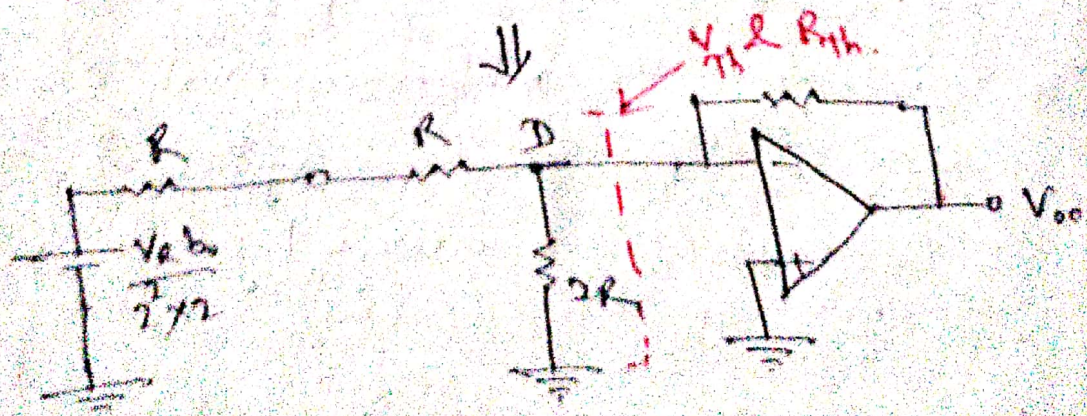
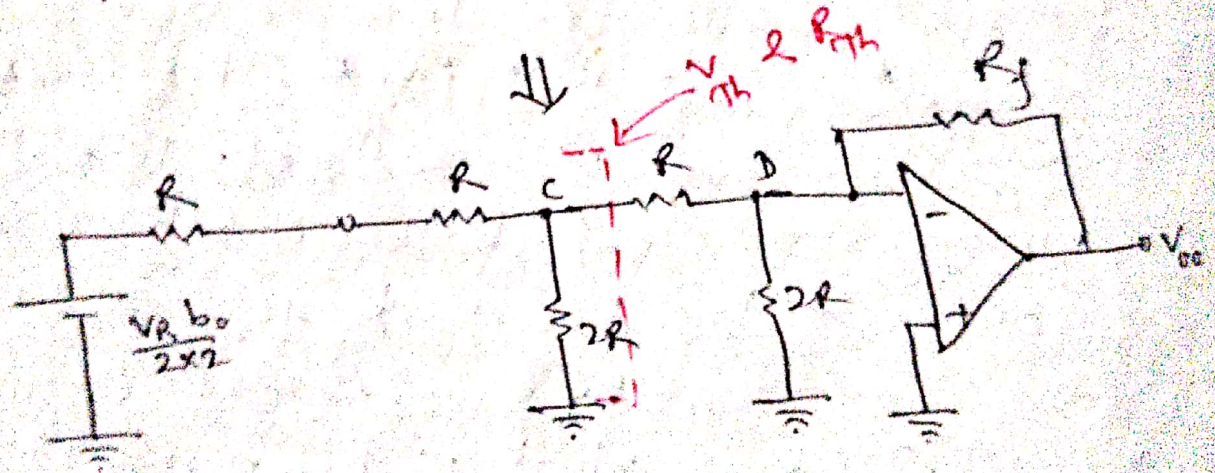
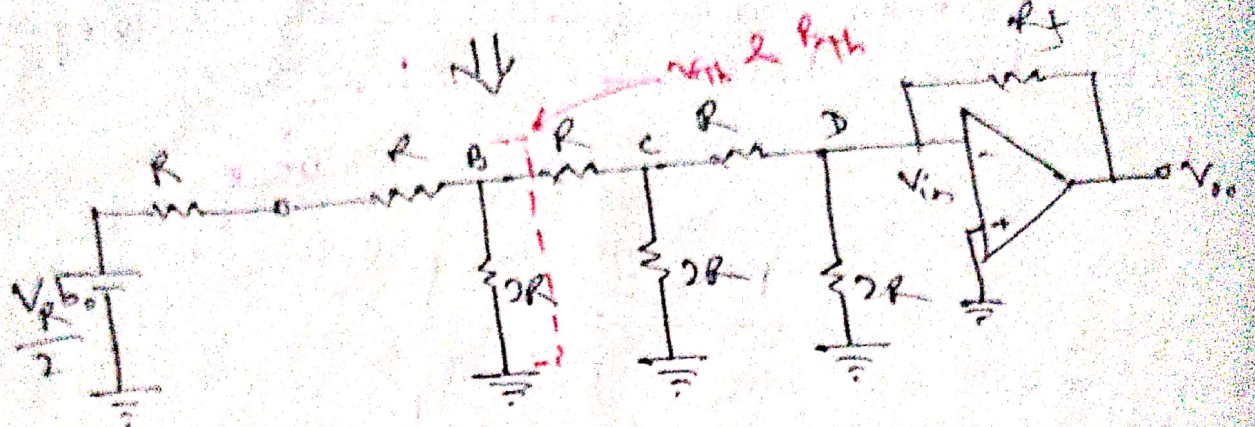


Fig-1.

A 4-bit R-2R ladder type D/A converter is shown in fig-1. Here four binary bits are b_3, b_2, b_1, b_0 in which b_3 is MSB and b_0 is LSB. In this condition, the output voltage is weighted sum of digital inputs which is performed by an operational amplifier with feedback resistor R_f . The analysis can be done in better way by following cases.

Case:-I. Let, $b_3, b_2, b_1, b_0 = 0001$.




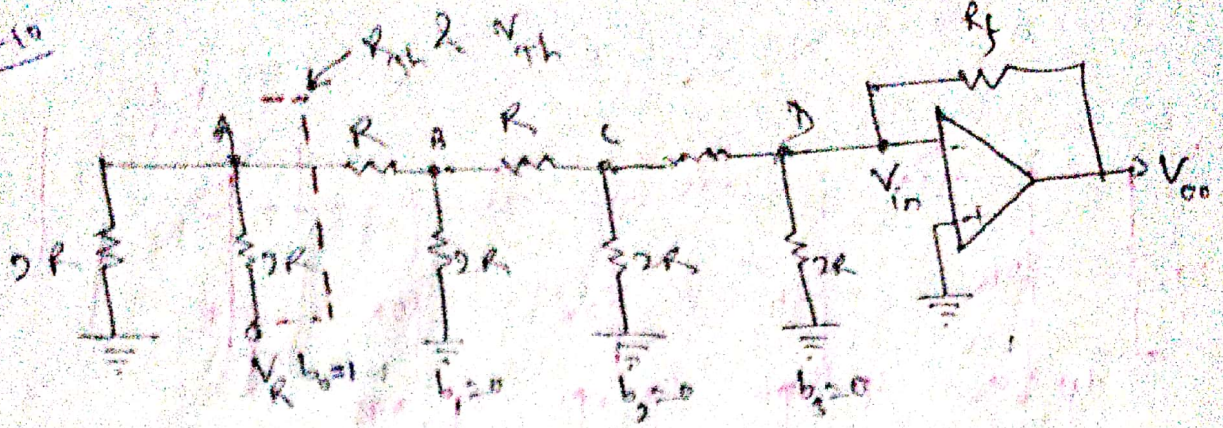
i.e. A reference voltage is applied only to the LSB bit b_0 . In this case, the ckt can be modified as in fig-2.



$$V_{00} = - \frac{R_f}{R} \cdot \frac{V_{Rb0}}{4}$$

Case:- II

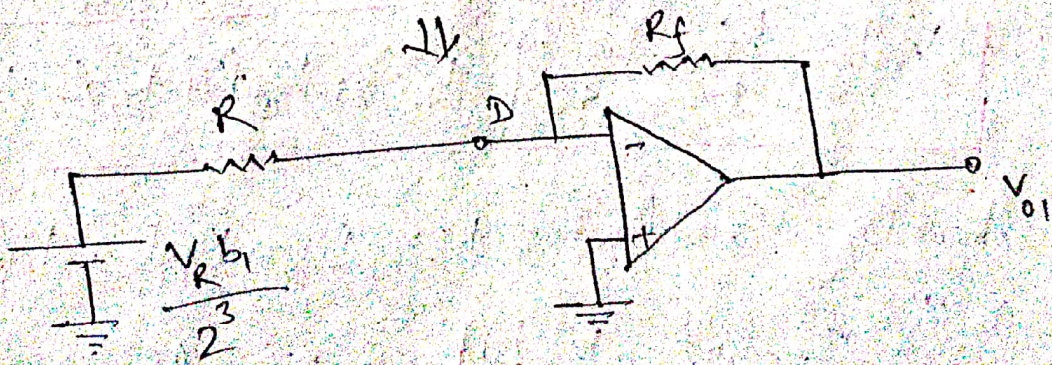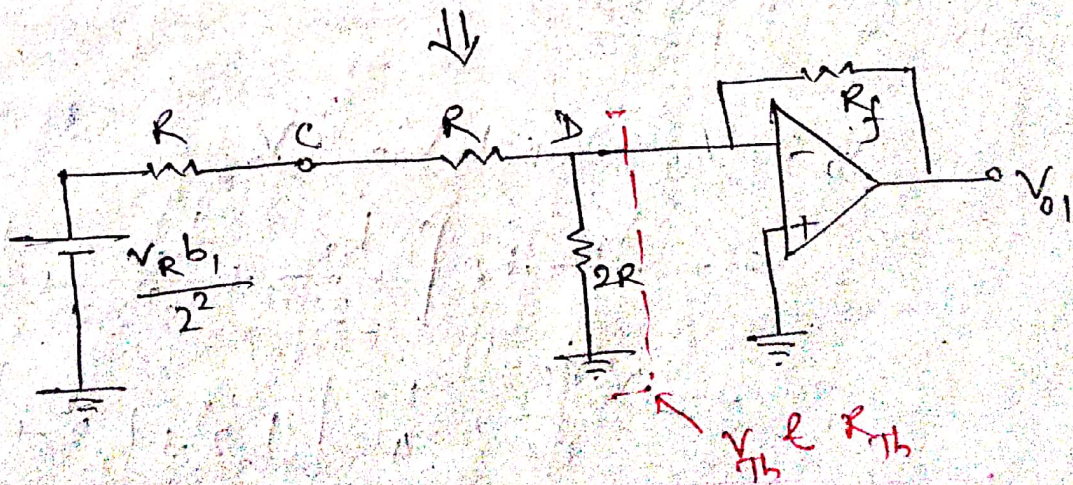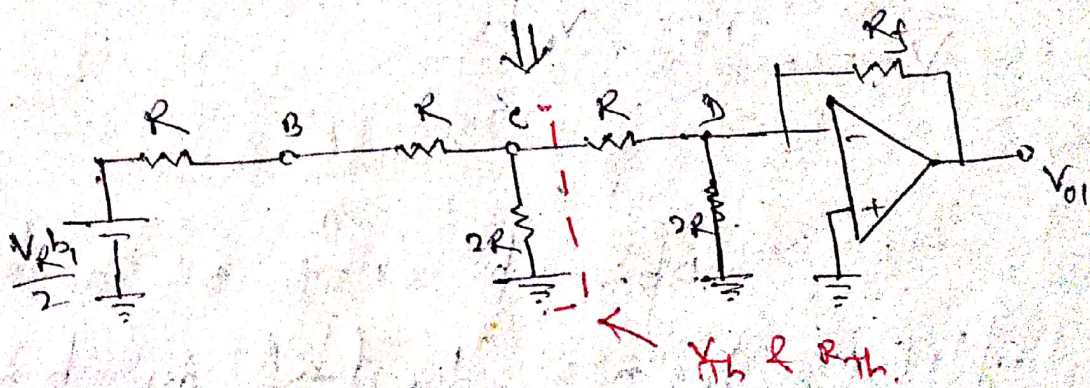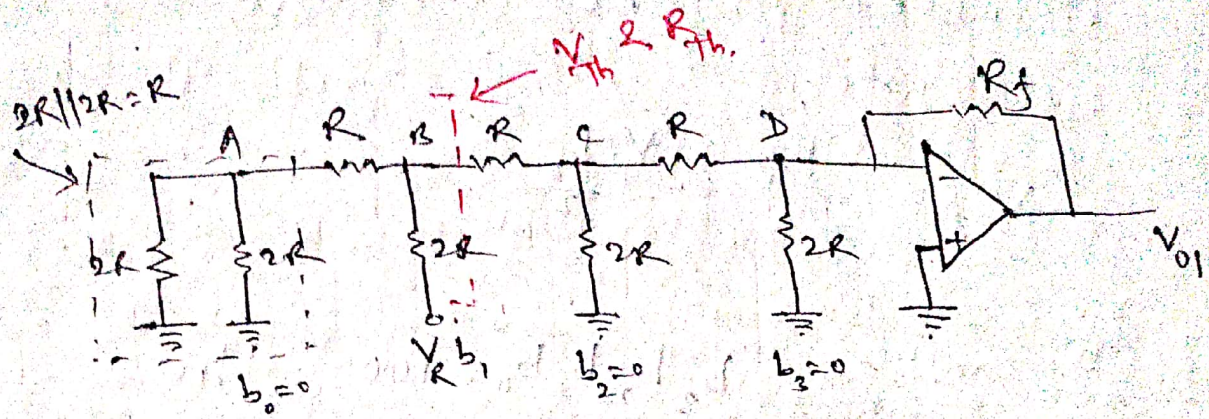When, $b_3 b_2 b_1 b_0 = 0010$ then ckt becomes _____



$$\therefore V_{O1} = - \frac{R_f}{R} \cdot \frac{V_R b_1}{2^3}$$

Case: - III. When, $b_3 b_2 b_1 b_0 = 0100$, then as discussed in case-I & II, We can calculate,

$$V_{02} = -\frac{R_f}{R} \cdot \frac{V_R b_2}{2^2}$$

Case: - IV. When, $b_3 b_2 b_1 b_0 = 1000$ then

$$V_{03} = -\frac{R_f}{R} \cdot \frac{V_R b_3}{2}$$

Since op-amp acts as here summing amplifier, hence total output is given by —

$$V_0 = V_{00} + V_{01} + V_{02} + V_{03}$$

$$= -\frac{V_R}{R} \cdot R_f \left[\frac{b_3}{2} + \frac{b_2}{2^2} + \frac{b_1}{2^3} + \frac{b_0}{2^4} \right]$$

$$= -\frac{V_R R_f}{R} \cdot \frac{1}{2^4} \left[b_3 2^3 + b_2 2^2 + b_1 2^1 + b_0 2^0 \right]$$

$$\therefore |V_0| = \frac{R_f}{R} \cdot \frac{V_R}{2^4} \left[b_3 2^3 + b_2 2^2 + b_1 2^1 + b_0 2^0 \right]$$

Analog output = $k \times$ Digital input.

Similarly, for n -bit R - $2R$ ladder type D/A converter, we can show that

$$V_0 = \frac{R_f}{R} \cdot \frac{V_R}{2^n} \left[b_{n-1} 2^{n-1} + b_{n-2} 2^{n-2} + \dots + b_0 2^0 \right]$$

$$V_o = \frac{R_f}{R} \cdot \frac{V_R}{2^n} \left[b_{n-1} 2^{n-1} + b_{n-2} 2^{n-2} + \dots + b_0 2^0 \right]$$

if $R_f = R$ then

$$V_o = \frac{b_{n-1} 2^{n-1} + b_{n-2} 2^{n-2} + \dots + b_1 2 + b_0 2^0}{2^n} \times V_R$$

The Resolution of R-2R ladder type D/A converter is given by—

$$\text{Resolution} \quad \boxed{1 = \frac{V_o}{R_f} = \frac{1}{2^n} \cdot \frac{V_R}{R}}$$

$$\text{Resolution } V = \frac{1}{2^n} \cdot \frac{R_f}{R} \times V_R$$

if $R = R_f$ then—

$$\boxed{\text{Resolution} = \frac{1}{2^n} \times V_R}$$

Note:- For non-inverting op. amp configuration—

$$V_o = \frac{V_R}{2^n} \left(1 + \frac{R_f}{R_1} \right) \left[b_{n-1} 2^{n-1} + b_{n-2} 2^{n-2} + \dots + b_0 2^0 \right]$$