 


FET (Field Effect transistor)

FET is a three terminal unipolar semiconductor device, in which the current is controlled by an electric field. Basically there are two types of FET —

- i) JFET (Junction Field Effect transistor)
- ii) MOSFET (Metal-Oxide-semiconductor FET).
 OR IGFET → Insulated gate FET.



Advantages of FET over conventional transistor: →

- i) FET is a unipolar semiconductor device, depending only upon the majority carrier (either electrons or holes) whereas BJT depends upon both the carriers majority and minority. Vacuum tube is also a unipolar device. i.e. in FET the current conduction is due to only one type of carrier (either electrons or holes).

- ②
- i) FET has high input impedance. For ex. FET offers a very high input impedance of order $10^9 \Omega$ and for MOSFET of 10^{10} to $10^{15} \Omega$. Thus, FET is voltage controlled device like the vacuum-tube whereas BJT is a current controlled device.
 - ii) FET is less noisy than the vacuum-tube and transistors.
 - iii) FET is less affected by radiation.
 - iv) ~~Better~~ Better thermal stability than BJT.
 - v) FET has very high power gain.
 - vi) Small in size, long life.
 - vii) There is no offset voltage comparision.

FET

- i) Unipolar device
- ii) Current conduction takes place ^{due to} only one carriers (Either electrons or holes) (Majority carriers)
- iii) Voltage-controlled device
- iv) High-input impedance. due to reverse bias.

BJT

- i) Bi-polar device
- ii) Current-conduct takes place due to both the carriers, major and minority carriers
- iii) Current-controlled device.
- iv) Low input impedance than FET.

③ $\Rightarrow$ Gain is characterised by β trans conductance

$\Rightarrow$ Better thermal stability

$\Rightarrow$ Transconductance is low and hence voltage gain is low.

Input rmp. high, $V_i \rightarrow$ High, $g_m = \frac{I_o}{V_i} \rightarrow$ Low.

$\Rightarrow$ Gain is characterised by voltage gain.

$\Rightarrow$ Less thermal stability






$\Rightarrow$ Transconductance is high and hence voltage gain is high.

Disadvantage :- $\Rightarrow$ Costly

$\Rightarrow$ Voltage gain is low.

$\Rightarrow$ FET has relatively small gain BW product.

Basic construction

     

N-channel



N-channel

P-channel

- ④ A FET has the following terminal nodes
- i) Source: $\rightarrow$ It is the terminal through which majority carriers enter the bar.
 - ii) Drain: $\rightarrow$ It is the terminal through which majority carriers leave the bar.
 - iii) Gate: $\rightarrow$ These are the heavily heavily doped impurity regions which are internally connected and form two p-n junctions.
 - iv) Channel: $\rightarrow$ The space betⁿ the two gates through which majority carriers pass.

Operation of "FET"

  To understand the operation of FET, we consider the following fig-1 & 2.



Let, first consider that the gate reverse bias voltage (battery) V_{GG} and Drain supply V_{DD} are not connected. We know that there exists a space charge region on either side

⑤ of p-n junction. Now, let V_{DD} is connected across Drain and source keeping V_{GG} disconnect. This voltage drop V_D betⁿ drain and source uniformly ~~de~~ decreases while going from drain to source. Let this voltage drops through a ~~channel~~ n-channel (fig-1) resistance (R_{DS}). Clearly, the voltage drop near the drain is higher than the drop near source. Let, A and B are two points near drain and source respectively as shown in fig-1. clearly $V_A > V_B$. Due to this ~~reason~~ the reverse-biasing effect at drain is high than the reverse biasing effect at source. This explains why the depletion region penetrates further more into the channel ~~than~~ at drain than the source.

Now, ~~let~~ when gate-reverse voltage is disconnected then the cross-sectional area of channel is high which causes the max^m drain current $I_D = \frac{V_{DD}}{R_{DS}}$. Now, let V_{GG} is applied. As the gate bias, the depletion region (space charge) increases which causes the decrease in cross-section at drain due to which the drain current decreases. Since there are no charge carriers available in depletion region, its conductivity

⑥

When, we increase the gate reverse bias further more, then at a certain -ve gate-source voltage, the two depletion region at near drain as shown in fig-2 touch each other and in this case drain current becomes zero. Thus, we see that for fixed value of V_D , we can vary the drain current controlled by gate voltage. Due to this fact, the FET is called voltage controlled current device.

FET characteristics

- i) Drain characteristic (static characteristic)
- ii) Transfer characteristic.

⑦

Static Drain characteristic of JFET

The curve drawn bet drain current I_D and drain ~~gate~~ to source voltage V_{DS} for different values of V_{GS} is called Drain characteristic.

The fig-1. shows ckt arrangement for drawing drain characteristic.

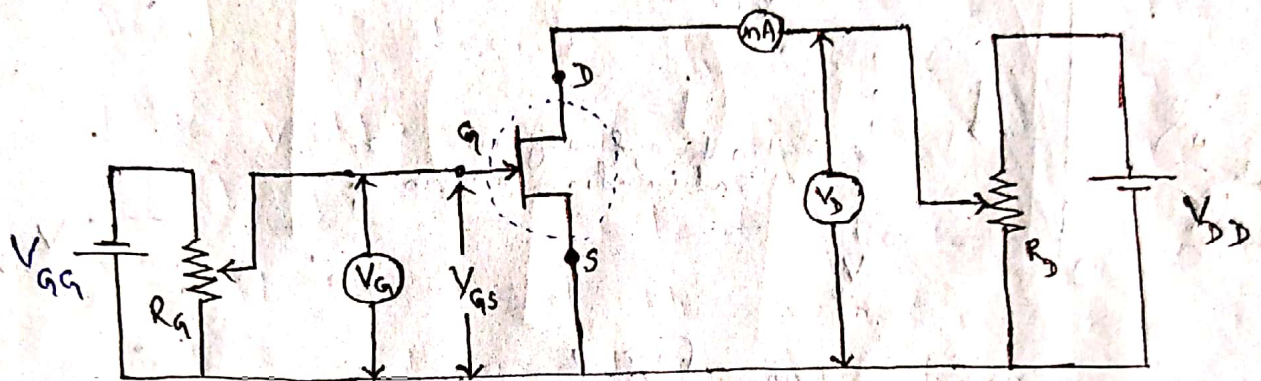


Fig-1.

Ckt consist of an N-channel FET, Potentio-meter R_D and R_G are used to vary V_{DS} and V_{GS} . The drain current I_D is measured by milli-ammeter (mA) connected in series with drain terminal and supply V_{DD} .

Working:- First of all, we set, V_{GS} to zero, and increase V_{DS} in small suitable steps and note-down corresponding value of I_D in each steps. The similar process is repeated for different values of V_{GS} as $V_{GS} = +0.5V, -1V, -2V$ etc and note-down the corresponding values of I_D .

⑧ When, we plot a graph for V_{DS} and I_D , we obtained a curve as shown in fig-2 called drain characteristic.

CP
7/03/2020

 


Fig-2

Analysis

When, $V_{GS} = 0$, $V_{DS} = 0$, no attracting potⁿ at the drain and hence drain current $I_D = 0$. As V_{DS} is increased, the electrons flow from source to drain through channel between depletion layers and drain current I_D increases linearly up to a point A' (knee-point). 'OA' shows, in this region FET behaves like an ordinary resistor till point A.

Now, if we increase V_{DS} and correspondingly I_D , the ohmic-voltage drop in the material bar, reverse biases the gate junction and

⑨ consequently, the channel region begins to constrict. The constriction is unequal along the length, being more at distances farther from source. Thus, if V_{DS} progressively increase the drain current I_D , from point 'A' increases at reverse square-law rate upto a point 'B' called pinch-off point shown in fig-2. The voltage corresponding to this point 'B' is called pinch-off voltage V_p . At this point, the channel is more or less blocked and current through channel almost becomes constant I_{DSS} called saturation drain current. Thus, the minimum drain-to-source voltage where drain current approaches a constant value (saturation value), is called pinch-off voltage. Beyond pinch-off voltage, the channel width can not be reduced. Here it should be remembered that, pinch-off does not mean drain current I_D cut-off moreover the channel is not completely closed.

As, V_{DS} is further increased, the channel resistance also increases in such a way that I_D practically remains constant upto a point 'C' shown in graph. The region 'BC' is called saturation-region or "amplifier-region".

⑩ In this region 'BC' FET operates as constant-current device (offering very large resistance, ideally infinity). A relationship betⁿ I_D and V_{GS} is given by "William Bradford Shockley" called Shockley eqⁿ as below —

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

Control variable

Constant

With continued increase of V_{DS} corresponding to point C (called avalanche breakdown), eventually breakdown across the gate junction takes place and I_D shoots to a high value.

Miller Theorem

 


Fig-1(a)

 


Fig-1(b)

Miller theorem states that, if an impedance Z is connected between input and output terminal of a two port network with gain A_v , then this impedance can be replaced by connecting $Z_1 = \frac{Z}{1-A_v}$ into input side and $Z_2 = \frac{Z}{1-A_v^{-1}}$ into output side as shown in above fig.

Analysis.

$$I_1 = \frac{V_1 - V_2}{Z} = \frac{V_1 \left(1 - \frac{V_2}{V_1}\right)}{Z} = \frac{V_1 (1 - A_v)}{Z}$$

$$\Rightarrow I_1 = \frac{V_1}{\left(\frac{Z}{1-A_v}\right)} = \frac{V_1}{Z_1}, \text{ where } Z_1 = \frac{Z}{1-A_v}$$


And,
$$I_2 = \frac{V_2 - V_1}{Z} = \frac{V_2 \left(1 - \frac{V_1}{V_2}\right)}{Z} = \frac{V_2 (1 - A_v^{-1})}{Z}$$

$$\Rightarrow I_2 = \frac{V_2}{\left(\frac{Z}{1-A_v^{-1}}\right)} = \frac{V_2}{Z_2}, \text{ where } Z_2 = \frac{Z}{1-A_v^{-1}}$$

 Q12
07/03/2020

Miller Effect capacitance

In the high frequency region, the capacitance (inter-electrode cap.) of active device and wiring capacitor betⁿ the leads of network takes play a vital role. For inverting, the input and output capacitance is increased by capacitance level sensitive to the inter-electrode capacitance betⁿ i/p and o/p terminals of device and the gain of amplifier. i.e. there is a feedback process. This feedback capacitance is C_f .



(Network employed for Miller's cap.)

Apply KCL at input-port —

$$I_i = I_1 + I_2 \quad \text{--- (i)}$$

$$\text{Now, } I_1 = \frac{V_i}{Z_i} \quad \text{--- (ii)}$$

and, $I_1 = \frac{V_i}{R_i}$ ——— (iii)

$I_2 = \frac{V_i - V_o}{X_{cf}}$ ——— (iv)

from eqs (i), (ii), (iii) & (iv)

$I_i = I_1 + I_2 \Rightarrow \frac{V_i}{Z_i} = \frac{V_i}{R_i} + \frac{V_i - V_o}{X_{cf}}$

since $A_v = \frac{V_o}{V_i} \Rightarrow V_o = A_v V_i$

$\therefore \frac{V_i}{Z_i} = \frac{V_i}{R_i} + \frac{V_i - A_v V_i}{X_{cf}}$

or $\frac{V_i}{Z_i} = V_i \left[\frac{1}{R_i} + \frac{(1 - A_v)}{X_{cf}} \right]$

or $\frac{1}{Z_i} = \frac{1}{R_i} + \frac{1}{\left\{ \frac{X_{cf}}{(1 - A_v)} \right\}}$

$\therefore Z_i = R_i \parallel \left\{ \frac{X_{cf}}{(1 - A_v)} \right\}$

which follows the statement of Miller's theorem. Hence $\left(\frac{X_{cf}}{1 - A_v} \right)$ is termed as Miller's capacitive reactance at input side.

Let $X_{CM_i} = \frac{X_{cf}}{1 - A_v}$

then,

$$X_{C_{M_i}} = \frac{X_{C_f}}{1 - A_v}$$

$$\text{or } \frac{1}{j\omega C_{M_i}} = \frac{1}{j\omega C_f (1 - A_v)}$$

$$\Rightarrow \boxed{C_{M_i} = (1 - A_v) C_f}$$

In similar manner, on output side —

$$I_o = I_1 + I_2 \quad \text{or } \frac{V_o}{Z_o} = \frac{V_o}{R_o} + \frac{V_o - V_i}{X_{C_f}}$$

$$\text{or } \frac{V_o}{Z_o} = \frac{V_o}{R_o} + \frac{(V_o - \frac{V_o}{A_v})}{X_{C_f}}$$

$$\text{or } \frac{1}{Z_o} = \frac{1}{R_o} + \frac{(1 - \frac{1}{A_v})}{X_{C_f}} \Rightarrow \frac{1}{Z_o} = \frac{1}{R_o} + \frac{1}{\frac{X_{C_f}}{(1 - \frac{1}{A_v})}}$$

$$\text{or } Z_o = R_o \parallel \left(\frac{X_{C_f}}{1 - \frac{1}{A_v}} \right)$$

$$\text{Let, } X_{C_{M_o}} = \frac{X_{C_f}}{1 - \frac{1}{A_v}} \quad \text{or } \frac{1}{j\omega C_{M_o}} = \frac{1}{j\omega C_f (1 - \frac{1}{A_v})}$$

$$\Rightarrow \boxed{C_{M_o} = (1 - \frac{1}{A_v}) C_f}$$

If $A_v \gg 1$, then, $C_{M_o} \approx C_f$.

2. DISTORTION

For an ideal amplifier, the output corresponding to sinusoidal input should be sinusoidal. But practically, output is not just the replica of input. The change in output waveform in comparison to input signal waveform is known as distortion. There are following types of distortions —

- i) Nonlinear distortion (OR Amplitude distortion)
- ii) Frequency distortion
- iii) phase-shift distortion.

i) Nonlinear distortion:- The distortion which results due to the production of new frequency components in output which was not present in input, is called 'non-linear distortion'. This distortion is caused mainly due to non-linear behaviour of active element.

ii) Frequency distortion:- The distortion which comes into existence when different frequency components are amplified differently. In BJT or FET, such type of distortion comes into existence due to internal capacitance or associated ext (coupling components or load) is reactive.

iii) Phase shift distortion:- This type of distortion comes into existence when different freq. component shifted at different or from unequal phase angle. Phase angle is