

In a similar way, the *transfer admittance* is defined as the ratio of current transform at output port to the voltage transform at the input port. It is given as

$$Y_{12}(s) = \frac{I_2(s)}{V_1(s)} \quad \dots (14.7)$$

14.4 VOLTAGE AND CURRENT TRANSFER RATIO

Voltage and current transfer ratios are basically transfer functions. *Voltage transfer ratio* is the ratio of voltage transform at output port to the voltage transform at the input port. It is usually denoted by $G(s)$. Thus,

$$G_{12}(s) = \frac{V_2(s)}{V_1(s)} \quad \dots (14.8)$$

In a similar way, the ratio of transform of current at output port to that at the input port of a two port network gives the *current transfer ratio*. It is represented by $\alpha(s)$. Thus,

$$\alpha_{12}(s) = \frac{I_2(s)}{I_1(s)} \quad \dots (14.9)$$

EXAMPLE 14.1 A series R-L circuit is in parallel with a capacitance. Find the input impedance in Laplace domain.

SOLUTION. Figure E14.1 represents the parallel combination of one series R-L circuit with a capa-

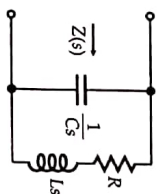


Fig. E14.1

ctance in Laplace domain. The input impedance is $Z(s)$ which is obviously

$$\begin{aligned} Z(s) &= \frac{(1/Cs)(R + Ls)}{\frac{1}{Cs} + (R + Ls)} \\ &= \frac{R + Ls}{1 + RCs + LCs^2} \\ &= \frac{R}{s + \frac{1}{L}} \\ &= \frac{C \left(s^2 + \frac{R}{L}s + \frac{1}{LC} \right)}{s + \frac{1}{L}} \end{aligned}$$

$\therefore$ Input impedance

$$Z(s) = \frac{s + (R/L)}{C \left(s^2 + \frac{R}{L}s + \frac{1}{LC} \right)}$$

EXAMPLE 14.2 Find $Z_{11}(s)$, $Z_{21}(s)$ in the following circuit. (Fig. E14.2)

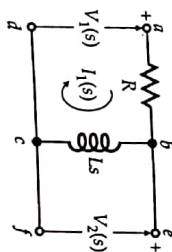


Fig. E14.2

SOLUTION. KVL gives for loop $abcd$,

$$RI_1(s) + I_1(s) Ls = V_1(s) \quad \dots (i)$$

or, $I_1(s)(R + Ls) = V_1(s)$

$$\therefore Z_{11}(s) = \frac{V_1(s)}{I_1(s)} = (R + Ls) \quad \dots (ii)$$

Again in loop $bcfe$, KVL yields

$$V_2(s) = I_1(s) Ls$$

$$\text{which gives, } Z_{12}(s) = \frac{V_2(s)}{I_1(s)} = Ls. \quad \dots (iii)$$

Equations (ii) and (iii) give the required result.

EXAMPLE 14.3 Obtain the transfer function $V_2(s)/V_1(s)$ in Fig. E14.3.

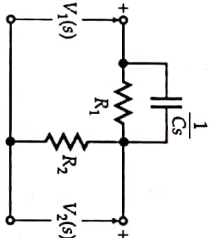


Fig. E14.3

SOLUTION. The equivalent impedance of $\frac{1}{Cs}$ and R_1 is given by $Z(s)$.

Obviously,

$$Z(s) = \frac{R_1 \times \frac{1}{Cs}}{R_1 + \frac{1}{Cs}} = \frac{R_1}{R_1 Cs + 1}$$

Applying KVL in left loop of Fig. E14.3, we get

$$V_1(s) = I_1(s)[Z(s) + R_2]$$

$$V_2(s) = R_2 I_1(s).$$

$$\therefore V_2(s)/V_1(s) = \frac{R_2}{R_2 + Z(s)}$$

$$= \frac{R_2}{R_2 + \frac{R_1}{R_1 Cs + 1}}$$

$$= \frac{R_2(1 + R_1 Cs)}{R_2 + R_1 R_2 Cs + R_1}$$

$$= \frac{R_2 + R_1 R_2 Cs}{R_1 + R_2 + R_1 R_2 Cs}$$

$$= \frac{R_2 R_1 C \left(s + \frac{1}{R_1 C} \right)}{R_2 R_1 C \left(s + \frac{R_1 + R_2}{R_1 R_2 C} \right)}$$

i.e., Voltage transfer ratio

$$= \frac{R_2 R_1 C \left(s + \frac{1}{R_1 C} \right)}{R_2 R_1 C \left(s + \frac{R_1 + R_2}{R_1 R_2 C} \right)}$$

EXAMPLE 14.4 Obtain $Z_{12}(s)$ for a parallel R-C network where $R = 1\Omega$; $C = 1\text{ F}$.

SOLUTION. In Fig. E14.4,

$$V_2(s) = I_1(s) \left[\frac{R \times \frac{1}{Cs}}{R + \frac{1}{Cs}} \right]$$

$$\text{or, } \frac{V_2(s)}{I_1(s)} = \frac{R}{RCs + 1} = \frac{1}{\left(s + \frac{1}{RC} \right) C}$$

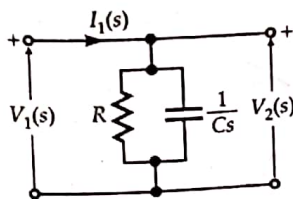


Fig. E14.4

$$\begin{aligned} \therefore Z_{12}(s) &= \frac{V_2(s)}{I_1(s)} \\ &= \frac{1}{C \left(s + \frac{1}{RC} \right)} = \frac{1}{1(s+1)} \\ \therefore Z_{12}(s) &= \frac{1}{s+1}. \end{aligned}$$

EXAMPLE 14.5 Find (V_2/V_1) and (V_2/I_1) in Fig. E14.5.

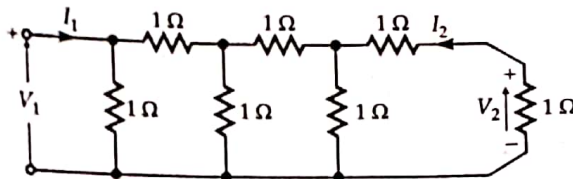


Fig. E14.5

SOLUTION. The figure is redrawn (Fig. E14.6) with marking of nodes and voltages at the node.

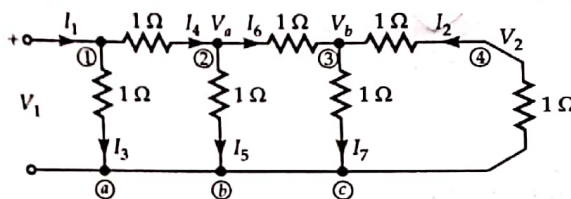


Fig. E14.6

At node (1), application of KCL yields

$$I_1 = I_3 + I_4 = \frac{V_1}{1} + \frac{V_1 - V_a}{1} = 2V_1 - V_a \quad \dots(1)$$

At node (2),

$$\begin{aligned} I_4 &= I_5 + I_6 \\ \text{or, } \frac{V_1 - V_a}{1} &= \frac{V_a}{1} + \frac{V_a - V_b}{1} \end{aligned}$$

$$\text{or, } V_1 - V_a = V_a + V_a - V_b$$

$$\text{or, } V_1 - 3V_a + V_b = 0 \quad \dots(2)$$

At node (3),

$$\begin{aligned} I_6 &= I_7 - I_2 \\ \text{or, } \frac{V_a - V_b}{1} &= \frac{V_b}{1} - \frac{V_2 - V_b}{1} \end{aligned}$$

$$\text{or, } V_a - V_b = V_b - V_2 + V_b$$

$$\text{or, } V_2 + V_a - 3V_b = 0 \quad \dots(3)$$

At node (4), KCL yields,

Current through = Current flows between nodes (3) and (4)

$$i.e., \quad \frac{V_2}{1} = \frac{V_b - V_2}{1}$$

$$or \quad 2V_2 - V_b = 0 \quad \dots(4)$$

From (4), $V_b = 2V_2$ and from (3) we then get $V_a = 5V_2$

From (2), we get

$$V_1 - 3(5V_2) + (2V_2) = 0 \quad or, \quad V_1 = 13V_2$$

and from (1), we get

$$I_1 = 2(13V_2) - (5V_2) = 21V_2$$

Then finally, we get

$$V_2/V_1 = \frac{1}{13} \quad \text{and} \quad V_2/I_1 = \frac{1}{21}$$

EXAMPLE 14.6 Find $Z(s)$ for the following network (Fig. E14.7).

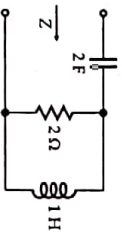


Fig. E14.7

SOLUTION. The transform network is shown in Fig. E14.7(a).

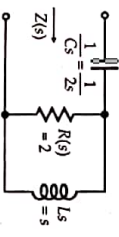


Fig. E14.7(a)

$$\begin{aligned} Z(s) &= \left[R(s) \parallel Ls \right] + \frac{1}{Cs} = \frac{2 \times s}{2 + s} + \frac{1}{2s} \\ &= \frac{4s^2 + s + 2}{2s(s+2)} = \frac{4s^2 + s + 2}{2s^2 + 4s} \\ \therefore Z(s) &= \frac{4s^2 + s + 2}{2s^2 + 4s} \end{aligned}$$

EXAMPLE 14.7 Find the driving point impedance for the network shown in Fig. E14.8.

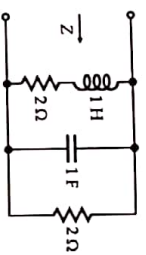


Fig. E14.8

SOLUTION. The transfer network is shown in Fig. E14.8(a).

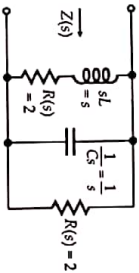


Fig. E14.8(a)

$$\begin{aligned} \text{Here } Z(s) &= \left[R_2(s) \parallel \frac{1}{Cs} \right] \parallel [sL + R_1(s)] \\ &= \frac{2 \times \frac{1}{s}}{\frac{2}{s} + \frac{1}{s}} \parallel \left(\frac{s}{2s+1} \right) \parallel (2+s) \\ &= \frac{2}{2s+1} \parallel (2+s) = \frac{2}{(2s+1)(2+s)} \times (2+s) \\ &= \frac{2}{2s+1} \end{aligned}$$

i.e., $Z(s)$, the driving point impedance = $\frac{2(s+2)}{2s^2 + 5s + 4}$.

EXAMPLE 14.9 Find the driving point admittance of the network shown in Fig. E14.9.

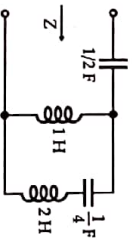


Fig. E14.9

SOLUTION. The transform network is shown in Fig. E14.9(a).

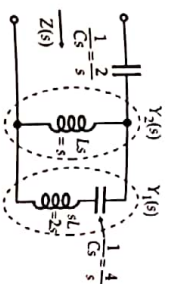


Fig. E14.9(a)

$$\begin{aligned} \text{Here } Y_1(s) &= \frac{1}{2s + \frac{4}{2s + 4}} = \frac{1}{2s + \frac{4}{2s + 4}} = \frac{s}{2s^2 + 4s + 4} \\ Y_2(s) &= \frac{1}{s} \\ \therefore Y_E(s) &= Y_1(s) + Y_2(s) = \frac{s}{2s^2 + 4s + 4} + \frac{1}{s} \\ &= \frac{3s^2 + 4}{2s^3 + 4s} \end{aligned}$$

$$\therefore Z_E(s) = \frac{1}{Y(s)} = \frac{2s^3 + 4s}{3s^2 + 4}$$

$$\begin{aligned} \text{Thus } Z(s) &= Z_E(s) + \frac{1}{Cs} \\ &= \frac{2s^3 + 4s}{3s^2 + 4} + \frac{1}{Cs} \\ &= \frac{2s^4 + 10s^2 + 8}{3s^3 + 4s} \end{aligned}$$

$$\therefore Y(s) = \frac{1}{Z(s)} = \frac{3s^3 + 4s}{2s^4 + 10s^2 + 8}$$

$$\text{here } Y(s) = \frac{3s^3 + 4s}{2s^4 + 10s^2 + 8}$$

EXAMPLE 14.9 Find the transfer function of the network shown in Fig. E14.10.

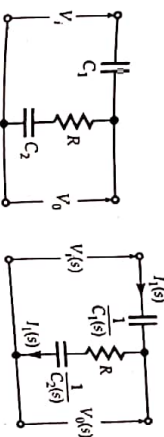


Fig. E14.10

Fig. E14.10(a)

SOLUTION. Transforming the given network in the Laplace domain [Fig. E14.10(a)].

$$V_1(s) = I_1(s) \left[R + \frac{1}{C_1 s} + \frac{1}{C_2 s} \right] \quad \dots(1)$$

and

$$V_0(s) = I_1(s) \left[R + \frac{1}{C_2 s} \right]$$

$$\therefore \frac{V_0(s)}{V_1(s)} = \frac{R + \frac{1}{C_2 s}}{R + \frac{1}{C_1 s} + \frac{1}{C_2 s}} = \frac{(RC_2 s + 1)C_1 s}{(RC_1 C_2 s^2 + C_1 s + C_2 s)}$$

$$= \frac{C_1(1 + RC_2 s)}{C_1(1 + RC_2 s) + C_2 s}$$

i.e., the transfer function (voltage transfer ratio) is given by

$$\left[\frac{C_1(1 + RC_2 s)}{C_1 + C_2 + RC_1 C_2 s} \right]$$

EXAMPLE 14.10 Find the expression of voltage transfer ratio for the network shown in Fig. E14.11.

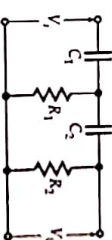


Fig. E14.11

SOLUTION. The equivalent circuit of Fig. E14.11 in Laplace domain is shown in Fig. E14.11(a).

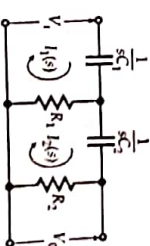


Fig. E14.11(a)

Here, in the leftmost loop,

$$V_1(s) = I_1(s) \left[R + \frac{1}{C_1 s} \right] - R_1 I_2(s) \quad \dots(a)$$

in the second loop,

$$-R_1 I_1(s) + \left(R + R_2 + \frac{1}{C_2 s} \right) I_2(s) = 0 \quad \dots(b)$$

and in the rightmost loop,

$$R_2 I_2(s) = V_0(s) \quad \dots(c)$$

$\therefore M_{02}$ (distance between "zero" to "pole" at -2) = 2

and $\phi_{02} = 180^\circ$

Also, $M_{32} = 1$ and $\phi_{32} = 0^\circ$

[$\because$ the distance between pole at -3 and pole at -2 is 1 unit and ϕ_{32} is directed in opposite sense to ϕ_{02}]

$$\therefore K_2 = H \frac{M_{02} e^{j\phi_{02}}}{M_{32} e^{j\phi_{32}}} = 10 \frac{2e^{j180^\circ}}{e^{j0^\circ}} = 20 e^{j180^\circ} = -20.$$

Next we consider the pole at -3 .

$\therefore M_{03} = 3$; $\phi_{03} = 180^\circ$

Also, $M_{23} = 1$; $\phi_{23} = 180^\circ$

$$\therefore K_1 = H \frac{M_{03} e^{j\phi_{03}}}{M_{23} e^{j\phi_{23}}} = 10 \frac{3e^{j180^\circ}}{e^{j180^\circ}} = 30$$

This gives $v(t) = 30 e^{-3t} - 20 e^{-2t}$.

EXAMPLE 14.24 Obtain the pole zero diagram of the given function and obtain the time domain response.

$$I(s) = \frac{2s}{(s+1)(s^2+2s+4)}$$

SOLUTION. Using partial fraction,

$$I(s) = \frac{2s}{(s+1)(s^2+2s+4)} = \frac{K_1}{(s+1)} + \frac{K_2}{(s+1-j\sqrt{3})} + \frac{K_3}{(s+1+j\sqrt{3})}$$

$$\therefore i(t) = K_1 e^{-t} + K_2 e^{-(1-j\sqrt{3})t} + K_3 e^{-(1+j\sqrt{3})t}$$

The pole zero plot has been exhibited in the adjacent figure (Fig. E14.27).

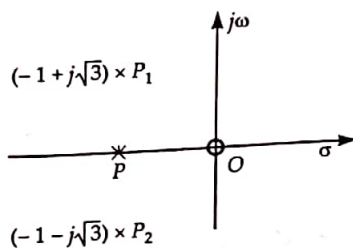


Fig. E14.27

$$K_1 = H \frac{M_{OP} e^{j\phi_{OP}}}{M_{P1-P} M_{P2-P} e^{j(\phi_{P1-P} + \phi_{P2-P})}}$$

$$= 2 \frac{1 \cdot e^{j180^\circ}}{(\sqrt{3} \times \sqrt{3}) e^{j(-90^\circ + 90^\circ)}}$$

$$[\because M_{OP} = 1; M_{P1-P} = M_{P2-P} = \sqrt{3}$$

$$\phi_{OP} = 180^\circ; \phi_{P1-P} = -90^\circ; \phi_{P2-P} = 90^\circ]$$

$$\therefore K_1 = 0.67 e^{j180^\circ} = -0.67$$

$$\text{and } K_2 = H \frac{M_{OP1} e^{j\phi_{OP1}}}{M_{P-P1} M_{P2-P1} e^{j(\phi_{P-P1} + \phi_{P2-P1})}}$$

(Please check with Fig. E14.28)

$$= 2 \frac{e^{j[\tan^{-1} \frac{OP}{PP1} + 90^\circ]}}{(\sqrt{3} \times 2 \sqrt{3}) e^{j(90^\circ + 90^\circ)}}$$

$$= 0.67 e^{j[\tan^{-1} \frac{OP}{PP1} + 90^\circ - 180^\circ]}$$

$$= 0.67 e^{-j(60^\circ)}$$

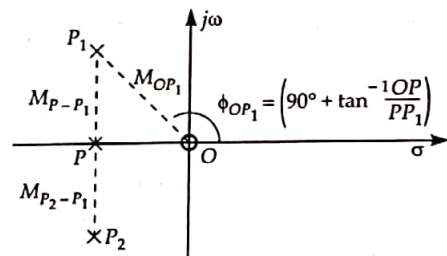


Fig. E14.28

$\therefore K_3$, being the conjugate of K_2 will be given by

$$K_3 = 0.67 e^{j(60^\circ)} [K_3 = K_2^*]$$

$$\therefore i(t) = -0.67 e^{-t} + 0.67 e^{+j(60^\circ)} e^{-(1+j\sqrt{3})t} + 0.67 e^{-j(60^\circ)} e^{-(1-j\sqrt{3})t}$$

EXAMPLE 14.25(a) Check the stability of the following polynomial by applying Routh-Hurwitz criterion :

$$P(s) = s^4 + 2s^3 + 4s^2 + 12s + 10$$

SOLUTION. Routh array of the polynomial can be obtained from the following coefficients.

$$b_0 = 1; b_2 = 4; b_4 = 10; b_1 = 2; b_3 = 12$$

$$c_1 = \frac{b_1 b_2 - b_0 b_3}{b_1} = \frac{8 - 12}{2} = -2$$

$$\therefore c_2 = \frac{b_1 b_4 - b_0 b_5}{b_1} = \frac{20 - 1 \times 0}{2} = 10$$

$$d_1 = \frac{c_1 b_3 - b_1 c_2}{c_1} = \frac{-2 \times 12 - 2 \times 10}{-2} = 22$$

$$d_2 = b_5 = 0$$

$$e_1 = \frac{c_2 d_1 - c_1 d_2}{d_1} = \frac{10 \times 16 - (-2) \times 0}{16} = 10$$

$$f_1 = d_2 = 0$$

This gives

s^4	1	4	10
s^3	2	12	
s^2	-2	10	
s^1	22	0	
s^0	10		

There is a sign change in the 1st column of the array. Hence the system is not stable.

EXAMPLE 13.25(a) For what value of 'K' the polynomial $s^4 + 10s^3 + 35s^2 + Ks + 24 = 0$ is said to be stable? Solve by using Routh Hurwitz Array.

SOLUTION. Given Polynomial is

$$s^4 + 10s^3 + 35s^2 + Ks + 24 = 0.$$

Routh Hurwitz Array is shown below

s^4	1	35	24
s^3	10	K	
s^2	$\frac{35 \times 10 - K \times 1}{10} = a_1$	$\frac{10 \times 24 - 0 \times 1}{10} = 24$	
s^1	$\frac{a_1 \times K - 24 \times 10}{a_1}$		
s^0	24		

For stability of the network, $a_1 > 0$

$$\text{i.e., } \frac{350 - K}{10} > 0 \quad \text{or} \quad K < 350.$$

Hence the range K is $(0 < K < 350)$.

EXAMPLE 14.26(a) A polynomial is given by

$$P(s) = s^3 + 2s^2 + 4s + M.$$

"M" is adjustable. Apply Routh Hurwitz criterion.

SOLUTION. Routh array gives

s^3	1	4
s^2	2	M
s^1	$\frac{8-M}{2}$	
s^0	M	

We see that if M is less than 8, the system is stable. There will be no change in the sign of 1st column. If $M = 8$, then also there is no change in sign in the first column and hence the system will also be stable.

EXAMPLE 13.26(b) Check whether the following polynomial $P(s) = s^4 + s^3 + 2s^2 + 2s + 3$ is stable or not. Comment on your findings.

SOLUTION. Given polynomial is

$$P(s) = s^4 + s^3 + 2s^2 + 2s + 3$$

where total number of rows are $(4 + 1) = 5$

Routh Hurwitz Array is shown below :

s^4	1	2	3
s^3	1	2	
s^2	$\frac{2-2=0}{1} = 0$	3	
s^1	∞		
s^0			

In above array, we found third row of first column has a zero value. Hence the subsequent value is infinite. Let us now assume a small value ϵ in place of the zero value. The modified array is given below :

s^4	1	2	3
s^3	1	2	
s^2	ϵ	3	
s^1	$\frac{2\epsilon - 3}{\epsilon} > 0$		
s^0	3		

For stability point of view, $\epsilon > 0$ i.e., $\frac{2\epsilon - 3}{\epsilon} > 0$.

This gives $\epsilon > 3/2$

Hence to have the stability of the function, we should have any value of ϵ more than $(3/2)$.

EXAMPLE 14.27 What should be the value of L such that $Z(s) = 1$ in the network of Fig. E14.29?

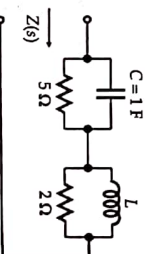


Fig. E14.29

$$\begin{aligned}
 &= V_2(s) \left[2s + \frac{1}{s} + \frac{2}{s} + \frac{1}{s^3} - s \right] \\
 &= V_2(s) \left[\frac{2s^4 + s^2 + 2s^2 - s^4 + 1}{s^3} \right] \\
 &= V_2(s) \left[\frac{s^4 + 3s^2 + 1}{s^3} \right]
 \end{aligned}$$

$$\therefore \frac{V_2(s)}{V_1(s)} = \frac{s^4}{s^4 + 3s^2 + 1} = G_{21}(s)$$

$$\text{i.e., } G_{12}(s) = \frac{s^4}{s^4 + 3s^2 + 1}.$$

EXAMPLE 14.31 Find $G_{21}(s)$ for the network shown in Fig. E14.36 when $V_1(s)$ is the applied voltage at the input terminals.

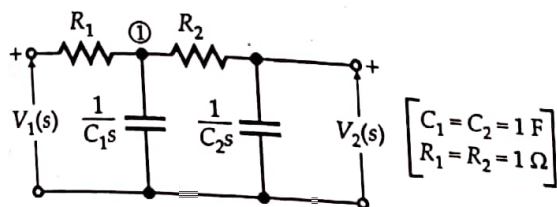


Fig. E14.36

SOLUTION. In the s -domain network of Fig. E14.36, let $V_3(s)$ be the potential at the junction of R_1, R_2, C_1 i.e., at node (1).

Applying KCL at node (1),

$$\begin{aligned}
 \frac{V_1(s) - V_3(s)}{R_1} + \frac{V_2(s) - V_3(s)}{R_2} &= \frac{V_3(s)}{\frac{1}{C_1 s}} \\
 &= V_3(s) C_1 s
 \end{aligned}$$

$$\text{or, } \frac{V_1(s)}{R_1} = V_3(s) \left[sC_1 + \frac{1}{R_1} + \frac{1}{R_2} \right] - \frac{V_2(s)}{R_2} \quad \dots(1)$$

It may also be evident that the current passing through R_2 also passes through C_2

$$\text{i.e., } \frac{V_3(s) - V_2(s)}{R_2} = \frac{V_2(s)}{\frac{1}{sC_2}}$$

$$\text{or, } 0 = \left[\frac{-V_3(s)}{R_2} \right] + V_2(s) \left[sC_2 + \frac{1}{R_2} \right]$$

$$\text{i.e., } V_3(s) = V_2(s) [sC_2 R_2 + 1] \quad \dots(2)$$

Utilising (2) in (1),

$$\frac{V_1(s)}{R_1} = V_2(s) [1 + sC_2 R_2] \left[sC_1 + \frac{1}{R_1} + \frac{1}{R_2} \right] - \frac{V_2(s)}{R_2}$$

$$\text{or, } V_1(s) = V_2(s) \left[(R_1 + sC_2 R_2 R_1) \left\{ sC_1 + \frac{1}{R_1} + \frac{1}{R_2} \right\} - \frac{R_1}{R_2} \right]$$

$$\text{or, } \frac{V_2(s)}{V_1(s)} = G_{12}(s)$$

$$\begin{aligned}
 &= \frac{1}{\left[(R_1 + sC_2 R_1 R_2) \left\{ sC_1 + \frac{1}{R_1} + \frac{1}{R_2} \right\} - \frac{R_1}{R_2} \right]} \\
 &= \frac{1}{[(1+s)(s+1+1)-1]} = \frac{1}{(s+1)[(s+2)-1]}
 \end{aligned}$$

$$\text{i.e., } G_{12}(s) = \frac{1}{(s+1)^2}.$$

EXAMPLE 14.32 Obtain the voltage transfer function of the network shown in Fig. E14.37.

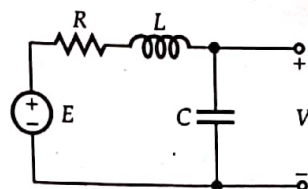


Fig. E14.37

SOLUTION. Let us first transform the network to frequency domain (Fig. E14.38).

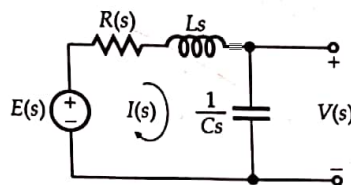


Fig. E14.38

$$\text{Here, } I(s) = \frac{E(s)}{R + Ls + \frac{1}{Cs}}$$

$$\therefore V(s) = I(s) \times \frac{1}{Cs} = \frac{E(s)}{R + Ls + \frac{1}{Cs}} \cdot \frac{1}{Cs}$$

$$\therefore \frac{V(s)}{E(s)} = \frac{\frac{1}{Cs}}{R + Ls + \frac{1}{Cs}} = \frac{1}{LCs^2 + RCs + 1}$$

Obviously, $\frac{V(s)}{E(s)}$ gives the voltage transfer ratio and

$$\frac{V(s)}{E(s)} = \frac{1}{LCs^2 + RCs + 1}$$

This gives,

$$I_2(s) = I_0(s) \frac{\frac{C_2 s}{1 + RC_2 s}}{C_1 s + \frac{C_2 s}{1 + RC_2 s}}$$

$$= I_0(s) \frac{C_2 s}{C_1 s(1 + RC_2 s) + C_2 s};$$

$$\frac{I_2(s)}{I_0(s)} = \text{Current transfer ratio}$$

$$= \frac{sC_2}{sC_2 + sC_1(1 + RC_2 s)}$$

Thus, current transfer ratio

$$= \frac{C_2}{C_2 + C_1(1 + RC_2 s)}$$

EXAMPLE 14.37 Obtain the driving point admittance of the network shown in Fig. E14.46.

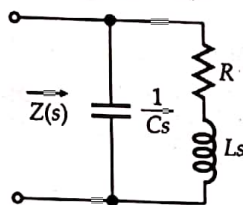


Fig. E14.46

SOLUTION.

$$Z(s) = \frac{(R + Ls) \frac{1}{Cs}}{R + Ls + \frac{1}{Cs}} = \frac{\frac{1}{Cs} (R + Ls)}{1 + RCs + LCs^2}$$

$$= \frac{R + Ls}{1 + RCs + LCs^2}$$

$\therefore Y(s)$, the driving point admittance

$$= \frac{1}{Z(s)} = \frac{LCs^2 + RCs + 1}{R + Ls}$$

i.e., $Y(s) = \frac{1 + RCs + LCs^2}{R + Ls}$

EXAMPLE 14.38 Find the driving point impedance of the network shown in Fig. E14.47.

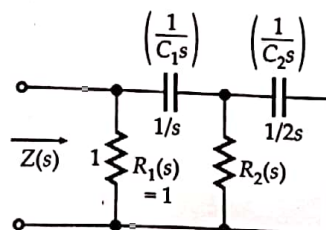


Fig. E14.47

SOLUTION. R_2 and C_2 are parallel

$$\therefore Y_2(s) = Y_{R_2}(s) + Y_{C_2}(s)$$

$$= 1 + \frac{1}{Z_{C_2}(s)} = 1 + \frac{1}{\frac{1}{2s}} = 1 + 2s$$

i.e., $Z_2(s) = \frac{1}{1 + 2s}$

However, $Z_2(s)$ is in series with C_1

$$\therefore Z_1(s) = Z_2(s) + \frac{1}{C_1 s} = \frac{1}{1 + 2s} + \frac{1}{s} = \frac{3s + 1}{s(2s + 1)}$$

$$\therefore Y_1(s) = \frac{s(2s + 1)}{3s + 1}$$

Again $Z_1(s)$ and $R_1(s)$ are in parallel.

$$\therefore Y(s) = \frac{1}{Z_1(s)} + \frac{1}{R_1(s)}$$

$$= \frac{s(2s + 1)}{3s + 1} + 1 = \frac{2s^2 + 4s + 1}{3s + 1}$$

$$\therefore Z(s) = \frac{1}{Y(s)} = \frac{3s + 1}{2s^2 + 4s + 1}$$

i.e., Driving point impedance = $\frac{3s + 1}{2s^2 + 4s + 1}$

EXAMPLE 14.39 In the network of Fig. E14.48, find pole-zero plot.

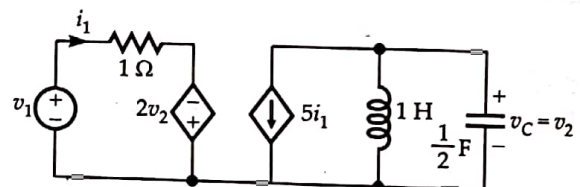


Fig. E14.48

SOLUTION. Let us first convert Fig. E14.48 to s-domain circuit (Fig. E14.49).

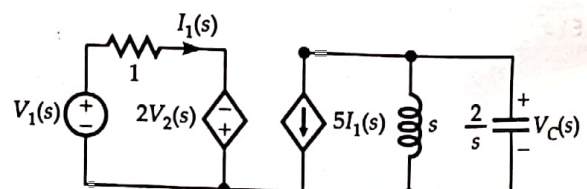


Fig. E14.49

Using KCL at right hand loop,

$$5I_1(s) + \frac{V_C(s)}{s} + \frac{V_C(s)}{2/s} = 0 \quad \dots(1)$$