 


MULTIPLEXERS 2

DE-MUX.


The word "Multiplex" stands for "many into one". Multiplexing is a process of transmitting a large number of information over a single transmission line or channel.

UX:- A multiplexer is a combinational ckt which combine a number of data input or information and transmit it over a single transmission line. In other word, a multiplexer is a combinational ckt or data selector that can select any one of input from a large number of inputs and transmit it through a single transmission line. Thus, a multiplexer has several number of input lines and only one output line. The selection of particular input line is decided by select input line. The no. of input lines of a MUX is also decided by the number of select input lines. If 'm' is the number of select input lines then number of data-input lines $n = 2^m$. A basic block diagram is shown in fig



Basic-four-input MUX or 4-to-1 MUX

2

 

Above fig. shows a block diagram of a basic 4-to-1 MUX. As the name, it has 4-input lines ($D_0 \rightarrow D_3$) and $4=2^2$, 2-select input lines.


If $S_1=0, S_0=0$, $Y=D_0$
 $S_1=0, S_0=1$, $Y=D_1$
 $S_1=1, S_0=0$, $Y=D_2$
 $S_1=1, S_0=1$, $Y=D_3$

S_1	S_0	Y	
0	0	D_0	
0	1	D_1	
1	0	D_2	
1	1	D_3	

By truth table, we can express output in boolean expression as below

$$Y = \bar{S}_1 \bar{S}_0 D_0 + \bar{S}_1 S_0 D_1 + S_1 \bar{S}_0 D_2 + S_1 S_0 D_3$$

 
This boolean expression can be implemented by basic logic gates as below




8-to-1 MUX

8-to-1 MUX has 8 input lines and $8=2^3$, 3 select input lines and a single output line. The fig. as below shows a block diagram of 8-to-1 MUX.


S_2	S_1	S_0	Y
0	0	0	D_0
0	0	1	D_1
0	1	0	D_2
0	1	1	D_3
1	0	0	D_4
1	0	1	D_5
1	1	0	D_6
1	1	1	D_7

 
 
$$Y = \bar{S}_2 \bar{S}_1 \bar{S}_0 D_0 + \bar{S}_2 \bar{S}_1 S_0 D_1 + \bar{S}_2 S_1 \bar{S}_0 D_2 + \bar{S}_2 S_1 S_0 D_3 + S_2 \bar{S}_1 \bar{S}_0 D_4 + S_2 \bar{S}_1 S_0 D_5 + S_2 S_1 \bar{S}_0 D_6 + S_2 S_1 S_0 D_7$$



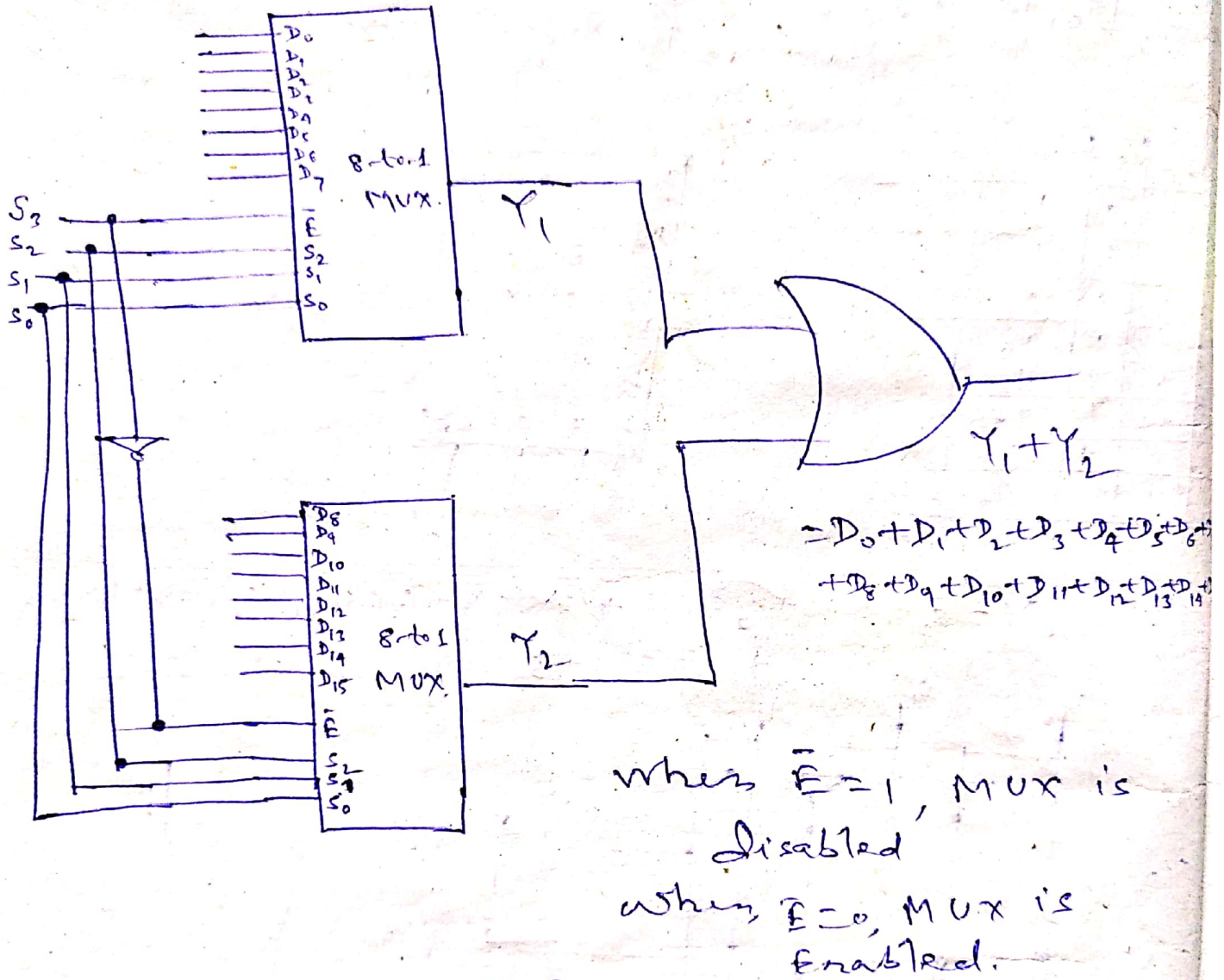Implementation of 16-to-1 MUX by using two 8-to-1 MUX




Implementation of Boolean Exp. by using MUX

$$F(A, B, C, D) = \sum(0, 1, 3, 4, 8, 9, 15)$$

Here there are 4-variables — A, B, C, D.
 Out of those are connected to 3-select input.
 Thus, this function can be implemented by 8-to-1 MUX.

5

	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
$\bar{A}$	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
	1	1	0	1	1	0	0	1

 


Application of MUX

 - i) Data Routing:- Used to route data from several source to one destination.
- ii) Logic function generator:- It can be used to implement logic function SOP.
- iii) Parallel to serial converter.
- iv) Control sequencer.


Demultiplex means "one to many". Demultiplexing is a process by which one information is transmitted over one of the several transmitting lines.

De-multiplexer is a combinational ckt which has one input and several output lines. Demultiplexer is a device that transmits one information over any one of several output lines. The total no. of output lines is determined by no. of select lines. A de-MUX is also called a Data Distributor. If 'm' is the number of select lines then number of output lines $n = 2^m$. A basic block diagram of DE-MUX is shown in fig as below —



1-to-4 (1X4) DE-MUX

 1-to-4 DE-MUX has one input and 4-output lines and $(4=2^2)$, 2-select lines.




Above fig. represents the basic block diagram of a 1X4-DE-MUX in which information input line can be transmitted through one of 4-output lines. ~~Real~~ selection of any one output line through which information is to be sent, determined by select line input. For example, if $s_1=0, s_0=0$, then it is clear that information at input line has to transmit through output line Y_0 . This can be understood is better way by following truth table.

Data input	select line input		Output Y			
	s_1	s_0	Y_3	Y_2	Y_1	Y_0
D	0	0	0	0	0	D
D	0	1	0	0	D	0
D	1	0	0	D	0	0
D	1	1	D	0	0	0
			$Y_3 = \bar{s}_1 \bar{s}_0 D$	$Y_2 = \bar{s}_1 s_0 D$	$Y_1 = s_1 \bar{s}_0 D$	$Y_0 = s_1 s_0 D$

Thus, we see that, Depending select & line input, there ~~are~~ may be four outputs as


$$Y_0 = \bar{S}_1 \bar{S}_0 D, Y_1 = \bar{S}_1 S_0 D, Y_2 = S_1 \bar{S}_0 D, Y_3 = S_1 S_0 D$$

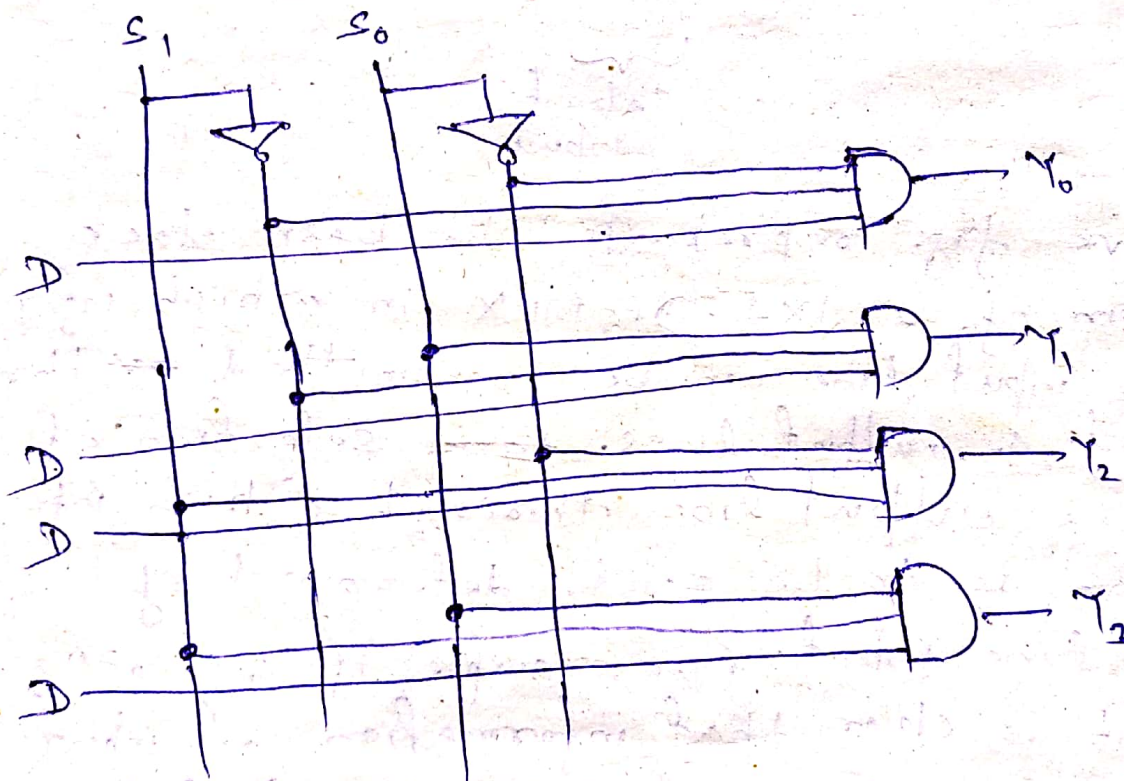The above expression can be implemented by four 3-input AND gates and two NOT gates as below —




1-to-8 DEMUX

 '1x8' DEMUX has one input, 3-select lines and 8-output lines. In accordance to the input to select line $S_2 S_1 S_0$, 1-to-8 DEMUX transmits input data through any one particular output line. A basic block diagram is shown in fig-(A)




The operation of 1x8-DEMUX can be understood in better way by following truth table —

Data Input	Select line input			output							
	s_2	s_1	s_0	Y_7	Y_6	Y_5	Y_4	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0	1	0
2	0	1	0	0	0	0	0	0	1	0	0
3	0	1	1	0	0	0	0	1	0	0	0
4	1	0	0	0	0	0	1	0	0	0	0
5	1	0	1	0	0	1	0	0	0	0	0
6	1	1	0	0	1	0	0	0	0	0	0
7	1	1	1	1	0	0	0	0	0	0	0

 

A decoder is a combinational ckt device that convert an n -bit binary input code (data) into 2^n output lines. "Decoder is similar to DE-MULTIPLEXER" but only the difference is that a DE-MUX has one input line but a decoder has not any data input ~~line~~. A decoder converts an n -bit binary code into 2^n output lines so that each of 2^n output lines is activated only one of the possible combination of inputs. No. of output lines is greater than number of input lines. If the number of input and output lines are equal then it is called converter.

 Basic Binary Decoder - An AND gate can be used as decoder element. This can be understood in better way as that suppose we want to decode a binary code '1001' by a logic ckt. If we want to decode this binary code by using an AND gate, then the middle two bit should be inverted as HIGH because an AND gate gives a HIGH when all of its inputs are at HIGH.



Let us consider the fig.1 where 4-input AND gate has input variables as ABCD = 1001. Input line 'B' and 'C' are connected to two inverters. When we supply 1001, $\gamma = 1$ but other than this binary code 1001, ~~the~~ output of this logic ckt is LOW or '0'. Hence we can say that this logic circuit decodes only 1001.

3-to-8 Decoder

As the name is 3-to-8 decoder, it has three inputs (A, B, C) and eight outputs lines (D_0 to D_7 or γ_0 to γ_7). Based on the combination of three inputs A, B, C, one of 8 output line is activated. This can be understood in better way by following the truth table —

Inputs			Outputs							
A	B	C	D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

12

from the above ~~the~~ truth table, we can write boolean expression for each activated output line as below —

$$D_0 = \bar{A}\bar{B}\bar{C}, D_1 = \bar{A}\bar{B}C, D_2 = \bar{A}B\bar{C}, D_3 = \bar{A}BC$$

$$D_4 = A\bar{B}\bar{C}, D_5 = A\bar{B}C, D_6 = AB\bar{C}, D_7 = ABC.$$

The above all expression can be implemented by a logic ckt using basic gates as below —

