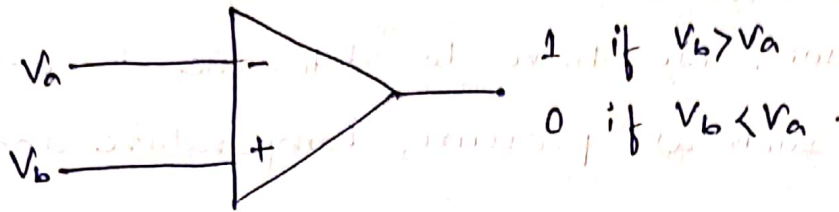


Interfacing instruments and computers:-

- In order to control the machines in our electronic industries, medical instruments or automobiles with microprocessor, we have to determine the values of variables such as pressure, temperature and flow.
 - There are many ways to get electrical signals to digital forms the microcomputer can work with.
 - Talking about analog device, the first step of design involves sensor, which converts physical variables like pressure, temperature, humidity etc. to a proportional voltage or current.
 - The electrical signals from the sensors are quite small, so they must next be amplified and filtered. This is generally done with the help of op-amp circuit.
 - The final step that we can use it to convert to the digital form which can be done by an analog to digital (A/D) converter.
- So, we will discuss the basic operations, interfacing with the microprocessor of both A/D converters and D/A converters.

→ The most elementary form of communication b/w analog and digital device is comparator.



One of the voltages on the comparator i/p's, V_a or V_b will be the variable i/p, and the other a fixed value called a trip, trigger or ~~volt~~ reference voltage.

And, one another comparator is hysteresis comparator using OPAMP (~~discuss~~ already discussed in classes before lockdown).

Digital to Analog Converter (DAC)

Objective:-


→ The digital-to-analog converter known as the D/A converter is a major interface circuit ~~the~~ that forms the bridge between the analog and digital worlds. DACs are the core of many circuits and instruments including digital voltmeters, plotters, oscilloscope displays, and many computer-controlled devices.

②

What is a DAC?

- A DAC is an electronic component that converts digital logic levels into an analog voltage.
- When DAC is used in connection with a computer, this binary no. or digital p/p is called a binary word or computer word. The digits are called bits of the word.

Block diagram:-

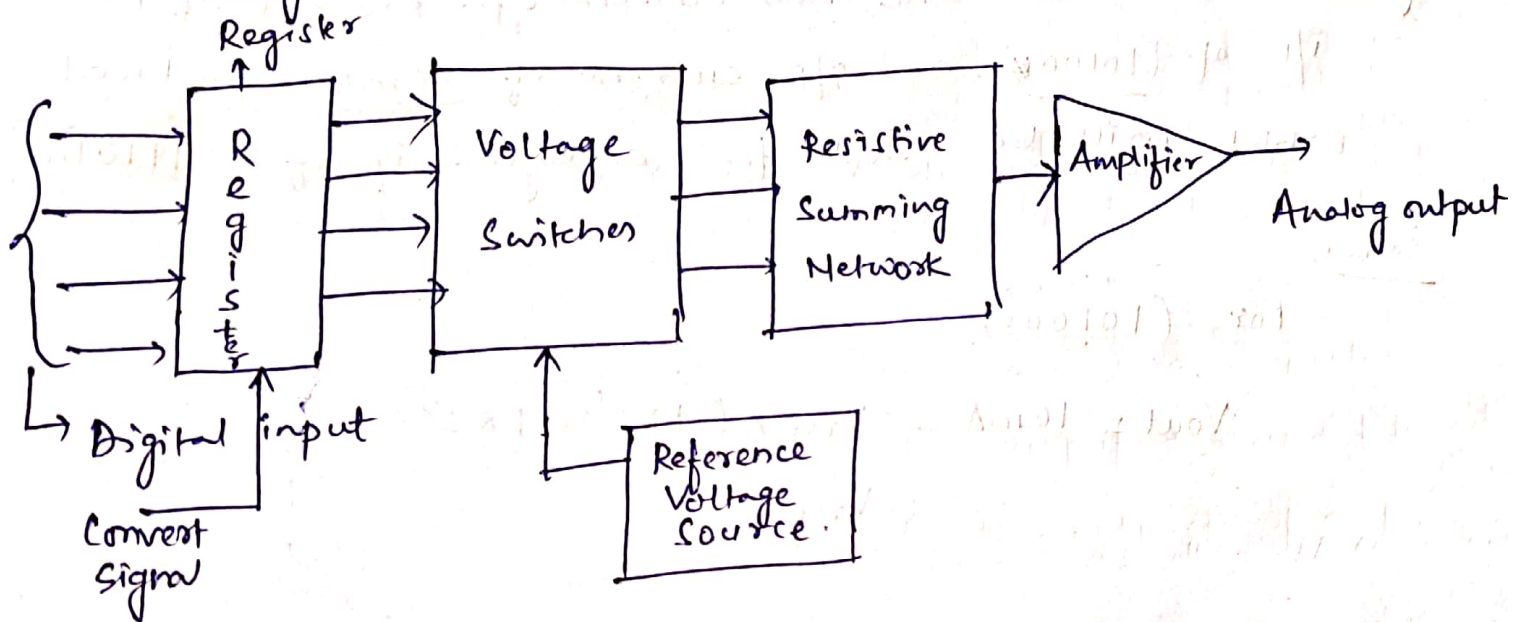

→ In general,

$$V_{out} = V_{ref} \times \text{decimal equivalent of digital i/p.}$$

$$= V_{ref} \times [b_1 2^{-1} + b_2 2^{-2} + \dots + b_n 2^{-n}]$$

V_{ref} = reference voltage.

$b_1, b_2, \dots, b_n = n\text{-bit binary word.}$

* V_{ref} is a constant value for a given DAC.

Eg:- $V_{ref} = 1V$, compute V_{out} for digital i/p = $(1100)_2$ (4)

$$\begin{aligned} 1100 &= 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 0 \times 2^0 \\ &= 8 + 4 + 0 + 0 \\ &= (12)_{10} \end{aligned}$$

$$\therefore V_{out} = \frac{1 \times 12}{1} = 12V$$

eg: ② A 5-bit DAC has a current o/p. For a digital i/p of $(10100)_2$, an o/p current of 10mA is produced. What will be I_{out} for a digital i/p of $(11101)_2$?

Soln:- For $(10100)_2$

$$I_{out_1} = I_{ref} \times (1 \times 2^4 + 1 \times 2^2) = 10\text{mA (given)}$$
$$= I_{ref} \times 20$$

$$I_{ref} = \frac{10}{20}\text{mA} = 0.5\text{mA} \quad \checkmark$$

Now,

$$I_{out_2} = I_{ref} \times (1 \times 2^4 + 1 \times 2^3 + 1 \times 2^2 + 1 \times 2^0)$$
$$= 0.5\text{mA} \times (29)_{10}$$

$$\boxed{I_{out_2} = 14.5\text{mA}}$$

eg: (3) what is the largest value of o/p voltage from an 8-bit DAC that produces 1V for a digital i/p of $(00110010)_2$?

Soln:-

$$\begin{array}{cccccc} & 5 & 4 & 3 & 2 & 1 & 0 \\ (00110010)_2 & = & 1 \times 2^5 & + & 1 \times 2^4 & + & 1 \times 2^1 = (50)_{10} \end{array}$$

A/c to question :- $1V = V_{ref} \times 50$

$$\therefore V_{ref} = \frac{1}{50} = 20 \text{ mV}$$

And, largest o/p will occur for largest i/p i.e. $(11111111)_2$ for 8-bit.

$$(V_{out})_{max} = 20 \text{ mV} \times (255)_{10}$$

$$\left\{ V_{out} = 5.10 \text{ V} \right\}$$

Resolution :-

→ Resolution of D/A converter is defined as the smallest change that can occur in the analog o/p as a result of the change in the digital i/p.

- The resolution is always ~~be~~ equal to the weight of the LSB and is also referred as step size.

→ Input weights :-

MSB		LSB	
D	C	B	A
0	0	0	1
0	0	1	0
0	1	0	0
1	0	0	0

$V_{out}(V)$

1 → A has weight of 1V
 2 → B " " " 2V
 4 → C " " " 4V
 8 → D " " " 8V

My, if 5-bit D/A converter produces $V_{out} = 0.2$ for digital i/p of 00001.

then, (0.2)V is the weight of LSB here.

And weights of other bits will be 0.4, 0.8, 1.6 & 3.2 respectively.

$$\text{And, } V_{out} \text{ for } (11111)_2 = 3.2 + 1.6 + 0.8 + 0.4 + 0.2 = 6.2V$$

⇒ Here, resolution (step size) is same as proportionality factor or reference voltage or current

% resolution :-

$$\% \text{ resolution} = \frac{\text{Step size}}{\text{full scale val (f.s)}} \times 100\%$$

eg:-

for 4-bit i/p ; full-scale is $(1111)_2 = 15V$

and step size is 1V

$$\text{then, } \% \text{ resolution} = \frac{1V}{15V} \times 100\% = 6.67\% \quad \leftarrow$$

8

eg:- A 10-bit DAC has a step size of 10mV. Determine the full-scale output voltage and % resolution.

Sol:-

for 10-bit full scale voltage = $2^{10} - 1 = 1023$

ie 1023 steps of 10mV each.

$$\therefore \text{full-scale o/p voltage} = 1023 \times 10\text{mV} \\ = 1023 \times 0.01 \\ = 10.23\text{V}.$$

$$\% \text{ resolution} = \frac{10\text{mV}}{10.23\text{V}} \times 100\% \\ = 0.09 \approx 0.1\% \checkmark$$

* % resolution can also be calculated as:-

$$\% \text{ resolution} = \frac{1}{\text{total no. of steps}} \times 100\%$$


$$\text{Here, } \% \text{ res} = \frac{1}{2^{10} - 1} \times 100$$

$$\% \text{ res} = 0.09 \approx 0.1\% \checkmark$$

D/A converter circuitry:-

(9)

1. Binary weighted resistor DAC:-

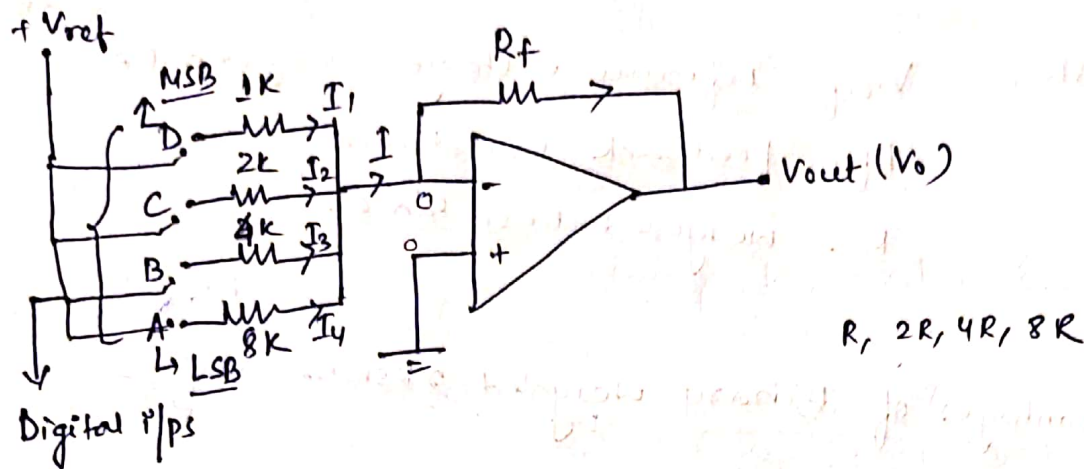

→ This is basic circuit for 4-bit DAC. i/p's A, B, C, D are binary i/p's which is applied to opamp. opamp is employed here as summing amplifier.

Analysis:-

$$\frac{0 - V_0}{R_f} = I \Rightarrow V_0 = -I R_f$$

$$I = I_1 + I_2 + I_3 + I_4$$

$$I_1 = \frac{V_{ref}}{R} \times b_0 \quad I_2 = \frac{V_{ref}}{2R} \times b_1 \quad I_3 = \frac{V_r}{4R} \times b_2$$

$$I_4 = \frac{V_r}{8R} \times b_3$$

$$\Rightarrow V_0 = -I R_f$$

$$= -R_f [I_1 + I_2 + I_3 + I_4]$$

$$= -R_f \left[\frac{V_r}{R} \underset{\text{MSB}}{b_0} + \frac{V_r}{2R} b_1 + \frac{V_r}{4R} b_2 + \frac{V_r}{8R} \underset{\text{LSB}}{b_3} \right]$$

$$\left\{ V_0 = -\frac{V_r R_f}{R} \left[\frac{b_0}{2^0} + \frac{b_1}{2^1} + \frac{b_2}{2^2} + \frac{b_3}{2^3} \right] \right\}$$

∴ general formula becomes:-

(10)

$$V_0 = -\frac{V_{ref} R_f}{R} \left[\frac{b_0}{2^0} + \frac{b_1}{2^1} + \dots + \frac{b_n}{2^{n-1}} \right]$$

where, V_{ref} = reference voltage for given DAC.

R_f = feedback resistance.


R = weighted resistance.

Disadvantages of Binary weighted resistor DAC:-


1. The difference b/w the resistance values corresponding to LSB and MSB will increase as the no. of bits present in the i/p increases.
2. It is difficult to design more accurate and high value of resistors as the digital i/p increases.

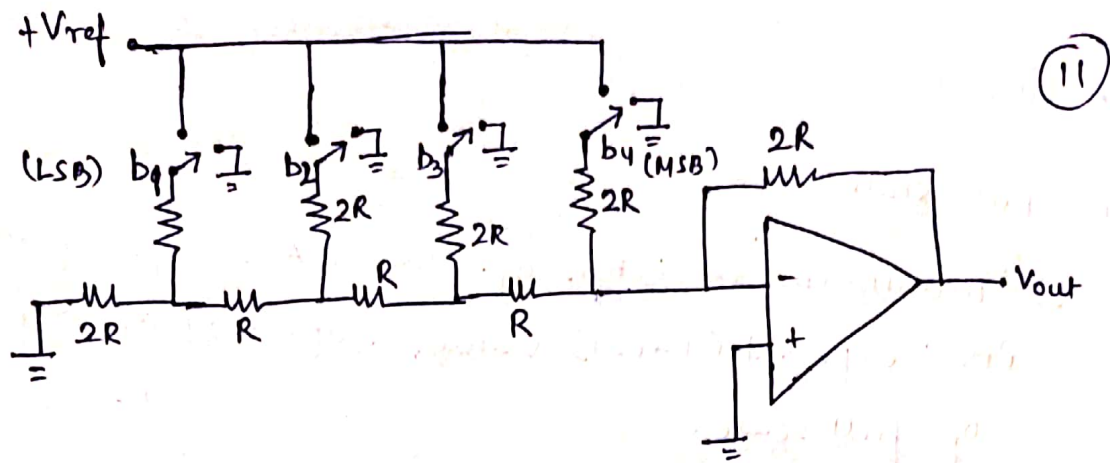2. R/2R Ladder DAC :-

- This DAC will overcome the drawbacks of above DAC as only two values of resistors will be used (R and $2R$).



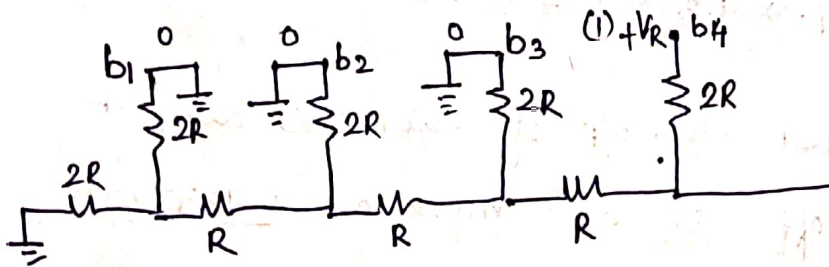→ The binary i/p control the states of switches.
 for example if we take $(1000)_2$ as digital i/p
 then, R-2R ladder becomes:-



Here,

$$V_o = -\frac{R_f}{R} \times V_{ref} \left[\frac{b_1}{2^4} + \frac{b_2}{2^3} + \frac{b_3}{2^2} + \frac{b_4}{2^1} \right]$$

$$\text{or, } \left\{ V_o = -\frac{R_f}{R} \times V_{ref} \left[\frac{b_1}{2^n} + \frac{b_2}{2^{n-1}} + \dots + \frac{b_n}{2^1} \right] \right\}$$

Accuracy:-

(12)

1. Full scale error:-

- maximum deviation of the DAC's o/p from its expected (ideal) value, expressed as a % of full scale.

For example, assume that DAC has a accuracy of $\pm 0.01\%$ f.s. and if the full scale value is $9.375V$.

then,

$$\pm 0.01\% \times 9.375 = \pm 0.9375 \text{ mV}$$

which means that the o/p of this DAC can, at any time, be off by as much as 0.9375 mV from its expected o/p.

2. Linearity error:-

- maximum deviation in the step size from the ideal step size.

For example, the DAC has an expected step size of $0.625V$. If this DAC has a linearity error of ± 0.01 f.s., this would mean that the actual step size could be off by as much as

$$\pm 0.01 \times 9.375 = 0.9375 \text{ mV}$$