

3. VERIFICATION OF NORTON'S THEOREM


AIM: To verify Norton's theorem for the given circuit.

APPARATUS REQUIRED:


S.No	Name Of The Equipment	Range	Type	Quantity
1	Voltmeter	(0-20)V	Digital	1 NO
2	Ammeter	(0-20)mA	Digital	1 NO
3	RPS	0-30V	Digital	1 NO
4	Resistors	10K Ω , 1K Ω		1 NO
		2.2 Ω		1 NO
		330 Ω		1 NO
5	Breadboard	-	-	1 NO
6	DMM	-	Digital	1 NO
7	Connecting wires			Required number

CIRCUIT DIAGRAM:

GIVEN CIRCUIT:

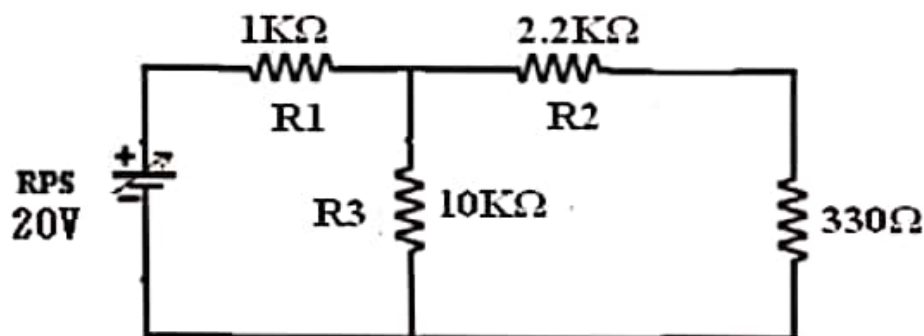

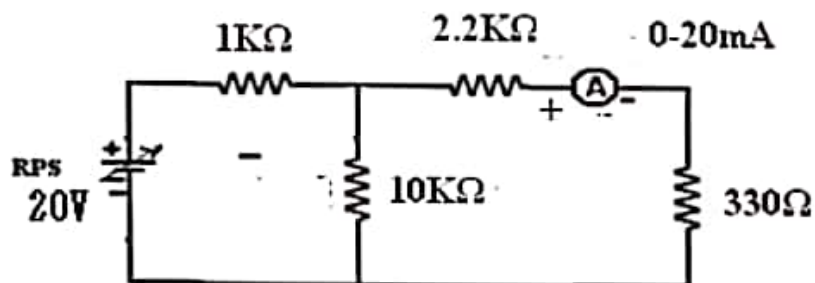PRACTICAL CIRCUIT DIAGRAMS: TO FIND I_L :



FIG(1)

TO FIND I_N :


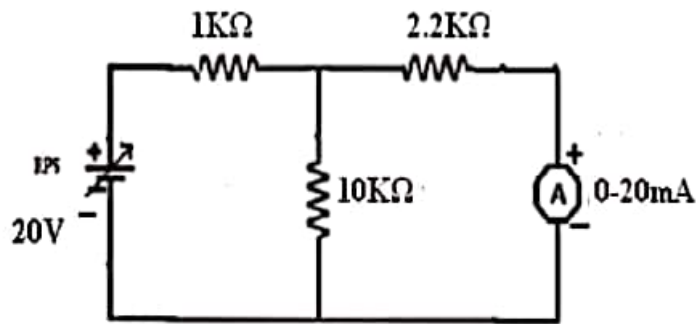


fig (2)

TO FIND R_N :

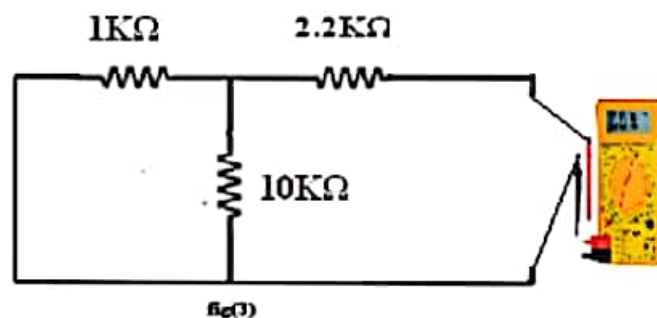

fig(3)

THEORY:

NORTON'S THEOREM:

Norton's theorem states that in a lumped, linear network the equivalent circuit across any branch is replaced with a current source in parallel a resistance. Where the current is the Norton's current which is the short circuit current though that branch and the resistance is the Norton's resistance which is the equivalent resistance across that branch by replacing all the sources with their internal resistances

for source current,

$$I = \frac{V}{R} = \frac{V(R_2 + R_3)}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

FOR NORTON's CURRENT

$$I_N = I \times \frac{R_1}{R_1 + R_2} = \frac{V R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

Load Current through Load Resistor

$$I_L = I_N \times [R_N / (R_N + R_L)]$$

PROCEDURE:

1. Connect the circuit as per fig (1)
2. Adjust the output voltage of the regulated power supply to an appropriate value (Say 20V).
3. Note down the response (current, I_L) through the branch of interest i.e. AB (ammeter reading).
4. Reduce the output voltage of the regulated power supply to 0V and switch-off the supply.
5. Disconnect the circuit and connect as per the fig (2).
6. Adjust the output voltage of the regulated power supply to 20V.
7. Note down the response (current, I_N) through the branch AB (ammeter reading).
8. Reduce the output voltage of the regulated power supply to 0V and switch-off the supply.
9. Disconnect the circuit and connect as per the fig (3).
10. Connect the digital multimeter (DMM) across AB terminals and it should be kept in resistance mode to measure Norton's resistance(R_N).


TABULATION FOR NORTON'S THEOREM:

THEORITICAL VALUES	PRACTICAL VALUES
$I_N=$ $R_N=$ $I_L=$	$I_N=$ $R_N=$ $I_L=$


RESULT:

EXERCISE QUESTIONS:

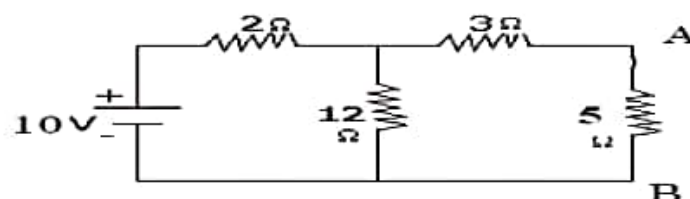1. Determine current through current 5 ohms resistor using Norton's theorem.



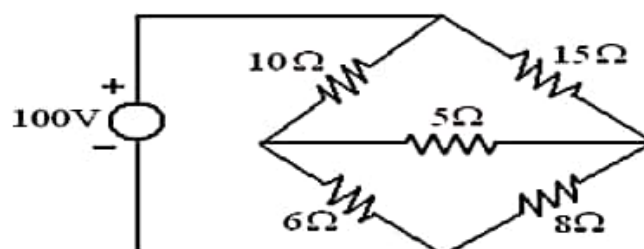2. Determine the current flowing through the 5 ohm resistor using Thevenin's theorem



VIVA QUESTIONS:

- 1) The internal resistance of a source is 2 Ohms and is connected with an External Load Of 10 Ohms Resistance. What is R_{th} ?
- 2) In the above question if the voltage is 10 volts and the load is of 50 ohms. What is the load current and V_{th} ? Verify I_L ?
- 3) If the internal resistance of a source is 5 ohms and is connected with an External Load Of 25 Ohms Resistance. What is R_{th} ?
- 4) In the above question if the voltage is 20V and the load is of 50 Ohms. What is the load current and I_N ? Verify I_L ?