

## 13.SCHERING'S BRIDGE

### Objective:

To determine the unknown value of capacitance using schering's bridge.

### Apparatus:

Software: Lab view software.


Hardware:	Name of the apparatus	Quantity
	Bread board	1 No
	Resistors	2 No
	Variable Resistor	1 No
	Capacitors	3No
	Digital Multimeter	1 No

### Theory:

Schering bridge is one of the most important of the a.c. bridge. It is extensively used in measurement of capacitance.

At balance,  $\{r_1 + 1/(j\omega C_1)\} \{R_4/(1+j\omega C_4 R_4)\} = R_3/(j\omega C_2)$
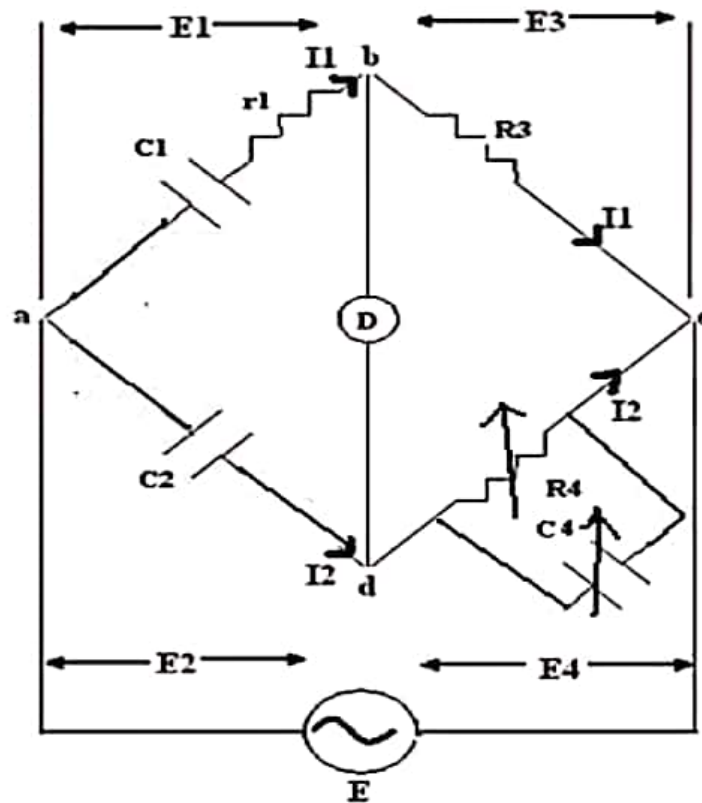
$$\{r_1 + 1/(j\omega C_1)\} R_4 = R_3/(j\omega C_2) * \{(1+j\omega C_4 R_4)\}$$



$$r_1 R_4 - \{ (jR_4) / (\omega C_1) \} = \{ (-jR_3) / (\omega C_2) \} + \{ (R_3 R_4 C_4) / (C_2) \}$$

Equating real and imaginary terms,

$$r_1 = R_3 C_4 / C_2 \quad \text{and} \quad C_1 = C_2 R_4 / R_3$$


Procedure:

1. Connect the circuit as shown in the figure.
2. Select any value of  $C_1$ .
3. Connect the multimeter between ground and output of imbalance amplifier.
4. Vary  $R_4$  and  $C_4$  from minimum position, in clockwise direction.
5. If the selection of  $C_1$  is correct the balance point can be obtained at minimum position.

6. If that is not the case, select another  $C_1$ .
7. Calculate the Capacitance by substituting known values.


Observation:

$C_4$	$C_1$	$C_2$	$R_3$	$R_4$

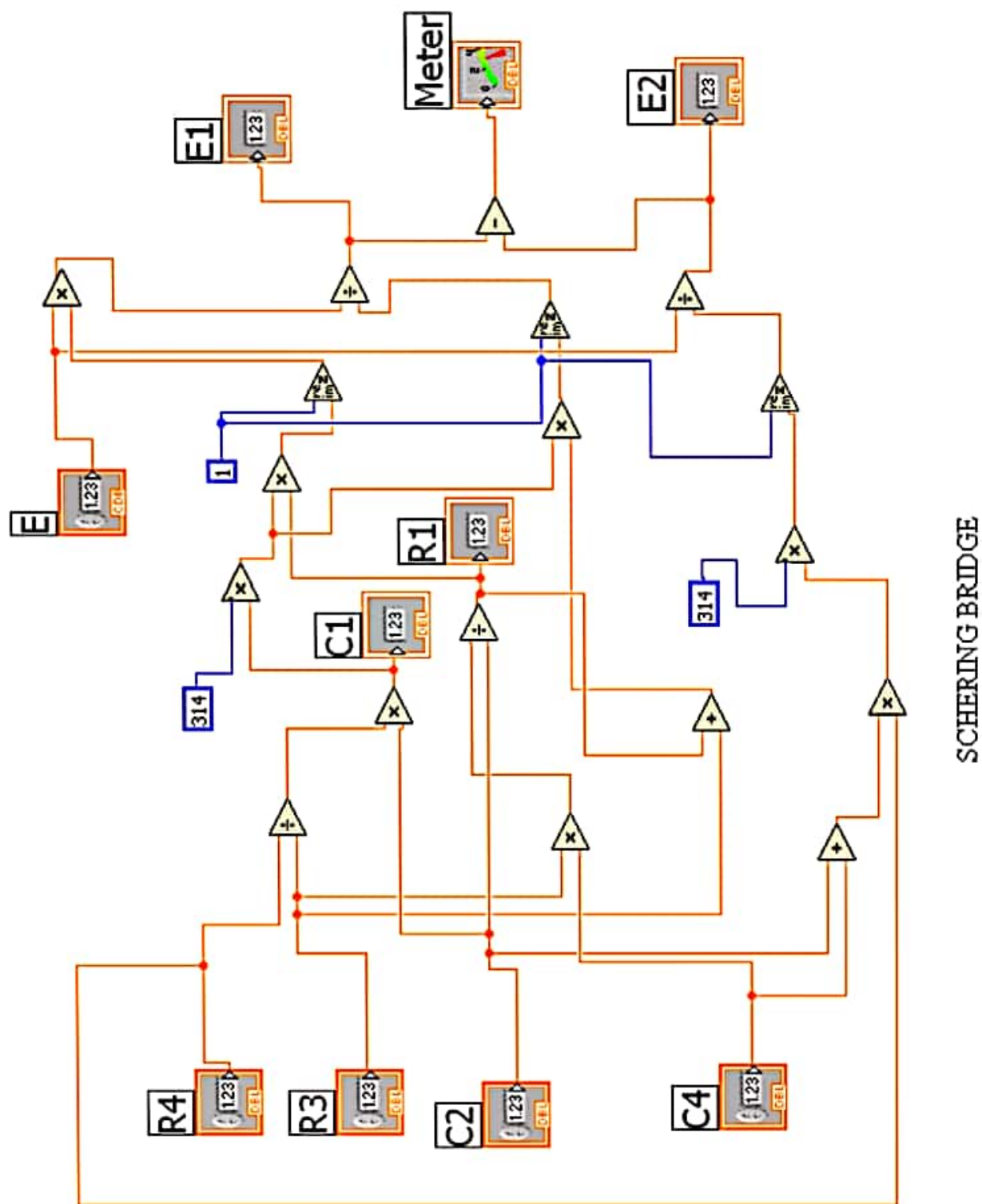

SCHERING BRIDGE

Front Panel in Labview:

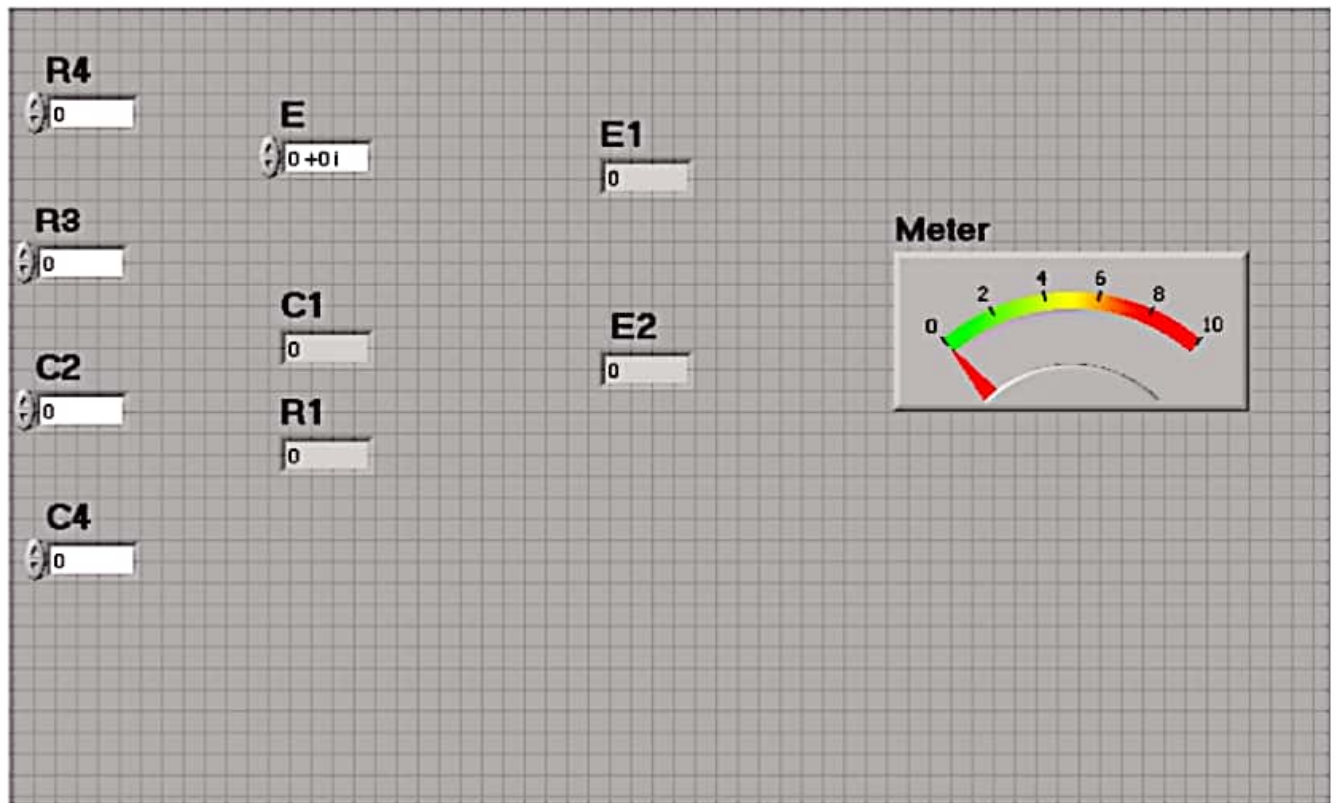

Result:

Hence the balanced condition of schering bridge is obtained and unknown value of capacitance is found.