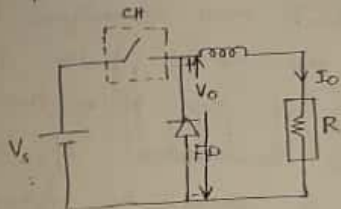


17/9/2011


## Choppers

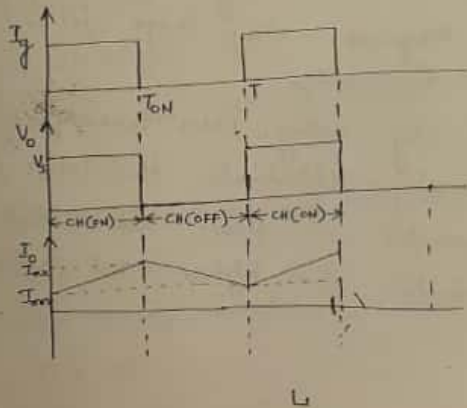(1)

Fixed DC  $\rightarrow$  Variable DC  
stepdown chopper ( $V_o < V_s$ )



$\rightarrow$  Inductance is added to reduce the ripple in the load current



L


(2)

Mode 1: 0 to  $T_{ON}$

CH is ON

$$V_o = V_s$$

L will store energy

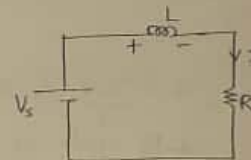


$$V_s = RI + L \frac{di}{dt}$$



$$P_{\text{source}} \rightarrow P_{\text{load}} \quad \left( \frac{1}{2} Li^2 + I^2 R \right)$$

Mode 2:  $T_{ON}$  to T

CH is OFF

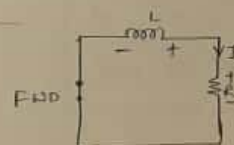

$$\frac{1}{2} Li^2 \rightarrow I^2 R$$

$$\rightarrow V_o = \frac{1}{T} \int_0^{T_{on}} V_s \cdot dt$$

$$= V_s \cdot \frac{T_{on}}{T}$$


$$V_o = \alpha V_s$$

where,  $\alpha = \frac{T_{on}}{T}$  is called duty cycle of chopper.


$$\rightarrow V_{or}^2 = \frac{1}{T} \int_0^{T_{on}} V_s^2 \cdot dt$$

$$= V_s^2 \cdot \frac{T_{on}}{T}$$
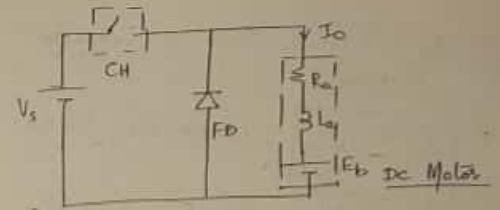
$$\Rightarrow V_{or} = \sqrt{V_s^2 \alpha} = \sqrt{\alpha} \cdot V_s$$



#### ① Continuous Conduction

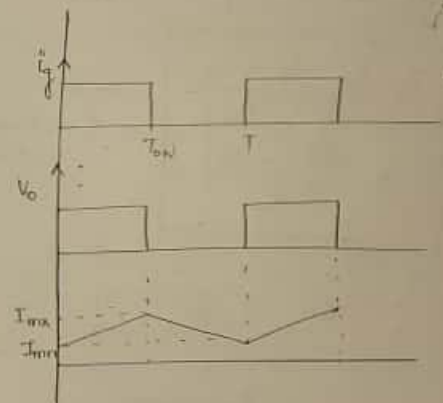

$$\begin{aligned} V_o &= \alpha V_s \\ V_{or} &= \sqrt{\alpha} V_s \end{aligned} \rightarrow R, R_L \text{ \& \& RLE (Continuous Conduction)}$$

$$I_0 = \frac{V_0}{R}$$

$$I_0 = \frac{\alpha V_s}{R} \rightarrow R, RL \text{ loads}$$

→ Inductor changes only the ripple but not average value of current.

$$I_0 = \frac{V_0 - E_b}{R_a} \rightarrow RLE \text{ (continuous conduction)}$$

$$= \frac{\alpha V_s - E_b}{R_a}$$

$$I_{mx} = \frac{V_s}{R_a} \left[ \frac{1 - e^{-T_{on}/T_a}}{1 - e^{-T/T_a}} \right] - \frac{E_b}{R_a}$$

where,  $T_a = \frac{L_a}{R_a}$

$$I_{mn} = \frac{V_s}{R_a} \left[ \frac{e^{T_{on}/T_a} - 1}{e^{T/T_a} - 1} \right] - \frac{E_b}{R_a}$$

$$\text{Ripple current} = I_{mx} - I_{mn}$$

$$= \frac{V_s}{R_a} \left[ \frac{1 - e^{-T_{on}/T_a}}{1 - e^{-T/T_a}} - \frac{e^{T_{on}/T_a} - 1}{e^{T/T_a} - 1} \right]$$

$$= \frac{V_s}{R_a} \left[ \frac{1 - e^{-T_{on}/T_a}}{1 - e^{-T/T_a}} - \frac{(e^{+T_{on}/T_a} - 1) e^{-T/T_a}}{1 - e^{-T/T_a}} \right]$$

$$= \frac{V_s}{R_a} \left[ \frac{1 - e^{-T_{on}/T_a} + e^{-T/T_a}}{1 - e^{-T/T_a}} \right]$$

$$\begin{aligned}
 &= \frac{V_s}{R_a} \left[ \frac{\left(1 - e^{-\frac{T_{on}}{T_a}}\right) - \left(e^{\frac{T_{on}}{T_a}} \cdot e - 1\right) e^{-\frac{T_{off}}{T_a}}}{\left(1 - e^{-T/T_a}\right)} \right] \quad (7) \\
 &= \frac{V_s}{R_a} \left[ \frac{1 - e^{-T_{on}/T_a} - \left(1 - e^{-T_{on}/T_a}\right) e^{-T_{off}/T_a}}{\left(1 - e^{-T/T_a}\right)} \right] \\
 &= \frac{V_s}{R_a} \frac{\left[1 - e^{-T_{on}/T_a}\right] \left[1 - e^{-T_{off}/T_a}\right]}{\left(1 - e^{-T/T_a}\right)} \\
 &= \frac{V_s}{R_a} \frac{\left[1 - e^{-\alpha T/T_a}\right] \left[1 - e^{-(1-\alpha)T/T_a}\right]}{\left[1 - e^{-T/T_a}\right]} \rightarrow (8)
 \end{aligned}$$

For getting the condition for max. ripple current, differentiate the above eqn. w.r.t  $\alpha$  & equate it to zero.

Then we get,

$$* \alpha = 0.5 \quad \left( \text{condition for max. ripple current} \right)$$

$\Rightarrow$  (8) becomes,

$$\Delta I_{max} = \frac{V_s}{R_a} \frac{\left[1 - e^{-0.5T/T_a}\right] \left[1 - e^{-0.5T/T_a}\right]}{\left[1 - e^{-T/T_a}\right]}$$

$$= \frac{V_s}{R_a} \frac{\left(1 - e^{-0.5T/T_a}\right)^2}{\left(1 - \left(e^{-0.5T/T_a}\right)^2\right)}$$

$$= \frac{V_s}{R_a} \frac{\left(1 - e^{-0.5T/T_a}\right)}{\left(1 + e^{-0.5T/T_a}\right)}$$

$$= \frac{V_s}{R_a} \cdot \tanh\left(\frac{T}{4T_a}\right)$$

$$\approx \frac{V_s}{R_a} \cdot \left(\frac{T}{4T_a}\right) \quad \left[ \because \tanh x \approx x \text{ for small value of } x \right]$$

$$\approx \frac{V_s}{R_a} \cdot \frac{T}{4 \cdot \frac{L_a}{R_a}}$$


(9)

$$(\Delta I)_{\max} \approx \frac{V_s}{4fL_a}$$

- The ripple current is inversely proportional to the load inductance & chopping frequency.
- Thus by increasing the chopping frequency, we can reduce the ripple in the current.
- Therefore SMPS works based on Chopper principle.
- With the advancement of high switching speed devices like MOSFET, SMPS are popularly used now-a-days for getting very good quality of dc power supply.

(10)

### Discontinuous conduction

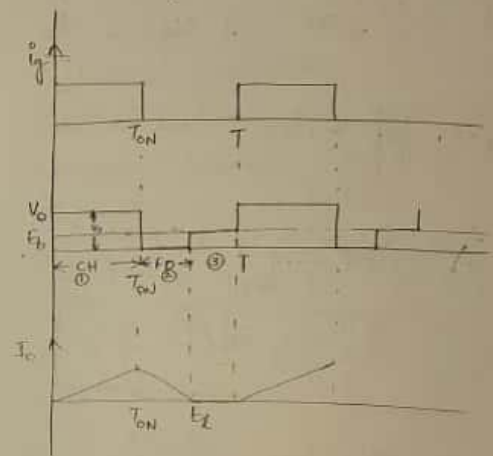

$t_x$  = Extinction time

→ Extinction time is the time at which inductor releases its complete energy.

$$t_x = T_{ON} + \frac{L}{V_s - E} \ln \left[ 1 + \frac{V_s - E}{E} (1 - e^{-T_{ON}/\tau_a}) \right]$$

$$V_o = \frac{1}{T} \left[ \int_0^{T_{ON}} V_s \cdot dt + \int_{T_{ON}}^{t_x} 0 \cdot dt + \int_{t_x}^T E_b \cdot dt \right] \quad (11)$$

$$= \frac{1}{T} \left[ V_s \cdot T_{ON} + E_b (T - t_x) \right]$$

$$= V_s \cdot \left( \frac{T_{ON}}{T} \right) + E_b \left( \frac{T - t_x}{T} \right)$$

$$V_o = \alpha V_s + E_b \left( 1 - \frac{t_x}{T} \right)$$

$$V_{or}^2 = \frac{1}{T} \left[ \int_0^{T_{ON}} V_s^2 \cdot dt + \int_{t_x}^T E_b^2 \cdot dt \right]$$

$$V_{or} = \left[ \frac{1}{T} \left[ V_s^2 \cdot T_{ON} + E_b^2 \cdot (T - t_x) \right] \right]^{1/2}$$

$$= \left[ \alpha V_s^2 + E_b^2 \left( 1 - \frac{t_x}{T} \right) \right]^{1/2}$$

Duty cycle limit for continuous conduction: (12)

Let  $\alpha'$  be the duty cycle limit for continuous conduction.

(Here  $\alpha'$  is the duty cycle at the boundary between continuous & discontinuous conduction)

$$I_{mn} = \frac{V_s}{R_a} \left[ \frac{e^{T_{ON}/T_a} - 1}{e^{T/T_a} - 1} \right] - \frac{E_b}{R_a}$$

$$= 0$$

$$\Rightarrow \frac{e^{T_{ON}/T_a} - 1}{e^{T/T_a} - 1} = \frac{E_b}{V_s}$$

$$\text{Let } \frac{E_b}{V_s} = m$$

$$\Rightarrow e^{T_{ON}/T_a} - 1 = m(e^{T/T_a} - 1)$$

$$\therefore e^{T_{ON}/T_a} = 1 + m(e^{T/T_a} - 1)$$



(13)

$$\frac{T_{ON}'}{T_a} = \ln [1 + m(e^{T/T_a} - 1)]$$


$$\Rightarrow T_{ON}' = T_a \ln [1 + m(e^{T/T_a} - 1)]$$

$$\Rightarrow \alpha' = \frac{T_{ON}'}{T} = \frac{T_a}{T} \ln [1 + m(e^{T/T_a} - 1)]$$


If  $\alpha < \alpha' \Rightarrow$  Discontinuous Conduction  
 $\alpha > \alpha' \Rightarrow$  Continuous Conduction

(14)

step up chopper

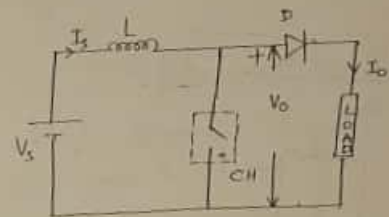

Mode 1: 0 to  $T_{ON}$

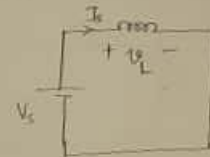


$$V_s = V_L$$

$$V_s = L \frac{dI_s}{dt}$$

$$\int dI_s = \int \frac{V_s}{L} dt$$

$$I_s = \frac{V_s}{L} t + K \quad (I_{mo})$$

Mode 2:

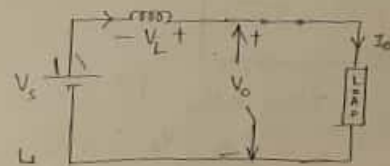


$$V_o = V_s + V_L$$

L is releasing energy

$$I_s = I_o$$
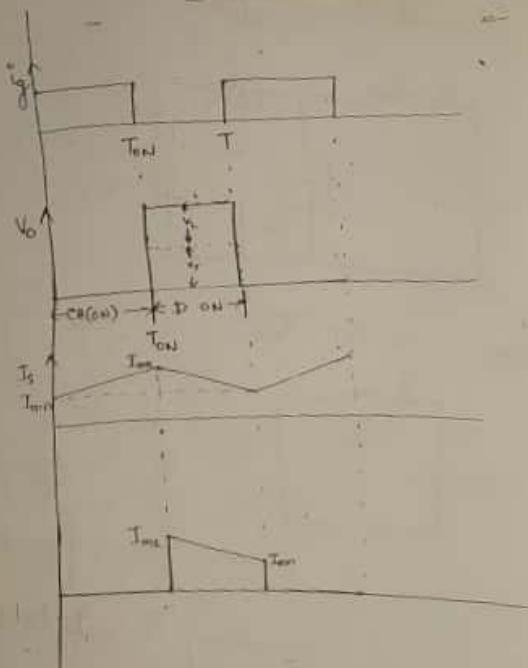
$$V_L = L \left( \frac{di}{dt} \right) \text{ and}$$



$$V_o = \frac{V_s}{1-\alpha}$$


Since  $\alpha < 1$ ,  $V_o > V_s$

$$V_o > \frac{V_s}{L}$$

with regenerative braking  
→ It is used in Regenerative braking of DC motor.

### Chopper fed DC drives

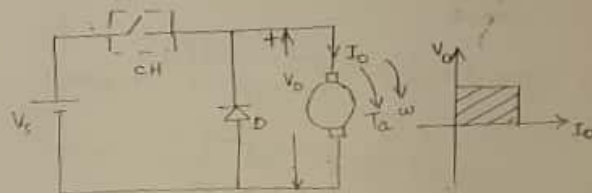1. First Quadrant chopper (or Type A chopper) Stepdown chopper



$$V_o = \alpha V_s$$

$I_o$  is +ve

⇒ P is +ve i.e.,  $P_{\text{source}} \rightarrow P_{\text{load}}$   
Elec → Mech

⇒ H/w Motoring

$$V_o = E_b + I_o R_a$$

$$\omega = \frac{V_o}{K} - \frac{R_a T_a}{K}$$



$$K \rightarrow \frac{V \cdot \text{sec} / \text{rad}}{\text{Nm/A}}$$

$$\omega = \frac{2V_s}{K} - \frac{R_a \cdot I_a}{K^2}$$

8. Second Quadrant Chopper:  
(Type B chopper)




Before  $t=0$ , the m/c is running at rated speed  $\omega_r$

Before  $t=0$ ,  $\frac{1}{2} I_a \omega_r^2$  energy


L

(17)

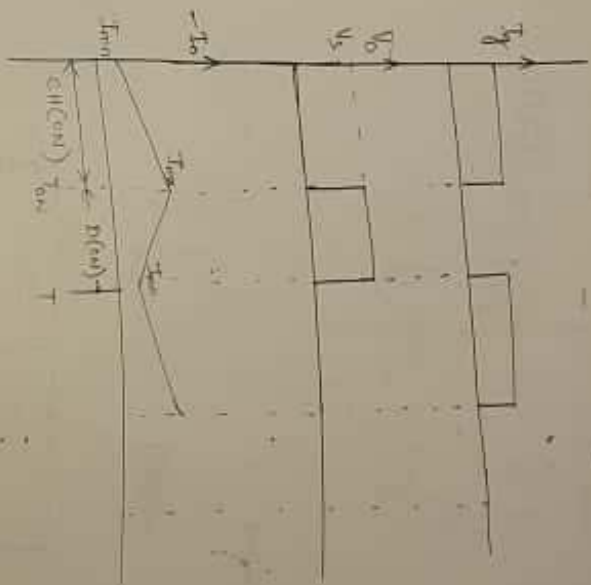

Mode 1:

At  $t=0$  sec, chopper is switched ON

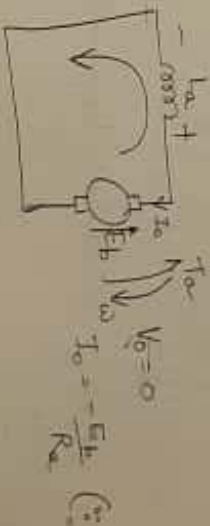


(18)

$$T_a \propto \phi I_a$$

$\Rightarrow T_a$  reverses immediately

$$\frac{1}{2} J \omega_r^2 \rightarrow \frac{1}{2} I_a^2$$


Mode 2:

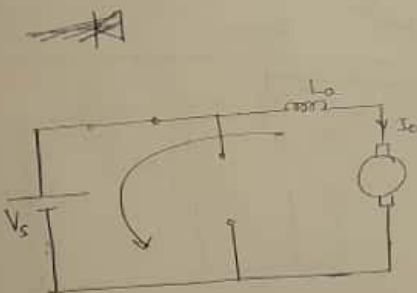

$$\frac{1}{2} L_o I_o^2 \rightarrow \frac{V_s I_o}{P_{\text{source}}}$$

Hence, Regenerative braking

(19)

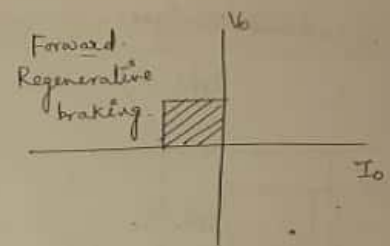

$$V_o = \frac{1}{T} \int_{T_{ON}}^T V_s dt$$

$$= \frac{T - T_{ON}}{T} V_s$$



$$V_o = (1-d) V_s \Rightarrow V_s = \frac{V_o}{1-d}$$

$$\Rightarrow V_s > V_o$$

$\rightarrow$  This <sup>alone</sup> can't be used in practical applications  
i.e., It is not stand alone chopper.

(20)

## Two Quadrant chopper (Type c)

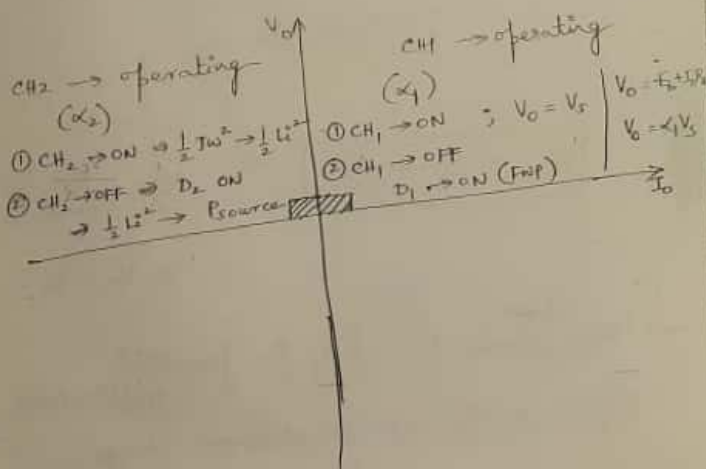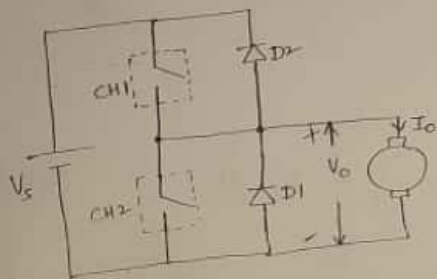

## Four Quadrant chopper

