

## Exp- 06. WEIN BRIDGE OSCILLATOR


### OBJECTIVE::


To study and calculate frequency of oscillations of Wein Bridge Oscillator and compare it with theoretical value.

### APPARATUS:

MULTISIM 2007 SOFTWARE PC

### CIRCUITDIAGRAM:

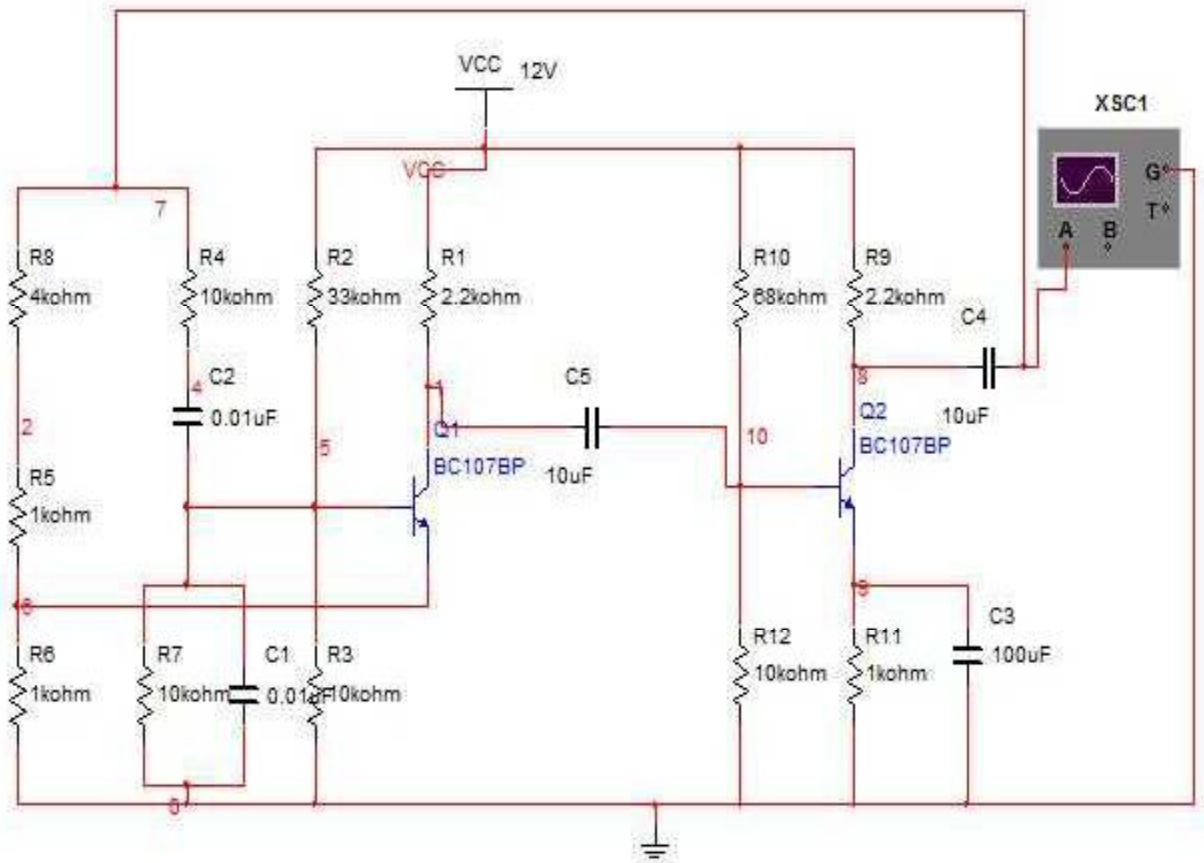

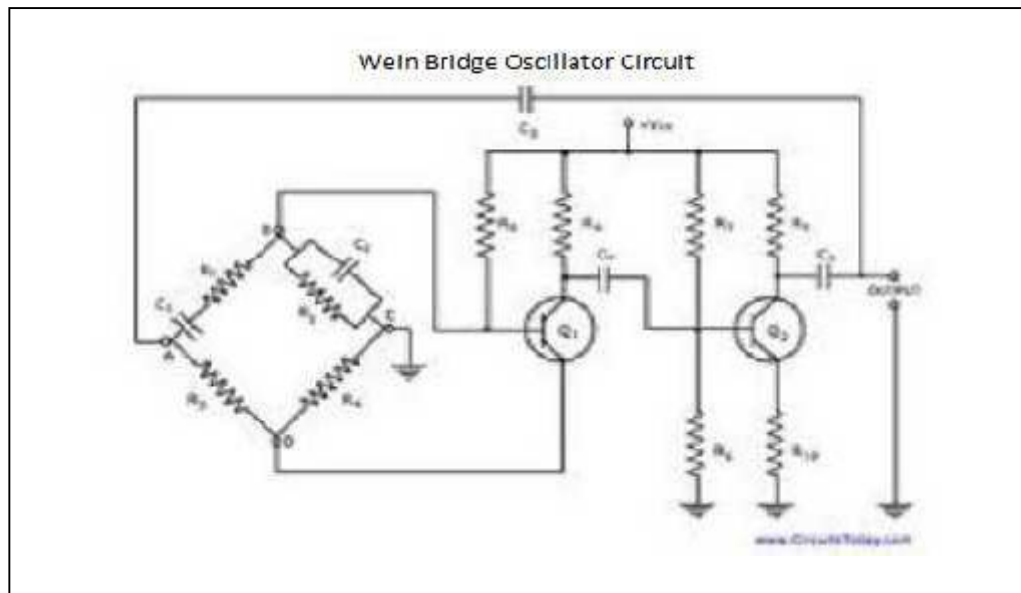

### Circuit highlighting the Bridge formation.

### THEORY:

The Wein Bridge oscillator is a standard circuit for generating low frequencies in the range of 10 Hz to 1MHz. The method used for getting +ve feedback in Wein Bridge oscillator is to use two stages of an RC-coupled amplifier. Since one stage of the RC-coupled amplifier introduces a phase shift of 180 deg, two stages will introduce a phase shift of 360 deg. At the frequency of oscillations  $f$  the +ve feedback network shown in fig makes the input & output in the phase. The formula for frequency of oscillations is given as

$$f = \frac{1}{2\pi R_1 C_1 R_2 C_2}$$

If  $R_1 C_1 = R_2 C_2 = RC$ , then  $f = 1/2\pi RC$

$$R_4 C_2 R_7 C_1$$

### PROCEDURE:

1. Start MULTISIM. A blank circuit window will appear on the screen along with a component tool bar.
2. Using component tool bar place all the components on the circuit window and wire the circuit.
3. Feed the output of the oscillator to a C.R.O by making adjustments in the Potentiometer connected in the +ve feedback loop, try to obtain a stable sine wave.
4. Measure the time period of the waveform obtained on CRO. & calculate the Frequency of oscillations.
5. Repeat the procedure for different values of capacitances.

### **OBSERVATION:**


Given  $R=10k\Omega$ ,  $C=0.01\mu F$

$$f_T = 1/2\pi RC$$

$$f_P = \frac{1}{T} =$$

Amplitude,  $V_0 =$  **MODEL**

### **WAVE FORMS:**

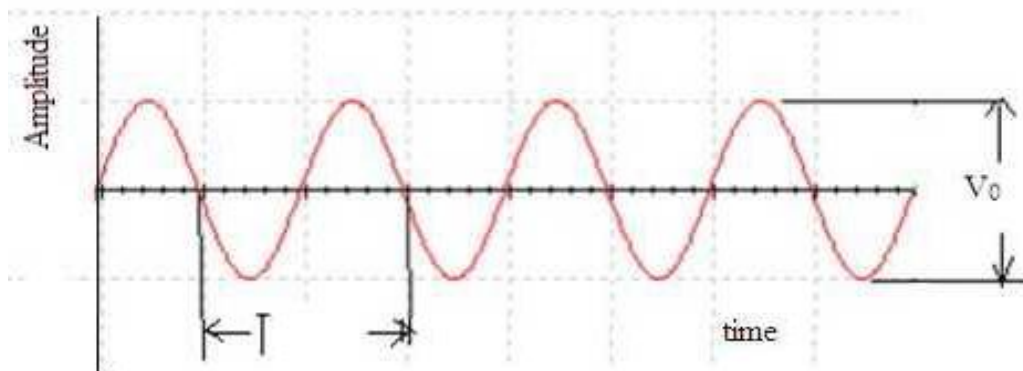

### **RESULT:**

The frequency of oscillations of the Wein Bridge oscillator is calculated and is verified.