

## 12.WHEATSTONE'S BRIDGE

### Objective:

To determine the unknown value of resistance using wheatstone's bridge.

### Apparatus:

Software: Lab view software.


Hardware:	Name of the apparatus	Quantity
	Bread board	1 No
	Resistors	3 No
	Variable Resistor	1 No
	Digital Multimeter	1 No

### Theory :

The bridge consists of four resistive arms together with a source of e.m.f. and null detector. The galvanometer is used as a null detector. When the bridge is balanced, the galvanometer carries zero current and it does not show any deflection. Thus bridge works on the principle of null deflection or null indication.

To have zero current through galvanometer, the points B and D must be at the same potential. Thus potential across arm AB must be same as the potential across arm AD.

Thus  $I_1 R_1 = I_2 R_4$

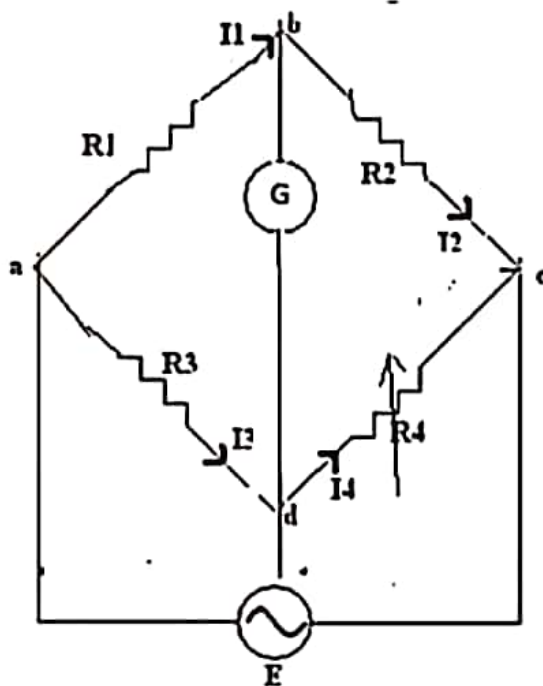

As galvanometer current is zero,

$$I_1 = I_3 \text{ and } I_2 = I_4$$

Considering the battery path under balanced condition,

$$I_1 = I_3 = E / (R_1 + R_2)$$

$$\text{And } I_2 = I_4 = E / (R_3 + R_4)$$

$$\text{Therefore } R_1(R_3 + R_4) = R_4(R_1 + R_2)$$

$$R_1 = R_2 R_4 / R_3$$


Procedure:

1. Connect the circuit as shown in the figure.
2. Select any value of  $R_1$ .
3. Connect the multimeter between ground and output of imbalance amplifier.
4. Vary  $R_3$ , from minimum position, in clockwise direction.
5. If the selection of  $R_1$  is correct the balance point can be obtained at minimum position.
6. If that is not the case, select another  $R_1$ .
7. Calculate the Resistance  $R_1$  by substituting known values.

**Observation:**


S.No	R <sub>1</sub>	R <sub>2</sub>	R <sub>3</sub>	R <sub>4</sub>

Block Diagram in Labview:

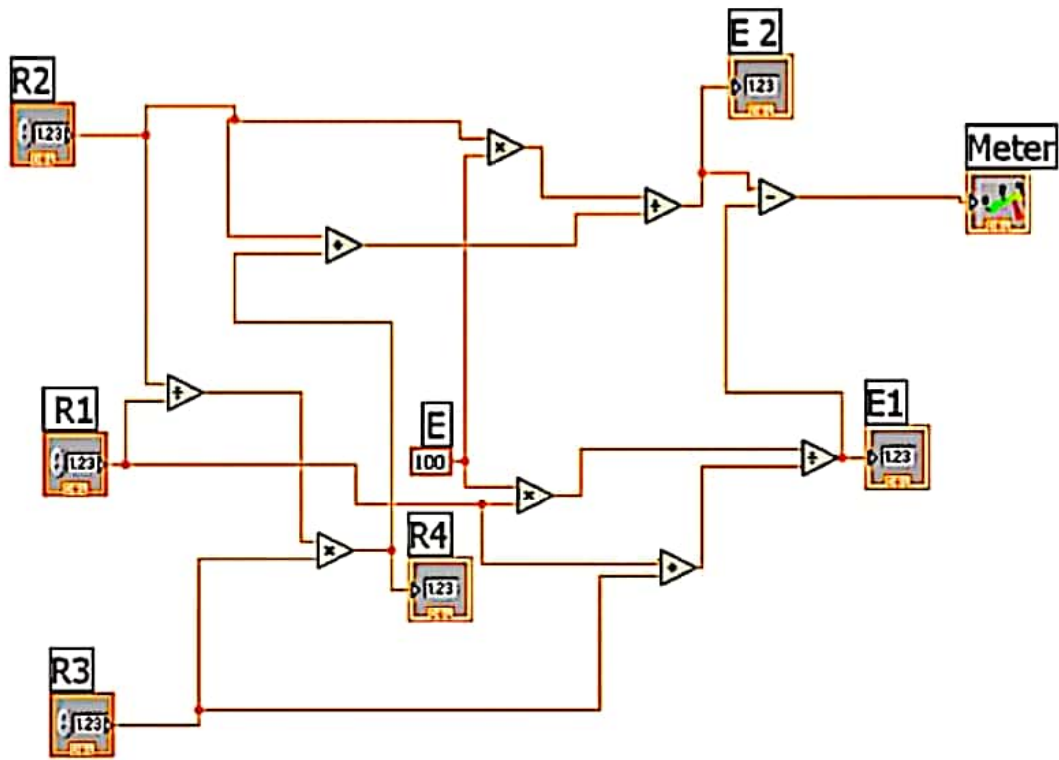

WHEATSTONE'S BRIDGE

Front Panel in Labview:

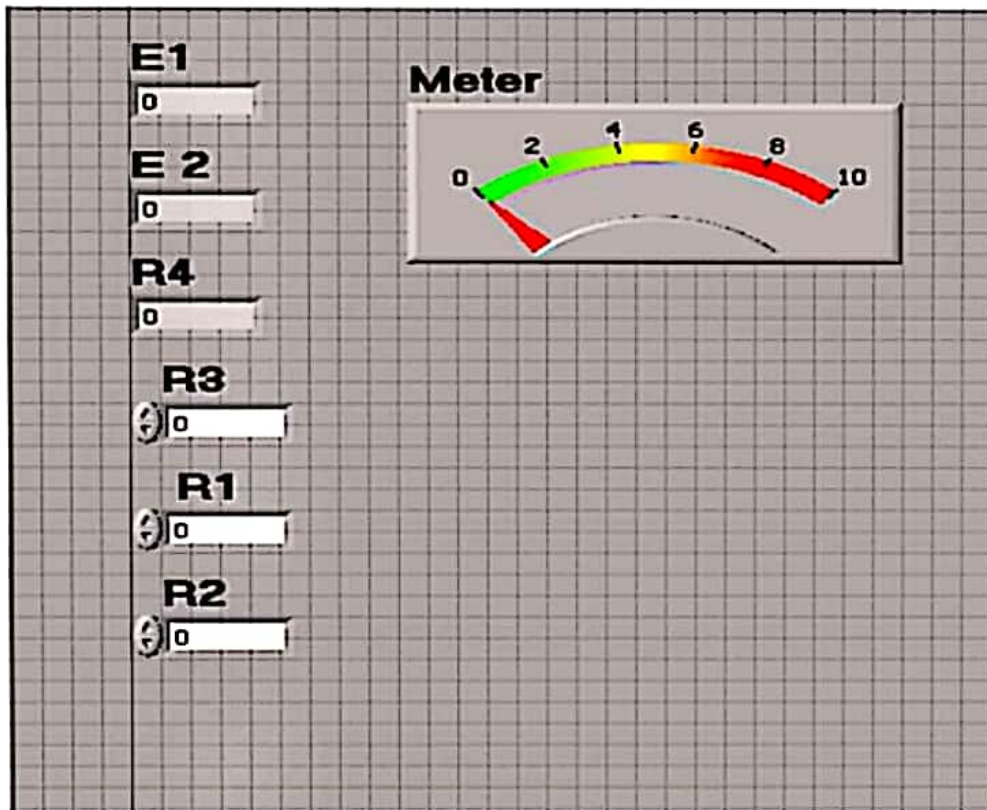

Result:

Hence the balanced condition of wheatstone's bridge is obtained and unknown values of resistances are found.